

## ECT304 VLSI CIRCUIT DESIGN

### SYLLABUS

#### MODULE-1

Module 1: VLSI Design Methodologies. (11 Hrs)		
1.1	Introduction: Moore slaw .ASIC design, Full custom ASICs, Standard cell based ASICs, Gate array based ASICs,	3
1.2	SoCs, FPGA devices	2
1.3	ASIC and FPGA Design flows Top-Down and Bottom-Up design methodologies.	3
1.4	Logical and Physical design. Speed power and area considerations in VLSI design	3

## SYLLABUS

### MODULE-2

Module 2: Static CMOS Logic Design (9 Hrs)		
2.1	<b>MOSFET Logic Design</b> - NMOS logic (Static analysis of Basic gates only)	3
2.2	CMOS logic, Static and transient analysis of CMOS inverter Switching power dissipation and delays	3
2.3	Realization logic functions in static CMOS logic, Pass transistor logic, and transmission gate logic (Static analysis only)	3

## SYLLABUS

### MODULE-3

Module 3: Dynamic logic Design and Storage Cells (8 Hrs)		
3.1	Dynamic Logic Design-Pre charge- Evaluate logic, Domino Logic, NP domino logic.	3
3.2	<b>Read Only Memory</b> -4x4 MOS ROM Cell Arrays(OR,NOR,NAND)	2
3.3	<b>Random Access Memory</b> –SRAM-Six transistor CMOS SRAM cell, DRAM –Three transistor and One transistor Dynamic Memory Cell.	3

## SYLLABUS

### MODULE-4

Module 4: Arithmetic circuits (5 Hrs)		
4.1	<b>Adders</b> - Static adder, Carry-Bypass adder, Linear Carry- Select adder, Square- root carry- select adder.	3
4.2	<b>Multipliers</b> -Array multiplier.	2

## SYLLABUS

### MODULE-5

Module 5: MOSFET physical Design and Fabrication techniques (13 Hrs)		
5.1	<b>Material Preparation</b> (qualitative analysis only) Purification and Crystal growth (CZ process), wafer preparation.	2
5.2	<b>Thermal Oxidation</b> - Growth mechanisms, Dry and Wet oxidation. Diffusion and ion implantation techniques.	3
5.3	<b>Epitaxy</b> : Molecular beam epitaxy. <b>Lithography</b> - Photo lithographic sequence, Electron Beam Lithography, Etching and metal deposition techniques	3
5.4	<b>MOSFET Fabrication techniques</b> ( <i>qualitative analysis only</i> ) Twin-Tub fabrication sequence, Fabrication process flow.	2
5.5	<b>Layout Design and Design rules</b> , Stick Diagram and Design rules- micron rules and Lambda rules. Layout of CMOS Inverter, two input NAND and NOR gates,	3


## MODULE-2

### Static CMOS logic design

## ECT304

### VLSI CIRCUIT DESIGN

## TRANSISTOR CLASSIFICATION


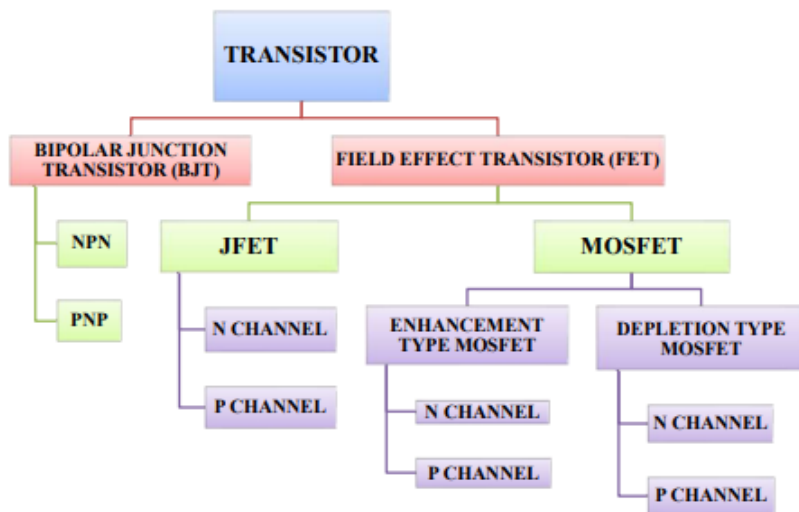


- BJT is a Current Controlled Device. i.e., output characteristics of the device is controlled by input current and not by input voltage.
- FET is a Voltage Controlled Device. i.e., output characteristics of the device is controlled by input voltage and not by input current.
- Two types of FET (Field effect Transistors)
  - Junction Field effect Transistors (JFET)
  - Metal Oxide Semiconductor/Silicon Field effect Transistors (MOSFET)

## CLASSIFICATION OF MOSFET

- **DEPLETION TYPE MOSFET OR D-MOSFET**
- Operated in both depletion/enhancement mode.
- Sometimes called as depletion/enhancement MOSFET
- **ENHANCEMENT TYPE MOSFET OR E-MOSFET**
- Can operate in Enhancement mode only

## CONSTRUCTION OF MOSFET


 
 


PROF. ARJUN PRABHUDAS, GCE KANNUR




11

## E-MOSFET SYMBOL

**P CHANNEL**

   


**N CHANNEL**

   


PROF. ARJUN PRABHUDAS, GCE KANNUR

12

## DEPLETION-MOSFET SYMBOL

 

**N CHANNEL DEPLETION TYPE MOSFET**

 


**P- CHANNEL DEPLETION TYPE MOSFET**

PROF. ARJUN PRABHUDAS, GCE KANNUR

13

## MOS TRANSISTOR OPERATION

 

$V_{gs} < 0 \rightarrow$  **ACCUMULATION MODE**

$V_t > V_{gs} > 0 \rightarrow$  **DEPLETION MODE**

$V_{gs} > V_t \rightarrow$  **INVERSION MODE**

$V_{gs} < V_t \rightarrow$  **CUT OFF REGION**


$V_{gs} > V_t \text{ \& } V_{ds} < (V_{gs} - V_t) \rightarrow$  **LINEAR REGION**

$V_{gs} > V_t \text{ \& } V_{ds} > (V_{gs} - V_t) \rightarrow$  **SATURATION REGION**

PROF. ARJUN PRABHUDAS, GCE KANNUR

14

## MOS TRANSISTOR OPERATION

 


**Figure 5.2** The enhancement-type NMOS transistor with a positive voltage applied to the gate. An  $n$  channel is induced at the top of the substrate beneath the gate.

- The induced  $n$  region thus forms a channel for current flow from drain to source
- The channel is created by inverting the substrate surface from  $p$  type to  $n$  type. Hence the induced channel is also called an **inversion layer**.
- The value of  $V_{GS}$  at which a sufficient number of mobile electrons accumulate in the channel region to form a conducting channel is called the **threshold voltage** and is denoted  **$V_t$** .
- **$V_t$**  for an  $n$ -channel MOSFET is positive.
- The value of  $V_t$  is controlled during device fabrication and typically lies in the range of 0.3 V to 1.0 V.

PROF. ARJUN PRABHUDAS, GCE KANNUR

15

## MOS TRANSISTOR OPERATION

 


**Figure 5.3** An NMOS transistor with  $v_{GS} > V_t$  and with a small  $v_{DS}$  applied. The device acts as a resistance whose value is determined by  $v_{GS}$ . Specifically, the channel conductance is proportional to  $v_{GS} - V_t$ , and thus  $i_D$  is proportional to  $(v_{GS} - V_t)v_{DS}$ . Note that the depletion region is not shown (for simplicity).

PROF. ARJUN PRABHUDAS, GCE KANNUR

16



## MOS TRANSISTOR CHARACTERISTICS

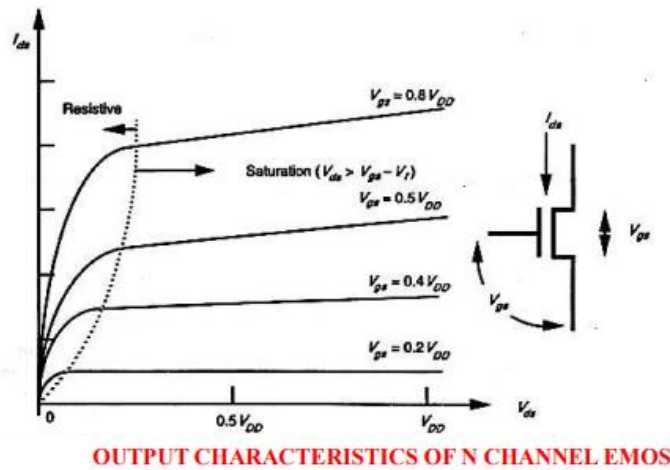

PROF. ARJUN PRABHUDAS, GCE KANNUR

17

## MOS TRANSISTOR CHARACTERISTICS

➤ Three regions of operation

1. Cut Off Region

$$V_{GS} < V_{TH}$$

$I_{DS}$  will be 0. i.e., no current flow

2. Ohmic or Resistive or Triode or Non-Saturated Region

$$V_{GS} > V_{TH} \quad \text{and} \quad V_{DS} < (V_{GS} - V_{TH})$$

$I_{DS}$  greater than 0

3. Saturation Region

$$V_{GS} > V_{TH} \quad \text{and} \quad V_{DS} \geq (V_{GS} - V_{TH})$$

$I_{DS}$  greater than 0

PROF. ARJUN PRABHUDAS, GCE KANNUR

18

## MOS TRANSISTOR CURRENT EQUATIONS

✓ Drain Current of EMOSFET is given by

$$I_{DS} = 0, \quad \text{Cut Off region}$$

$$I_{DS} = \mu C_{ox} \frac{W}{L} \left[ V_{DS}(V_{GS} - V_{TH}) - \frac{V_{DS}^2}{2} \right], \text{ Ohmic region}$$

$$I_{DS} = \mu C_{ox} \frac{W}{L} \left[ \frac{(V_{GS} - V_{TH})^2}{2} \right], \quad \text{Saturation Region}$$

- $C_{ox}$  is the Gate/Channel Capacitance per unit area ( $\text{F}/\text{cm}^2$ )
- $\mu$  is the mobility of majority carrier ( electron or hole mobility)
- $\frac{W}{L}$  is the channel width to channel length ratio of MOS
- $V_{TH}$  is the threshold voltage

## BASIC INVERTER CIRCUITS


## INVERTER CIRCUITS

- The basic requirement for producing a complete range of logic circuits is the inverter.
- Inverter is needed for restoring logic levels for NAND and NOR gates and for sequential and memory circuits of various forms.
- **CLASSIFICATION**

- **NMOS INVERTER**

- RESISTIVE LOAD
- DEPLETION TYPE LOAD
- ENHANCEMENT TYPE LOAD
- PSEUDO NMOS LOAD

- **CMOS INVERTER**

 


NOT Gate

Figure 2.1: Inverter Symbol

 
## NMOS INVERTER

- The basic inverter circuit requires a transistor with source connected to ground and a load resistor of some sort connected from the drain to the positive supply rail  $V_{DD}$ .
- The output is taken from the drain and the input applied between gate and ground.
- NMOS acts as a switch


 
## RESISTIVE LOAD NMOS INVERTER

- Here the load used is a resistor.
- This arrangement is not often used because of the large space requirements of resistors produced in a silicon substrate.
- Also standby leakage is more, poor noise margin
- Resistors are not conveniently produced on the silicon substrate; even modest values occupy excessively large areas so that some other form of load resistance is required.
- A convenient way to solve this problem is to use a transistor as the load.




PROF. ARJUN PRABHUDAS, GCE KANNUR

23
 
## DEPLETION TYPE LOAD NMOS INVERTER

- With no current drawn from the output, the currents  $I_{ds}$  for both transistors must be equal.
- For the depletion mode transistor, the **gate is connected to the source** so it is **always on** and only the characteristic curve  $V_{gs} = 0$  is relevant.
- In this configuration the **depletion mode device** is called the **pull-up (p.u.)** and the **enhancement mode device** the **pull-down (p.d.) transistor**.
- The D-MOS here acts as a nonlinear resistor (as always on)
- D-MOS work in either in Linear region or in saturation region.




PROF. ARJUN PRABHUDAS, GCE KANNUR

24
 
## DEPLETION TYPE LOAD NMOS INVERTER


- The maximum voltage across the enhancement mode device corresponds to minimum voltage across the depletion mode transistor.
- When  $V_{in}$  ( $= V_{gs}$  p.d. transistor) exceeds the p.d. threshold voltage current begins to flow.
- The output voltage  $V_{out}$ , thus decreases and the subsequent increases in  $V_{in}$  will cause the p.d. transistor to come out of saturation and become resistive.
- The p.u. transistor is initially resistive




PROF. ARJUN PRABHUDAS, GCE KANNUR

25

## DEPLETION TYPE LOAD NMOS INVERTER

 

**Figure 2.4: Derivation of NMOS Inverter transfer characteristics**

 


**Figure 2.5: NMOS Inverter transfer characteristics**

PROF. ARJUN PRABHUDAS, GCE KANNUR

26
 
## DEPLETION TYPE LOAD NMOS INVERTER

- Dissipation is high, since rail to rail current flows when  $V_{in} = \text{logical 1}$ .
- Switching of output from 1 to 0 begins when  $V_{in}$  exceeds  $V_{TH}$  of pull down device.
- When switching the output from 1 to 0, the pull up device is non-saturated initially and this presents lower resistance through which to charge capacitive loads.




PROF. ARJUN PRABHUDAS, GCE KANNUR

27
 
## ENHANCEMENT TYPE LOAD NMOS INVERTER

- Dissipation is high since current flows when  $V_{in} = \text{logical 1}$  ( $V_{GG}$  is returned to  $V_{DD}$ ).
- $V_{out}$  can never reach  $V_{DD}$  (logical 1) if  $V_{GG} = V_{DD}$  as is normally the case.




PROF. ARJUN PRABHUDAS, GCE KANNUR

28
 
## PSEUDO NMOS LOAD NMOS INVERTER

- The inverter that uses a p-device pull-up or load that has its gate permanently ground



PROF. ARJUN PRABHUDAS, GCE KANNUR

29


## CMOS INVERTER

PROF. ARJUN PRABHUDAS, GCE KANNUR

30

 
## CMOS INVERTER

- A CMOS inverter consists of two opposite polarity MOSFETs  $M_n$  (nMOS) and  $M_p$  (pMOS) with their gates connected together at the input.
- The applied voltage is denoted by  $V_{in}$ .
- The inverter output voltage  $V_{out}$  is taken from the common drain terminals.



A	$\bar{A}$
0	1
1	0

(a) Logic symbol

 

(b) CMOS circuit

## CMOS INVERTER

- An nMOS - pMOS group with a common gate is called a **complementary pair**, which gives us the “C” in “CMOS.”
- The transistors are connected in a manner that ensures that only one of the MOSFETs conducts when the input is stable at a low or high voltage.
- This is due to the use of the complementary arrangement.
- From the circuit we have

$$V_{GSn} = V_{in}$$

$$V_{SGp} = V_{DD} - V_{in}$$

- where  $V_{in}$  is assumed to be in the voltage range  $[0, V_{DD}]$  with  $V_{DD}$  the power supply.



## CMOS INVERTER – DC OPERATION

- When  $V_{in} = V_{DD}$ , i.e., high input voltage (Logic 1)

$$\begin{aligned} V_{GSn} &= V_{DD} \\ V_{SGp} &= 0 \end{aligned}$$

- pMOS  $M_p$  is in Cut off while nMOS  $M_n$  is conducting in the non-saturated mode.
- $M_n$  provide a current path to ground, resulting in an output voltage of

$$\min(V_{out}) = V_{OL} = 0$$

- where  $V_{OL}$  is called the output low voltage, and represents the smallest voltage available at the output.

PROF. ARJUN PRABHUDAS, GCE KANNUR

33

## CMOS INVERTER – DC OPERATION

- When  $V_{in} = 0$ , i.e., low input voltage (Logic 0)

$$\begin{aligned} V_{GSn} &= 0 \\ V_{SGp} &= V_{DD} \end{aligned}$$

- nMOS  $M_n$  is in Cut off while pMOS  $M_p$  is conducting in the non-saturated mode.
- The pMOS  $M_p$  provides a conductive path to the power supply and gives

$$\max(V_{out}) = V_{OH} = V_{DD}$$


- which defines the output high voltage  $V_{OH}$  of the circuit
- $V_{OH}$  is the largest value of  $V_{out}$

PROF. ARJUN PRABHUDAS, GCE KANNUR

34

## CMOS INVERTER – DC OPERATION

### CMOS INVERTER – DC OPERATION

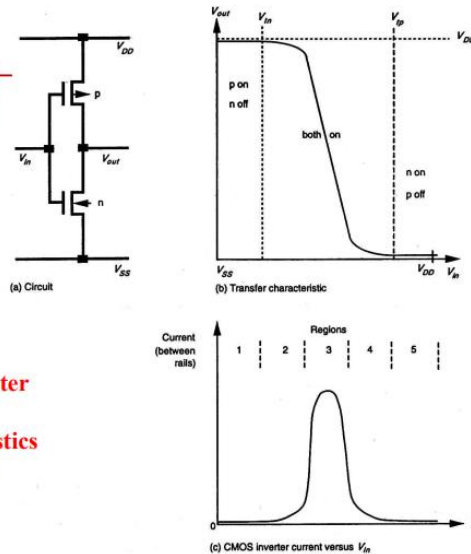

- : CMOS Inverter
- (a) Circuit
- (b) Transfer Characteristics
- (c) Current v/s Voltage

PROF. ARJUN PRABHUDAS, GCE KANNUR

35

## CMOS INVERTER – DC OPERATION

- ✓ The Current - Voltage relationships for the MOSFET is given by

$$I_D = \beta \left[ V_{DS}(V_{GS} - V_{TH}) - \frac{V_{DS}^2}{2} \right]$$

- in the resistive region or

$$I_D = \frac{\beta}{2} (V_{GS} - V_{TH})^2$$

- in the Saturation.

- where  $\beta = \mu C_{ox} \frac{W}{L}$

- ✓ CMOS inverter has five distinct regions of operation.

PROF. ARJUN PRABHUDAS, GCE KANNUR

36

## CMOS INVERTER – DC OPERATION

### ✓ Region 1

- $V_{in} = \text{logic 0}$ , we have the pMOS fully turned on while the nMOS is fully turned off.
- Thus no current flows through the inverter and the output is directly connected to  $V_{DD}$  through the p-transistor.
- A good logic 1 output voltage is thus present at the output.

### ✓ Region 5

- $V_{in} = \text{logic 1}$ , the nMOS is fully on while the pMOS is fully off.
- Again, no current flows and a good logic 0 appears at the output.



## CMOS INVERTER – DC OPERATION

### ✓ Region 2

- The input voltage has increased to a level which just exceeds the threshold voltage of the nMOS.
- The nMOS conducts and has a large voltage between source and drain; so it is in saturation.
- The pMOS is also conducting but with only a small voltage across it, it operates in the unsaturated resistive region.
- A small current now flows through the inverter from  $V_{DD}$  to  $V_{SS}$ .



## CMOS INVERTER – DC OPERATION

### ✓ Region 4

- Region 4 is similar to region 2 but with the roles of the p- and n-transistors reversed.
- The input voltage has increased to a level which just exceeds the threshold voltage of the pMOS.
- The pMOS conducts and has a large voltage between source and drain; so it is in saturation.
- The nMOS is also conducting but with only a small voltage across it, it operates in the unsaturated resistive region.
- A small current now flows through the inverter from  $V_{DD}$  to  $V_{SS}$ .

## CMOS INVERTER – DC OPERATION

### ✓ Region 3

- The current magnitudes in regions 2 and 4 are small and most of the energy consumed in switching from one state to the other is due to the larger current which flows in region 3.
- Region 3 is the region in which the inverter exhibits gain and in which both transistors are in saturation.
- The currents in each device must be the same since the transistors are in series i.e.,  $I_{dsn} = -I_{dsp}$


$$I_{dsp} = \frac{\beta_p}{2} (V_{in} - V_{DD} - V_{tp})^2 \quad \text{and} \quad I_{dsn} = \frac{\beta_n}{2} (V_{in} - V_{tn})^2$$

➤ Hence 
$$V_{in} = \frac{V_{DD} + V_{tp} + V_{tn}(\beta_n/\beta_p)^{1/2}}{1 + (\beta_n/\beta_p)^{1/2}}$$

- If  $\beta_n = \beta_p$  and if  $V_{tn} = -V_{tp}$ , then  $V_{in} = 0.5V_{DD}$
 
## CMOS INVERTER

- Because of the placement and operation of each MOSFET,  $M_n$  is called a pull-down transistor, while  $M_p$  is termed a pull-up device.




**CMOS Inverter – Input and Output Voltages**

PROF. ARJUN PRABHUDAS, GCE KANNUR

41

## CMOS INVERTER – DC CHARACTERISTICS

 

**Voltage Transfer Characteristics of CMOS Inverter**

PROF. ARJUN PRABHUDAS, GCE KANNUR

42

## CMOS INVERTER – DC CHARACTERISTICS

- The DC input-output characteristics are portrayed graphically using the Voltage-Transfer Curve (or VTC)
- This is simply a plot of  $V_{out}$  as a function of  $V_{in}$
- When  $V_{in}$  is small,  $V_{out}$  is large, and vice-versa.
- The sharpness of the transition is a measure of how well the circuit is able to perform digital operations.
- The VTC itself gives a set of critical voltages to work with in creating the defined ranges.
- The important values are the output voltages ( $V_{OH}$  and  $V_{OL}$ ), the input voltages ( $V_{IH}$  and  $V_{IL}$ ), and the inverter threshold voltage ( $V_I$ ).
- Assume that the MOSFETs have known device transconductance values of

$$\beta_n = k'_n \left( \frac{W}{L} \right)_n \quad \text{and} \quad \beta_p = k'_p \left( \frac{W}{L} \right)_p$$

PROF. ARJUN PRABHUDAS, GCE KANNUR

43

## CMOS INVERTER – DC CHARACTERISTICS

- This means that the layout has been completed and the aspect ratios  $(W/L)_n$  and  $(W/L)_p$  are known quantities.
- The critical voltages are established by the MOSFET parameters and characterize the DC response of the circuit.
- These are directly related to the method we use to define logic 0 and logic 1 levels.
- In CMOS circuit design, only the device aspect ratios  $(W/L)_n$  (for nMOS) and  $(W/L)_p$  (for the pMOS) can be adjusted in the design phase.
- The other electrical parameters such as  $k'$  and  $V_{TH}$  and are a result of the fabrication and cannot be changed.
- The critical voltages may be computed by setting the input voltage to the desired value and then equating the drain currents  $I_{Dn} = I_{Dp}$  at the output node.

PROF. ARJUN PRABHUDAS, GCE KANNUR

44

## CMOS INVERTER – DC CHARACTERISTICS

### ✓ OUTPUT HIGH VOLTAGE ( $V_{OH}$ )

- The output-high voltage  $V_{OH}$  is the largest value of  $V_{out}$ .
- It may be calculated by applying an input voltage  $V_{in} < V_{THn}$  which insures that the nMOS is in cut off while the pMOS is biased into the active region.
- Ideally, the simplified MOSFET equations give  $I_{Dp}=0$ , which implies that the source-drain voltage  $V_{SDp}=0$ .
- Since the source of the pMOS is connected to the power supply voltage  $V_{DD}$ , KVL gives

$$V_{out} = V_{DD} - V_{SDp} = V_{DD} = V_{OH}$$

PROF. ARJUN PRABHUDAS, GCE KANNUR

45

## CMOS INVERTER – DC CHARACTERISTICS

### ✓ OUTPUT LOW VOLTAGE ( $V_{OL}$ )

- The output-low voltage  $V_{OL}$  represents the smallest value of  $V_{out}$  from the circuit.
- Setting the input voltage to a value  $V_{in} = V_{DD} > (V_{DD} - |V_{THp}|)$  places  $M_p$  in cut off and defines the condition needed to calculate the value of  $V_{out}=V_{OL}$
- Since  $M_n$  is biased active but has  $I_{Dn}=0$ , the drain-source voltage across the nMOS is  $V_{DSn}=0$ .
- The inverter output is given by

$$V_{out} = V_{DSn} = 0 = V_{OL}$$

PROF. ARJUN PRABHUDAS, GCE KANNUR

46

## CMOS INVERTER – DC CHARACTERISTICS

- An important property of CMOS is that the output logic swing  $V_L$  is given by

$$\begin{aligned} V_L &= V_{OH} - V_{OL} \\ &= V_{DD} \end{aligned}$$

- This shows that the CMOS inverter exhibits a **full-rail** output voltage swing, i.e., the entire power supply range.
- This helps provide well-defined logic 0 and logic 1 voltages.



## CMOS INVERTER – DC CHARACTERISTICS

### ✓ INPUT LOW VOLTAGE ( $V_{IL}$ )

- The input low voltage  $V_{IL}$  represents the largest value of  $V_{in}$  that can be interpreted as a logic 0 input.
- If the input voltage satisfies  $V_{in} < V_{IL}$  then the output voltage  $V_{out}$  is either at  $V_{DD}$  or close to it, indicating that the output can be interpreted as a logic 1.
- If  $V_{in}$  is increased above  $V_{IL}$ , the circuit moves into the transition region.
- Using stability arguments, we define  $V_{IL}$  as the point where the slope of the VTC has a value of -1, i.e.,

$$\frac{dV_{out}}{dV_{in}} = -1$$





## CMOS INVERTER – DC CHARACTERISTICS

### ✓ INPUT LOW VOLTAGE ( $V_{IL}$ )

- At this point, the  $M_n$  is saturated while the  $M_p$  is conducting in the non-saturated mode.
- Equating currents  $I_{Dn} = I_{Dp}$  gives

$$\frac{\beta_n}{2}(V_{in} - V_{THn})^2 = \frac{\beta_p}{2}[2(V_{DD} - V_{in} - |V_{THp}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2]$$

**EQN 2.13**

- The derivative condition is applied by first writing the functional relationship

$$I_{Dn}(V_{in}) = I_{Dp}(V_{in}, V_{out})$$

- Taking differentials of both sides gives

## CMOS INVERTER – DC CHARACTERISTICS

### ✓ INPUT LOW VOLTAGE ( $V_{IL}$ )

- Substituting and calculating the derivatives yields

$$V_{in}\left(1 + \frac{\beta_n}{\beta_p}\right) = 2V_{out} - V_{DD} - |V_{THp}| + \frac{\beta_n}{\beta_p} V_{THn}$$

## CMOS INVERTER – DC CHARACTERISTICS

### ✓ INPUT HIGH VOLTAGE ( $V_{IH}$ )

- The input high voltage  $V_{IH}$  is the smallest value of  $V_{in}$  that can be interpreted as a logic 1 level.
- An input voltage of  $V_{in} \geq V_{IH}$  gives an output voltage that is either 0V or close to it.
- To calculate  $V_{IH}$ , we use the current flow equations and the unity slope condition as in finding  $V_{IL}$ .
- Now,  $M_n$  is non-saturated while  $M_p$  is saturated so that equating currents gives

$$\frac{\beta_n}{2} [2(V_{in} - V_{THn})V_{out} - V_{out}^2] = \frac{\beta_p}{2} (V_{DD} - V_{in} - |V_{THp}|)^2$$



## CMOS INVERTER – DC CHARACTERISTICS

### ✓ INPUT HIGH VOLTAGE ( $V_{IH}$ )

- Substituting the current equations and differentiating equation

$$V_{in} \left(1 + \frac{\beta_p}{\beta_n}\right) = 2V_{out} + V_{THn} + \frac{\beta_p}{\beta_n} (V_{DD} - |V_{THp}|)$$



## CMOS INVERTER – DC CHARACTERISTICS

### ✓ INVERTER THRESHOLD (MIDPOINT) VOLTAGE ( $V_I$ )

- The voltage  $V_I$  is called the **inverter gate threshold voltage**, and is defined by the point where the voltage transfer curve intersects the unity gain line defined by  $V_{out}=V_{in}$
- $V_I$  is the midpoint between the borders of the logic 0 and logic 1 input voltages  $V_{IL}$  and  $V_{IH}$  and is a very useful parameter that characterizes the entire VTC.
- This gives rise to the alternate notation and terminology in the literature for this voltage as  $V_M$ , **the midpoint voltage**.

## CMOS INVERTER – DC CHARACTERISTICS

### ✓ INVERTER THRESHOLD (MIDPOINT) VOLTAGE ( $V_I$ )

- The value of  $V_I$  can be found by definition,

$$V_{out} = V_{in} = V_I$$

- so that

$$V_{GSn} = V_I = V_{DSn}$$

$$V_{SGp} = V_{DD} - V_I = V_{SDp}$$

- holds for the MOSFET voltages.
- These equations show that both the nMOS and the pMOS are operating in the saturation region.
- Equating currents gives

$$\frac{\beta_n}{2} (V_I - V_{THn})^2 = \frac{\beta_p}{2} (V_{DD} - V_I - |V_{THp}|)^2$$

## CMOS INVERTER – DC CHARACTERISTICS

### ✓ INVERTER THRESHOLD (MIDPOINT) VOLTAGE ( $V_I$ )

➤ so that

$$V_I = \frac{V_{DD} - |V_{THp}| + \sqrt{\frac{\beta_n}{\beta_p}} V_{THn}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}} = V_M$$


➤ gives the desired result.

➤ Note that the device ratio  $\frac{\beta_n}{\beta_p}$  is the important quantity that determines the value of  $V_I$  for a given circuit.



## CMOS INVERTER – DC CHARACTERISTICS

### ✓ INTERPRETATION OF CRITICAL VOLTAGES

 

**Figure 2.12: Interpretation Of Critical Voltages**



## CMOS INVERTER – DC CHARACTERISTICS

### ✓ INTERPRETATION OF CRITICAL VOLTAGES

- Consider the input voltage  $V_{in}$  as it is increased from 0V.
- For input voltages in the range  $0 \leq V_{in} \leq V_{IL}$ , the output voltage is high at either a perfect logic 1 voltage  $V_{out} = V_{DD}$  or very close to it.
- This then allows us to identify this range of voltages as logic 0 input values.
- When  $V_{in}$  is in the high range defined by  $V_{IH} \leq V_{in} \leq V_{DD}$ , then the output voltage is either at a perfect logic 0 value  $V_{out} = 0V$  or very close to it.
- We thus identify these values of  $V_{in}$  as corresponding to logic 1 inputs.



## CMOS INVERTER – DC CHARACTERISTICS

### ✓ INTERPRETATION OF CRITICAL VOLTAGES

- The inverter threshold voltage always has the characteristic that  $V_{IL} \leq V_I \leq V_{IH}$
- We may thus interpret this as the midpoint voltage  $V_M = V_I$  such that
 

$V_{in} < V_M \rightarrow \text{Input is probably a logic 0}$   
 and  
 $V_{in} > V_M \rightarrow \text{Input is probably a logic 1}$
- with  $V_{IL}$  and  $V_{IH}$  providing more precise limits.



## CMOS INVERTER – DC CHARACTERISTICS

### ✓ NOISE MARGINS

- The meaning of the critical input and output voltages gains greater significance when coupled to the concept of noise margins.
- Consider the situation in Figure 2.13a where the input of an inverter is close to a neighbouring interconnect line.

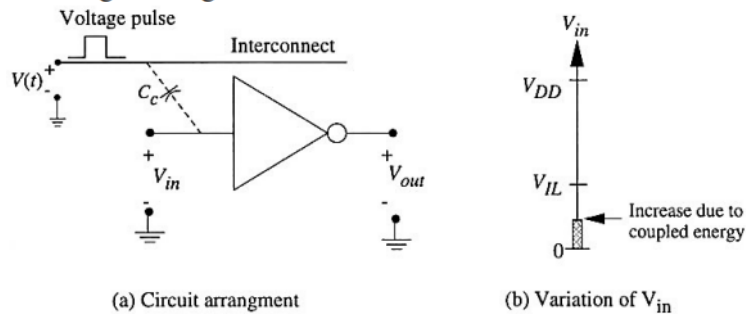


Figure 2.13: Noise Margin

## CMOS INVERTER – DC CHARACTERISTICS

### ✓ NOISE MARGINS

- A parasitic coupling capacitance  $C_C$  exists between the two, so that applying a voltage pulse to one line will cause a change in the voltage in the other.
- Suppose that the input to the inverter is initially at 0v.
- With this type of electric coupling, the value of  $V_{in}$  can jump to a voltage as shown in Figure 2.13b.
- If the increase is large, then an incorrect switching event may occur.
- However, so long as the input voltage remains below  $V_{IL}$ , then the input will still be correctly interpreted as a logic 0 voltage.
- *Noise margins provide a quantitative measure of how resistant a circuit is to false switches.*

## CMOS INVERTER – DC CHARACTERISTICS

### ✓ NOISE MARGINS


- We define the voltage noise margin for logic 1 (high) voltages as

$$\begin{aligned} \text{VNM}_H &= V_{OH} - V_{IH} \\ &= V_{DD} - V_{IH} \end{aligned}$$

- Similarly, the voltage noise margin for logic 0 (low) voltages as

$$\begin{aligned} \text{VNM}_L &= V_{IL} - V_{OL} \\ &= V_{IL} \end{aligned} \quad \text{EQN 2.25}$$

Figure 2.14: Noise Margins

 

PROF. ARJUN PRABHUDAS, GCE KANNUR

61

## CMOS INVERTER – DC CHARACTERISTICS

### ✓ NOISE MARGINS

- For a functional digital circuit, we must have  $\text{VNM}_L > 0$  and  $\text{VNM}_H > 0$
- Noise margins are particularly important when designing low voltage circuits, i.e., those with small power supply values.
- This is because as  $V_{DD}$  shrinks, the definitions of logic 0 and 1 voltage ranges also shrink, and the gates are more susceptible to spurious signals from neighboring lines.

PROF. ARJUN PRABHUDAS, GCE KANNUR

62