

## **MODULE-2**

**1.CMOS Inverter Switching Characteristics**


**2.Power dissipation in CMOS**

**ECT304**

**VLSI CIRCUIT DESIGN**


 
# CMOS INVERTER SWITCHING CHARACTERISTICS

- Transient switching times are used to calculate data throughput rates and are also important in system timing.
- Switching times are determined by two circuit properties: Transistor current flow levels & parasitic capacitances.
- Both are set by the chip design parameters and are sensitive to transistor aspect ratios, layout geometry and logic routing.
- In this CMOS inverter PMOS is pull up device and NMOS is the pull down device.
- ***When the Input is High the NMOS will be ON and Capacitor  $C_{out}$  will discharge and Output will be Low.***
- ***When the Input is Low the PMOS will be ON and Capacitor  $C_{out}$  will charge and Output will be High.***




 
 
# CMOS INVERTER SWITCHING CHARACTERISTICS

- High-speed digital system design is based on the ability to perform calculations very quickly.
- This requires that logic gates introduce a minimum amount of time delay when the inputs change.
- Designing fast logic circuits is one of the more challenging (but critical) aspects of VLSI physical design.
- An input voltage  $V(t)$  is applied to the inverter, resulting in an output voltage  $V_{out}(t)$ .
- Assume that  $V_{in}(t)$  has step-like characteristics and makes an abrupt transition from 0 to 1 at time  $t_1$  and back to 1 to 0 at time  $t_2$ .
- The output waveform reacts to the input, but output voltage cannot change instantaneously.



  
 
# CMOS INVERTER SWITCHING CHARACTERISTICS

- The output 1 to 0 transition introduces a **Fall time delay**
- The output 0 to 1 transition introduces a **Rise time delay**
- The Rise time and Fall time delays are due to the **parasitic resistance and capacitances of the transistors**.



- The simplified RC model of the inverter circuit is shown with transistors replaced by switches.
  
# CMOS INVERTER SWITCHING CHARACTERISTICS




- The parasitic resistance  $R_n$  and  $R_p$  is given by

$$R_n = \frac{1}{\beta_n (V_{DD} - V_{Tn})}$$

$$R_p = \frac{1}{\beta_p (V_{DD} - |V_{Tp}|)}$$
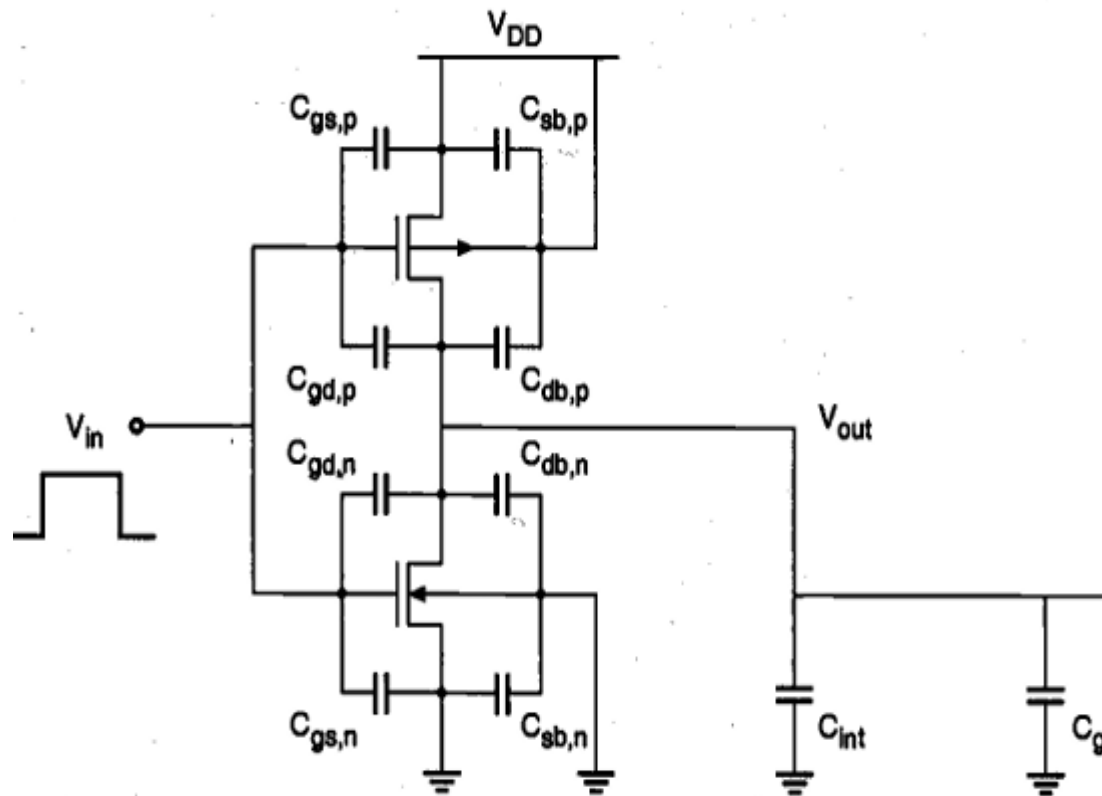
# CMOS INVERTER SWITCHING CHARACTERISTICS



## Load Capacitance

$$C_{load} = C_{gd,n} + C_{gd,p} + C_{db,n} + C_{db,p} + C_{int} + C_g$$



- The capacitances  $C_{gd}$  and  $C_{gs}$  are primarily due to gate overlap with diffusion
- while  $C_{db}$  and  $C_{sb}$  are voltage-dependent junction capacitances
- The capacitance component  $C_g$  is due to the thin-oxide capacitance over the gate area.
- the lumped interconnect capacitance  $C_{int}$ , represents the parasitic capacitance contribution of the metal or polysilicon connection between the two inverters.

# CMOS INVERTER SWITCHING CHARACTERISTICS
  
## FALL TIME ( $t_F$ )

- **Fall Time:** Time interval from where output drops from  $0.9V_{DD}$  to  $0.1V_{DD}$
- Initial Condition,  $V_{out} = V_{DD}$
- When input is switched **PMOS – OFF & NMOS – ON**
- Capacitor discharges to 0 through  $R_n$ .
- Current is leaving the capacitor, so
$$i = -C_{out} (dv_{out}/dt)$$

- Solving the initial condition
$$V_{out}(t) = V_{DD} \cdot e^{-t/\tau_n}$$
$$e^{-t/\tau_n} = V_{out} / V_{DD}$$
$$T = \tau_n \ln(V_{DD}/V_{out})$$



# CMOS INVERTER SWITCHING CHARACTERISTICS

## FALL TIME ( $t_F$ )

- **Fall Time:** Time interval from where output drops from  $0.9V_{DD}$  to  $0.1V_{DD}$


$$T = \tau_n \ln(V_{DD}/V_{out})$$

$$T_f = t_y - t_x$$

$$= \tau_n \ln(V_{DD}/0.1V_{DD}) - \tau_n \ln(V_{DD}/0.9V_{DD})$$

$$= \tau_n \ln(9)$$

$$T_f = 2.2 \tau_n$$


 




# CMOS INVERTER SWITCHING CHARACTERISTICS
  
## RISE TIME ( $t_R$ )

- **Rise Time:** Time interval where output increase from  $0.1V_{DD}$  to  $0.9V_{DD}$
- Initial Condition,  $V_{out} = 0$
- When input is switched **PMOS – ON & NMOS – OFF**
- Capacitor charged to  $V_{DD}$  through  $R_p$ .
- Charging current, so  
 $i = C_{out} (dv_{out}/dt)$



- Solving the initial condition  $V_{out}(t) = V_{DD}[1 - e^{-t/\tau_p}]$   
 $\tau_p = R_p C_{out}$   
 $e^{-t/\tau_p} = (V_{DD} - V_{out}) / V_{DD}$   
 $T = \tau_p \ln(V_{DD} / (V_{DD} - V_{out}))$

# CMOS INVERTER SWITCHING CHARACTERISTICS

## RISE TIME ( $t_R$ )

- **Rise Time:** Time interval where output increase from  $0.1V_{DD}$  to  $0.9V_{DD}$


$$T = \tau_p \ln.[V_{DD}/(V_{DD} - V_{out})]$$

$$T_r = t_v - t_u$$

$$= \tau_p \ln(V_{DD}/V_{DD} - 0.9V_{DD}) - \tau_p \ln(V_{DD}/V_{DD} - 0.1V_{DD})$$

$$= \tau_p \ln(9)$$

$$T_r = 2.2 \tau_p$$

 

# CMOS INVERTER SWITCHING CHARACTERISTICS


## PROPAGATION DELAY ( $t_p$ )

- It is used to estimate delay time from input to output.
- It is given by  $T_p = (t_{pf} + t_{pr})/2$
- $T_{pf}$  - time interval for the output to fall from maximum level to 50% of voltage (  $V_{DD}$  to  $0.5 V_{DD}$  )
- $T_{pr}$  - time interval for the output to rise from minimum level to 50% of voltage (  $0$  to  $0.5 V_{DD}$  )

$$T_{pf} = \ln 2 \tau_n$$

$$T_{pr} = \ln 2 \tau_p$$

$$T_p = 0.35(\tau_n + \tau_p)$$

 


# SOURCES OF POWER DISSIPATION IN CMOS

- Power dissipation in CMOS comes from two components.
- **Dynamic dissipation due to**
  - **Charging and discharging load capacitance** as gate switches.
  - **Short circuit current** while both PMOS & NMOS are partially ON.

$$P_{\text{dynamic}} = P_{\text{switching}} + P_{\text{short circuit}}$$

 - **Static dissipation due to**
  - Sub threshold leakage through OFF transistors
  - Gate leakage through the gate dielectric
  - Junction leakage from source/drain diffusions.




# DYNAMIC POWER DISSIPATION

- **SWITCHING POWER DISSIPATION**

- Switching Power Dissipation represents the **power dissipation during a switching event**.
- Switching power dissipation means the **power dissipation due to charging and discharging of load capacitor** due to the transition of input from 1 to 0 or 0 to 1 state.
- consider the circuit given in Fig. Here, a two- input NOR gate drives two NAND gates, through interconnection lines. The total capacitive load at the output of the NOR gate consists of

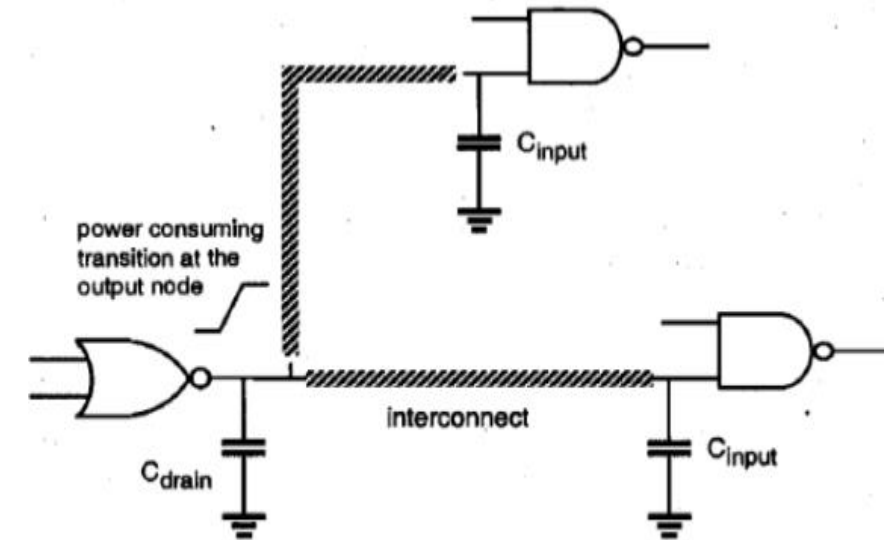- (1) The output capacitance of the gate itself
- (2) The total interconnect capacitance, and
- (3) The input capacitances of the driven gates.




A NOR gate driving two NAND gates through interconnection lines.

# DYNAMIC POWER DISSIPATION

- **SWITCHING POWER DISSIPATION**
- **Output capacitance:**
  - Consists mainly of the junction parasitic capacitances, which are due to the drain diffusion regions of the MOS transistors in the circuit.
  - The size of the total drain diffusion area determines the amount of parasitic capacitance.
- **Total interconnect capacitance:**
  - The interconnect lines between the gates contribute to the total interconnect capacitance.
  - In sub-micron technologies, the interconnect capacitance can become the dominant component, compared to the transistor-related capacitances.
- **Input capacitances:**
  - Due to gate oxide capacitances of the transistors connected to the input terminal.
  - The amount of the gate oxide capacitance is determined primarily by the gate area of each transistor.
 
# DYNAMIC POWER DISSIPATION

- **SWITCHING POWER DISSIPATION CALCULATION**






- To find the **dynamic power dissipation** we use a square wave input  $v_{in}(t)$ . The period of the wave form is  $T$
- In 1st half cycle  $\rightarrow V_{in}=0$
- **NMOS is OFF, PMOS is ON**, current  $I_{DD}$  flows through PMOS and  $C_{out}$  charges to a voltage of  $V_{out}=V_{DD}$



# DYNAMIC POWER DISSIPATION
   
## • SWITCHING POWER DISSIPATION CALCULATION



- In 2<sup>nd</sup> half cycle → The input voltage is high and capacitor  $C_{out}$  discharges and  $V_{out}$  becomes zero.
- The dynamic power  $p_{dyn}$  arises from the observation that a complete cycle create a path for the current to flow from the power supply to ground.
- The charging event makes  $C_{out}$  with a output voltage of  $V_{DD}$



# DYNAMIC POWER DISSIPATION

## • SWITCHING POWER DISSIPATION CALCULATION

- The stored charge in a capacitor is given by  $Q_e = C_{out} \cdot VDD$
- When the capacitor discharges the same amount of charge is lost.
- The average power dissipated over a single cycle with period T

$$P_{avg} = \frac{1}{T} \int_0^T i_{DD}(t) \cdot VDD dt$$

$$V = \frac{1}{C} \int i dt$$

$$\int i dt = C V$$

$$\int_0^T i_{DD}(t) \cdot dt = C_{out} \cdot VDD$$

$$P_{avg} = \frac{1}{T} C_{out} \cdot VDD \cdot V_{DD}$$

# DYNAMIC POWER DISSIPATION

- **SWITCHING POWER DISSIPATION CALCULATION**

$$P_{avg} = \frac{1}{T} C_{out} \cdot VDD \cdot V_{DD}$$



$$P_{avg} = \frac{C_{out} \cdot VDD^2}{T} = C_{out} \cdot VDD^2 \cdot f$$

**Switching power dissipation** depends on **Output load capacitance**, **switching frequency** and **square of supply voltage**
  
# DYNAMIC POWER DISSIPATION

- **SHORT CIRCUIT POWER DISSIPATION**

- As the input changes slowly, there will be certain duration of time for which some of the transistor(s) in the pull-up network and pull-down network are turned 'ON' simultaneously, **forming a short-circuit path from  $V_{DD}$  to GND**
- This is called **Short Circuit power dissipation**.



# STATIC POWER DISSIPATION

- **Power dissipation in CMOS when there is no input transition.**
- The nMOS and pMOS transistors used in a CMOS logic gate generally have nonzero reverse leakage and sub threshold currents.
- In a CMOS VLSI chip containing a very large number of transistors, these currents can contribute to the overall power dissipation even when the transistors are not undergoing any switching event.
- **Static power dissipation in CMOS inverter is comparatively less than when compared with NMOS inverter.**
- The magnitude of the leakage currents is determined mainly by the processing parameters.
- Two main leakage current components found in a MOSFET are
  - (1) Reverse diode leakage current
  - (2) Sub threshold leakage current