

# PHASE LOCKED LOOP (PLL)

PREPARED BY RINJU RAVINDRAN, EDI/OC ASST. PROFESSOR-ECE, GCEK

# Phase Lock Loop Applications

## Applications

**Synchronization and Demodulation Circuits**

**Clock Recovery**

**Noise and Jitter Reduction**

**Frequency Synthesizers**

**Microprocessors (Clock Multiplier and Clock Distribution)**

## Clock Recovery



## Noise and Jitter Reduction



## Frequency Synthesizer




PREPARED BY RINJU RAVINDRAN, ADHOC

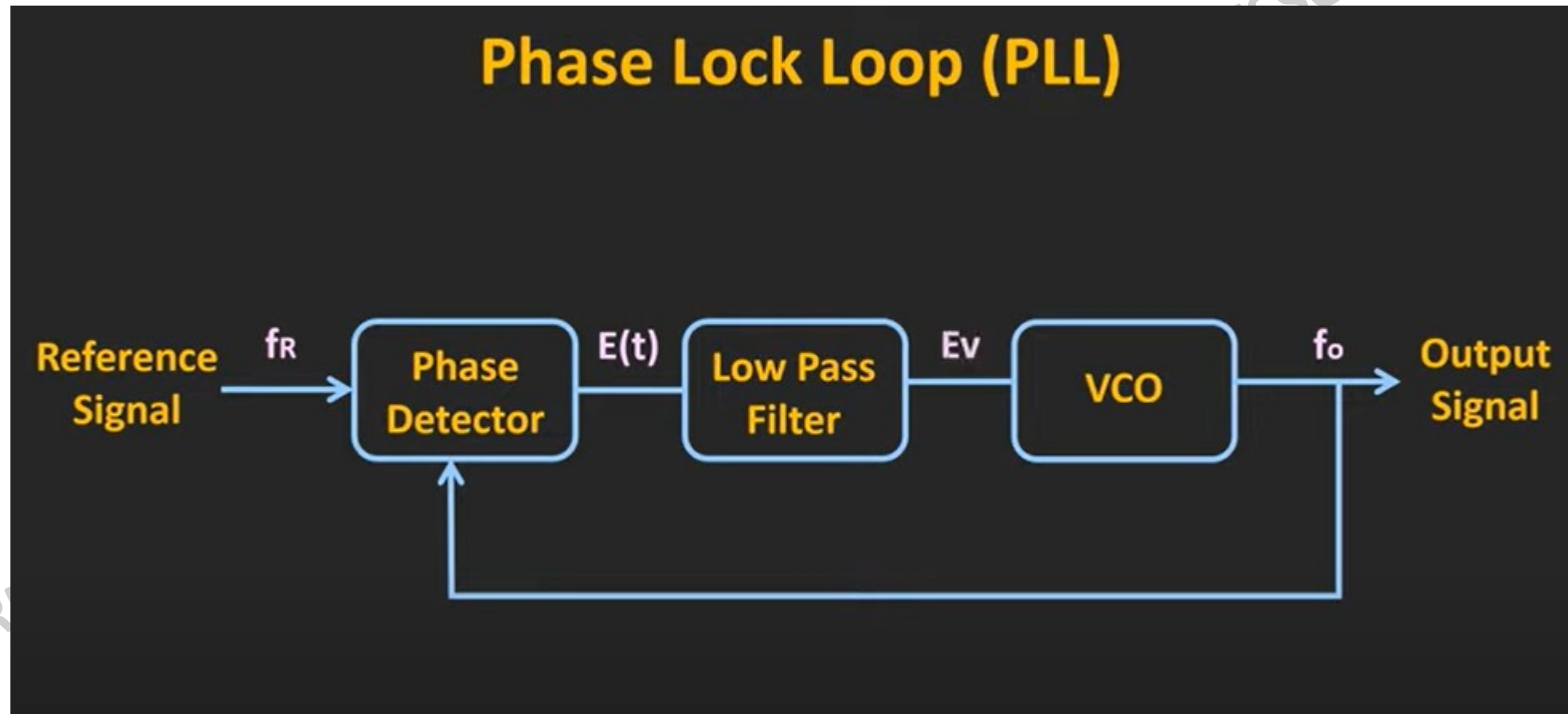
# PLL

- It is a control s/m or control loop which maintains the same phase btw the i/p & o/p s/g.
- PLL synchronises o/p and i/p in phase as well as freq.
- PLL is a system that generates an output signal whose phase is related to its input.
- The two signals will have the same frequency and either no phase difference or a constant phase difference between them.

$f_o = f_{in}$  & , we can say that loop is in the lock condition.



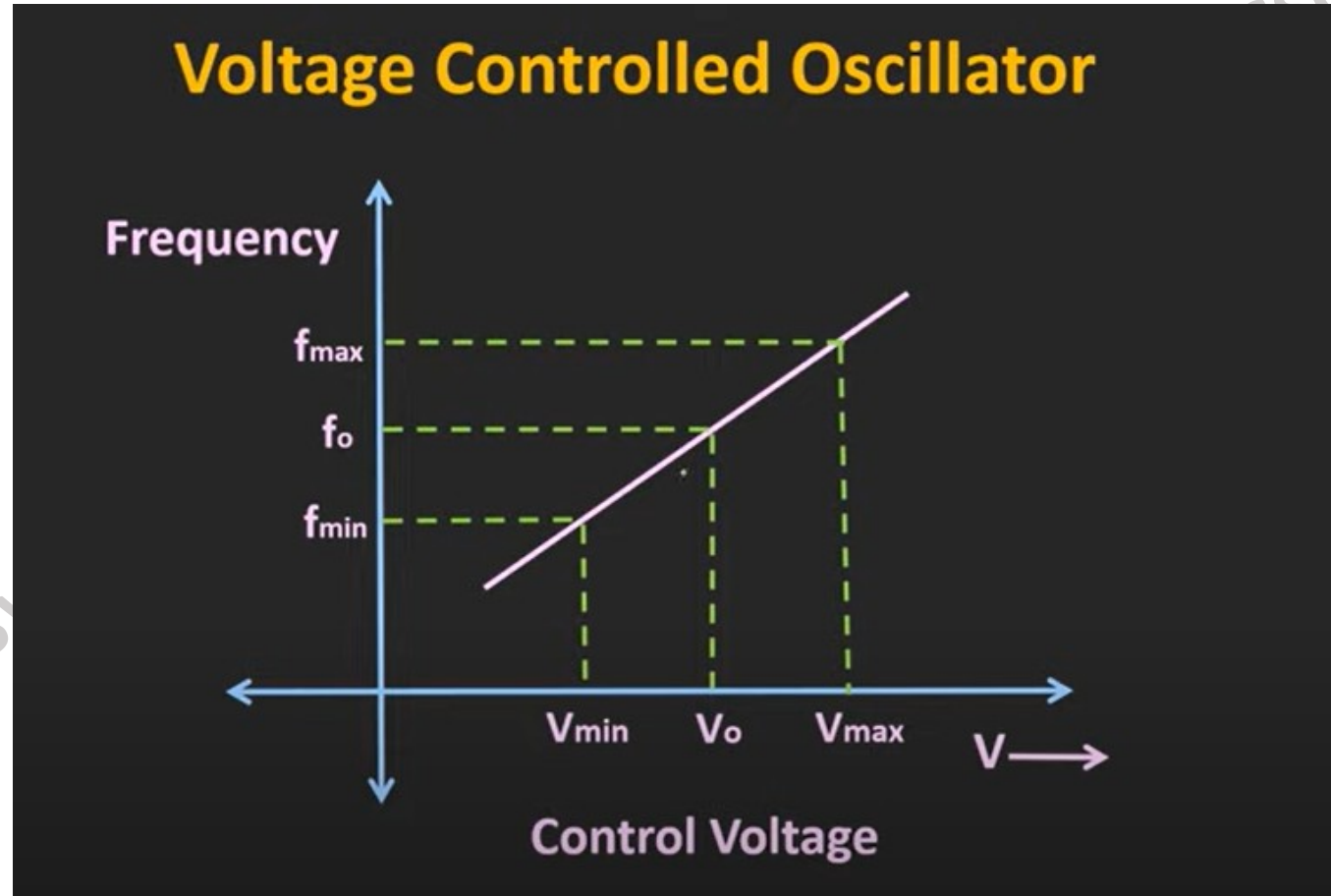VCO : As the control  $V$  changes, freq of oscn also changes.



# OPERATING PRINCIPLES:

- Whenever loop is turned ON, VCO runs at centre freq  $f_0$  (free running freq).
- A **phase detector or comparator** compares the i/p or reference freq  $f_R$  with the f/b freq  $f_0$ .
- o/p of phase detector is proportional to the phase difference btw  $f_R$  &  $f_0$ .
- The output  $V$  of a phase detector is a dc voltage and is called as **error voltage**.



- o/p of P.D. is applied to **LPF** which removes high freq noise and produce a DC level.
- Filter also helps in establishing dynamic chara of PLL ckt.
- This DC level is given as i/p to **VCO**.
- o/p freq of VCO is directly proportional to the i/p dc level.
- VCO freq is compared with i/p freq and adjusted until it is equal to the i/p freqs.

# PLL goes thru 3 states:


- ☐ Free running
- ☐ Capture
- ☐ Phase lock

PREPARED BY RINJU RAVINDRAN, ADHOC ASST. PROFESSOR-ECE, GCEK

- Before the i/p is applied, PLL is in **free running state**.
- Once i/p freq is applied, VCO freq starts to change and PLL is said to be in **capture mode**.
- VCO freq continues to change until it equals the i/p freq and PLL is then in the **phase locked** state.
- When phase locked, the loop tracks any change in the i/p freq thru its repetitive action.

 
# Capture Range:

- Range of i/p freqs around the VCO centre freq onto which the loop can lock when starting from the unlocked condition.


 
# Lock (Tracking) Range:


- Range of i/p freqs over which the loop remain in the lock condition once it has captured the i/p s/g.
- Lets say VCO is already locked to i/p freq  $f$ .



- If i/p freq changes, then VCO will follow that freq if i/p freq is within the lock range.



 - But if i/p freq goes out of lock range, VCO starts running at the free running freq.



- It won't be able to lock to the i/p freq until the i/p freq is within the capture range of PLL.


**Pull in time: total time taken by PLL to establish lock.** This depends on the initial phase and frequency difference between the two signals as well as on the overall loop gain and loop filter characteristics.

- **Capture range is symmetrically located with respect to the VCO free running freq.**
- PLL cannot acquire a s/g outside capture range, but once captured it will hold on till the s/g freq goes beyond lock in range.
- In order to increase the ability of lock in range, large capture range is required.
- But a large capture range will make PLL more susceptible to noise and undesirable signal.
- Hence a suitable compromise is often reached btw these 2 opposing requirements of the capture range.



- Many a times, BW of LPF is first set for a large value for initial acquisition of s/g, then once the s/g is captured, BW of LPF is reduced substantially.
- This will minimize interference of undesirable s/gs and noise.

(VCO control voltage)

 

**Fig. 9.11** PLL lock-in range and capture range

- Lock in range

$$= K_v K_\phi A \pi$$

$$= K_v K_\phi A (\pi/2)$$

- Capture range

$K_v$  = voltage to freq transfer coefficient of VCO

$K_\phi$  = phase angle to voltage transfer coefficient of phase detector.

$A$  = voltage gain of amplifier

$$f_1 = 1/2\pi RC$$

- Lets say at a given pt of time, 1 s/g has phase and other has phase
- Phase diff = -
- If phase difference is very small, then - = -
- 2<sup>nd</sup> term HF s/g eliminated using LPF.
- So jz by multiplying 2 s/gs, it is possible to generate phase diff btw them.

## Phase Detector


$$\alpha \quad \beta \quad \Rightarrow \quad \text{Phase Difference} = \alpha - \beta \approx \sin(\alpha - \beta)$$

$$\sin(\alpha - \beta) = \sin \alpha \cos \beta - \sin \beta \cos \alpha$$

$$\sin \alpha \cos \beta = \frac{\sin(\alpha - \beta)}{2} + \underbrace{\frac{\sin(\alpha + \beta)}{2}}_{\text{LPF}}$$

In freq domain

### Phase Detector

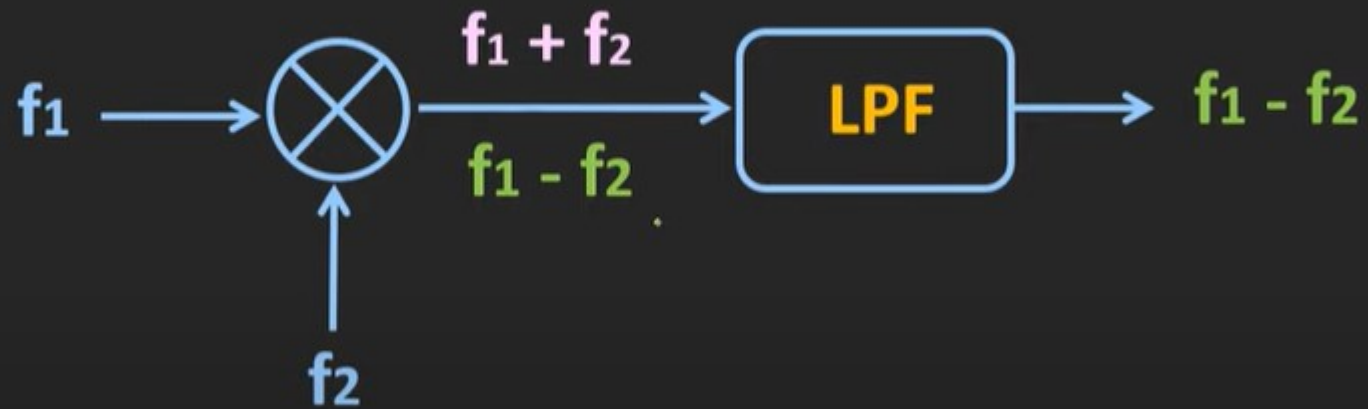

# Types of phase detector used:

**Phase Detector**

**RF Applications: Balanced Mixer**

**Digital Signals: XOR Gate**

**Phase Frequency Detector**

# How XOR gate can be used as a phase detector?

Phase Detector



XOR Gate





X	Y	Output
0	0	0
0	1	1
1	0	1
1	1	0



 
 
- Whenever 2 i/ps are different, o/p is high.
- When no phase shift btw 2 s/gs, ideally XOR o/p = 0
- Practically there will be spikes at transition.
- Avg of phase difference s/g = 0.



  
- When phase diff btw 2 s/gs = 90 deg:
- If we take avg of phase diff s/g, we will get o/p V = half of the peak value.



  - When phase diff = 180, o/p will be max. and ideally high for all time.
- But practically, spikes at transition.
- Avg of this o/p w/f will give max value.



 - That is , as phase difference btw 2 s/gs increases, avg value of o/p w/v will increase.




- Slope of curve = conversion gain of phase detector =  $k_\phi$

$$k_\phi =$$



- If XOR gate uses a supply voltage  $V_{cc} = V = 5\text{V}$ , then
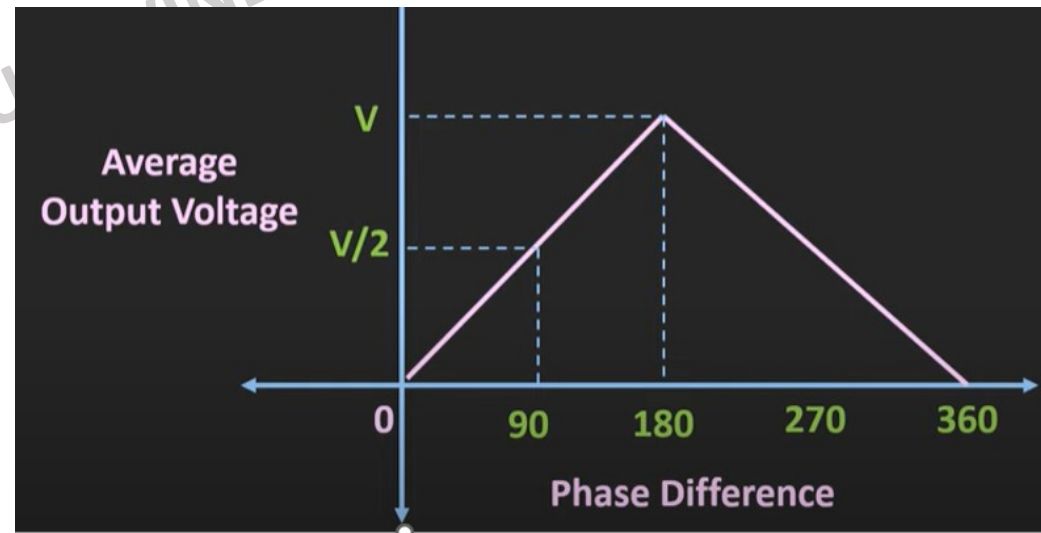
$$k_\phi = \quad = \quad = 1.59 \text{ V/rad}$$



- When phase diff btw 2 s/gs increases from 0 to 180, avg o/p V also increases linearly.
- So this is a **linear phase detector**.
- But it is linear only till 180.
- When p.d. increases from 180 to 360, avg o/p V starts decreasing.
- And it is also difficult to identify which s/g is leading/lagging.

  - Irrespective of  $V_1$  lagging or leading  $V_2$ , we get same o/p.



- For XOR gate to work as linear phase detector, both s/gs shud be square waves (must have approx. 50% duty cycle).

PREPARED BY RINJU RAVINDRAN, ADHOC ASST. PROFESSOR-ECE, GCEK



# Edge triggered phase detector

- Preferred if i/p s/gs are pulse waveforms with  $< 50\%$  duty cycle.
- Advs over XOR type of detector:
  1. Dc o/p  $V$  is linear over  $2\pi$  radians or 360 deg
  2. Exhibits better capture, tracking and locking characteristics than XOR type.

- Uses a SR FF.
- SR FF is formed from a pair of cross coupled NOR gates.
- o/p of detector changes its logic state on +ve(leading) edge of i/ps.


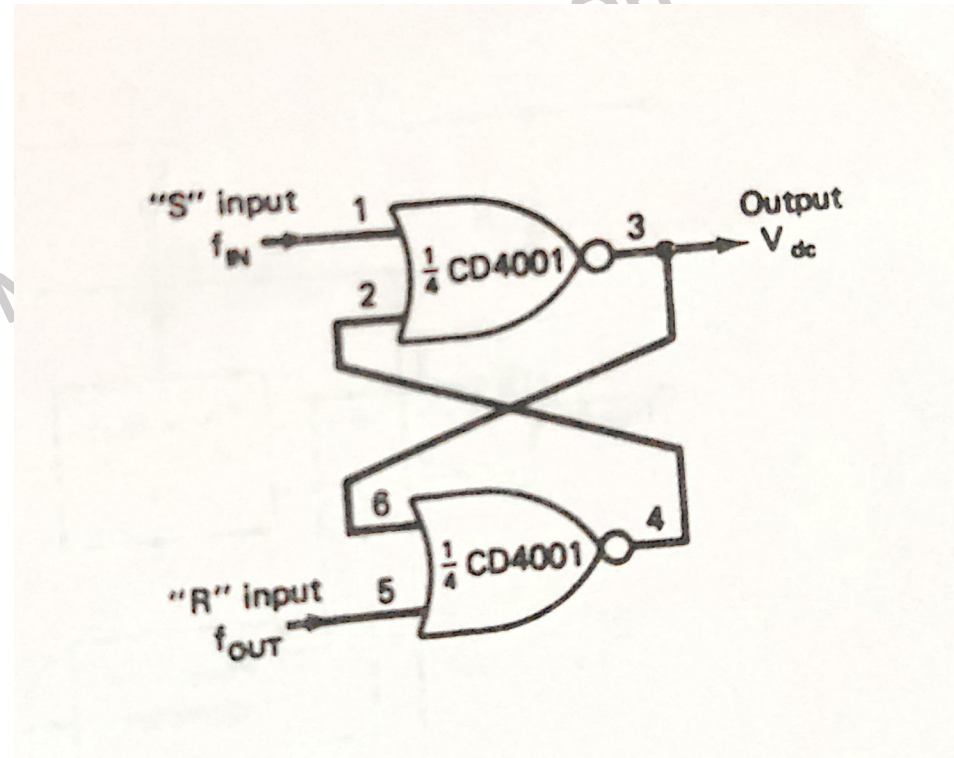
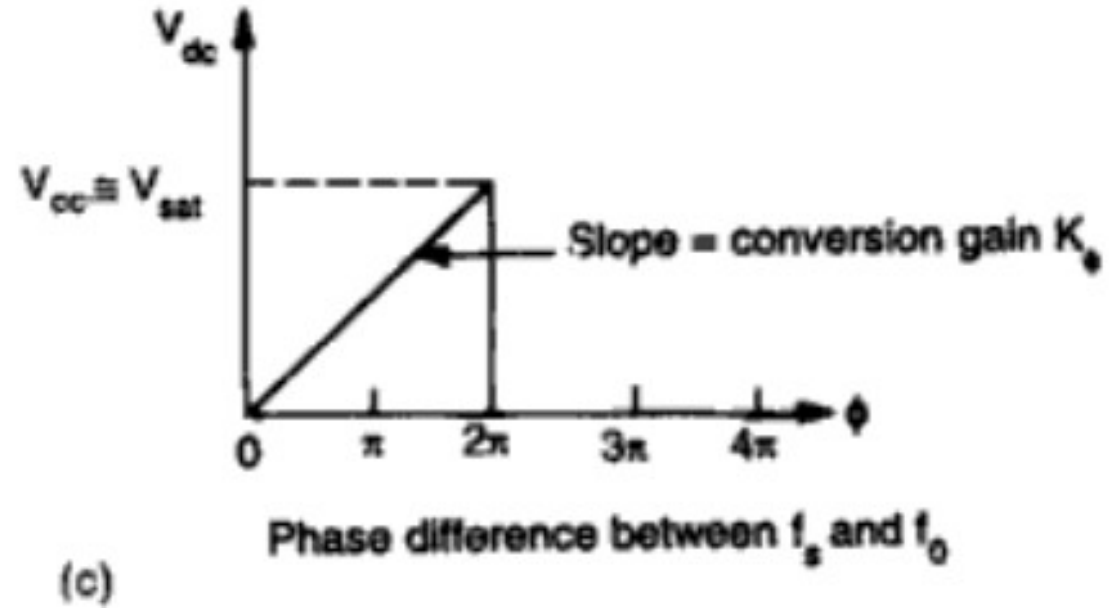


Fig : Edge triggered type of phase detector

a) NOR gate SR FF connection diagram

b) i/p & o/p w/f

 c) DC o/p V vs p.d. btw  $f_{IN}$  and  $f_{OUT}$




# LOW PASS FILTER


- o/p of P.D. is applied to **LPF** which removes high frequency noise and produce a DC level.
- Filter **controls the dynamic characteristics** of PLL ckt. These characteristics include capture and lock ranges, BW and transient response.
- If the **filter BW is reduced, response time increases.**
- But reducing BW of filter also **reduces capture range of PLL.**

- The charge on the filter capacitor gives a short time memory to the PLL.
- The loop filter used in PLL may be one of the 3 types shown in fig.

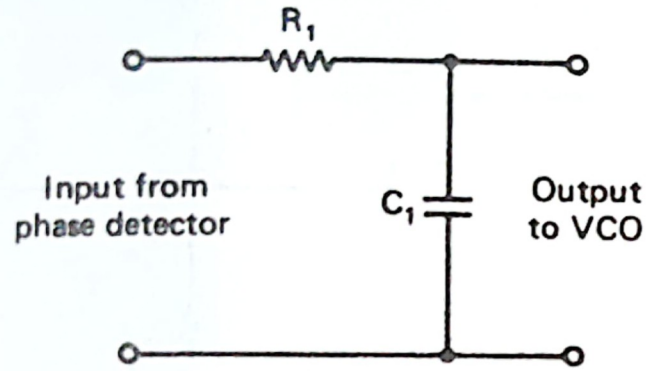
PREPARED BY RINJU RAVINDRAN, ADHOC ASST. PROFESSOR-ECE, GCEK



(a)

 

(b)

 

(c)

**FIGURE 9-29** Low-pass filters. (a) and (b) Passive filters. (c) Active filter.

- With the passive filters, an amplifier is generally used for gain.
- Active filter includes gain.

PREPARED BY RINJU RAVINDRAN, ADHOC ASST. PROFESSOR-ECE, GCEK

# VCO

- Generates o/p freq that is directly proportional to its i/p V.


**EXPLAIN VCO using block diagram and waveforms**

PREPARED BY RISHU RAVINDRAN, ADHOC ASST. PROFESSOR-ECE, GCEK


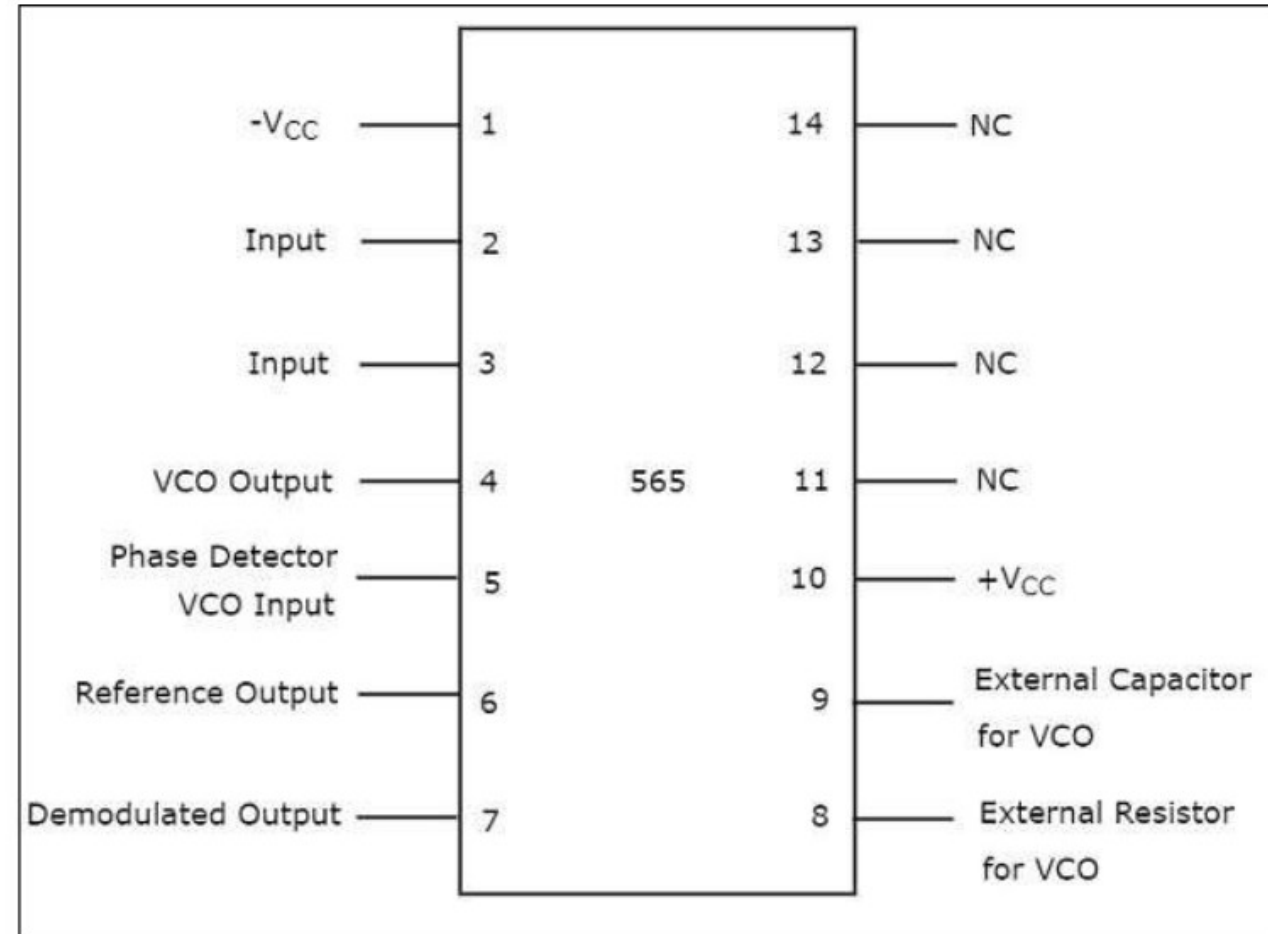
# IC PLL 565

- IC 565 is the most commonly used phase locked loop IC.
- It is a 14 pin Dual-In line Package (DIP).




- Out of 14 pins, only 10 pins (pin number 1 to 10) are utilized for the operation of PLL. So, the remaining 4 pins (pin number 11 to 14) are labelled with NC (No Connection).
- The **VCO** produces an output at pin number 4 of IC 565, when the pin numbers 2 and 3 are grounded.
- Mathematically, we can write the VCO output frequency,

**Hz**

- $R_T$  is the external resistor that is connected to the pin number 8
- $C_T$  is the external capacitor that is connected to the pin number 9
- Value btw **2 K & 20 K** is recommended for  $R_T$ .
- VCO free running freq is adjusted with  **$R_T$  &  $C_T$  to be at the centre of input freq range.**
- **Pin numbers 4 and 5** are to be shorted with an external wire so that the output of VCO can be applied as one of the inputs of phase detector.

- IC 565 has an **internal resistance of 3.6 Kohm**.
- A capacitor, C has to be connected between pin numbers 7 and 10 in order to make a **low pass filter** with that internal resistance.

# NE/SE565 PLL BLOCK DIAGRAM

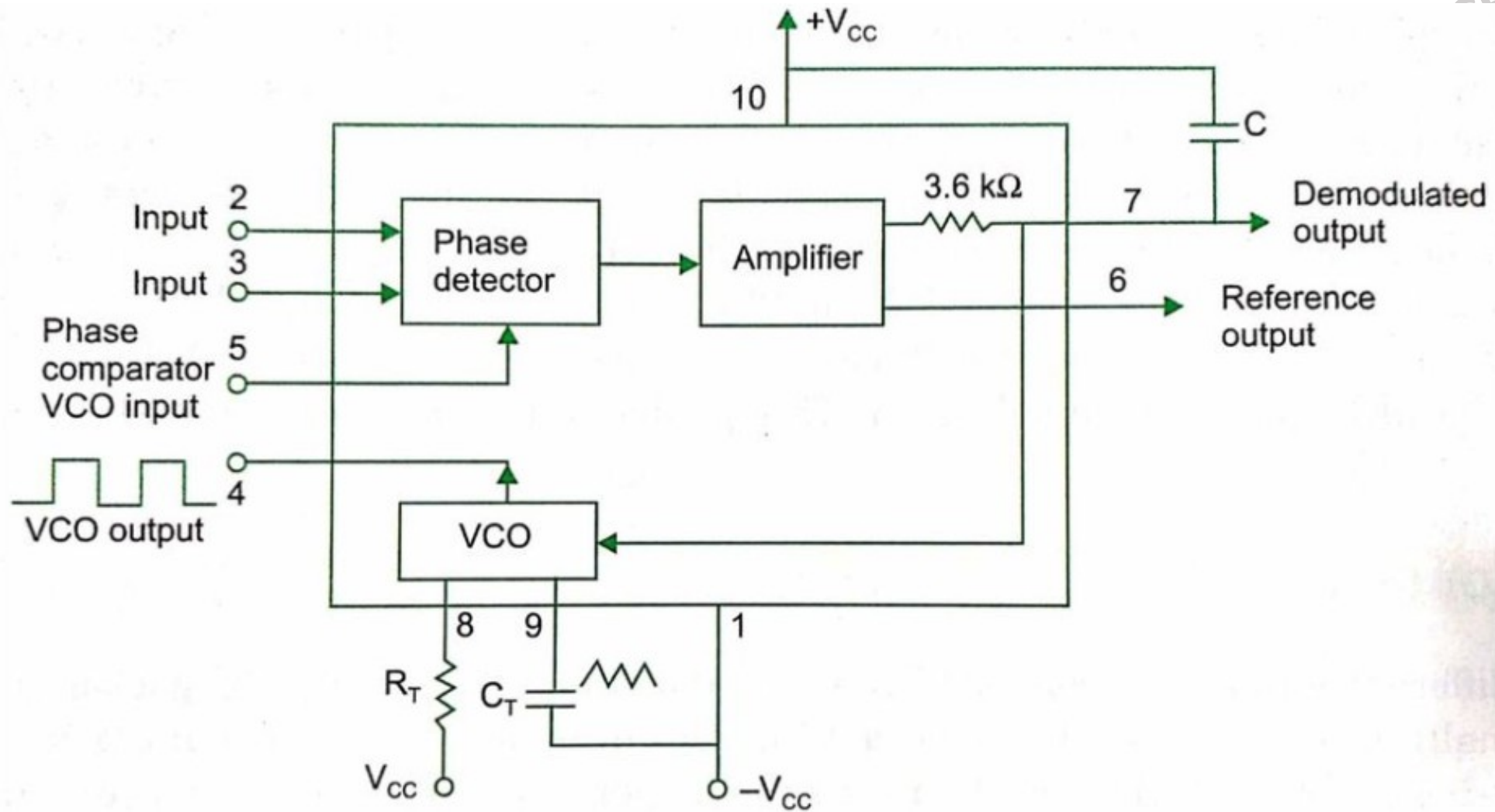

**Fig. 9.9** (b) NE/SE565 PLL block diagram

# Important electrical parameters of 565 PLL

Sr No.	CHARACTERISTIC	RANGE/VALUE
1	Operating frequency range	0.001Hz to 500KHz
2	Operating voltage range	$\pm 6$ to $\pm 12$
3	Input level required for tracking	10mV rms minimum to 3Vp-p maximum
4	Input impedance	10k $\Omega$ typically
5	Output sink current	1mA typically
6	Output source current	10mA typically
7	Drift in VCO center frequency $f_o$ with temperature	300 ppm/ $^{\circ}$ C typically
8	Drift in VCO center frequency $f_o$ with supply voltage	1.5% / V maximum
9	Triangular wave amplitude	Typically 2.4 V <sub>p-p</sub> at $\pm 6$ supply voltage
10	Triangular wave amplitude	Typically 5.4 V <sub>p-p</sub> at $\pm 6$ supply voltage
11	Bandwidth adjustment range	$< \pm 1$ to $\pm 60\%$

- For IC PLL 565,

$K_v =$  where  $V = +V_{cc} - (-V_{cc})$  and  $f_0$  is VCO free running freq

$$K_\phi = 1.4/\pi$$

$$A = 1.4$$

- Lock in range  $= K_v K_\phi A \pi$

=

- For IC PLL 565,  $R = 3.6 \text{ k}$

$$f_1 = 1/2\pi RC$$

- Capture range


PREPARED BY RINJU RAVINDRAN, ADHOC ASST. PROFESSOR-ECE, GCEK



# PLL APPLICATIONS


ASSOR-ECE, GCEK

## Frequency Synthesizer

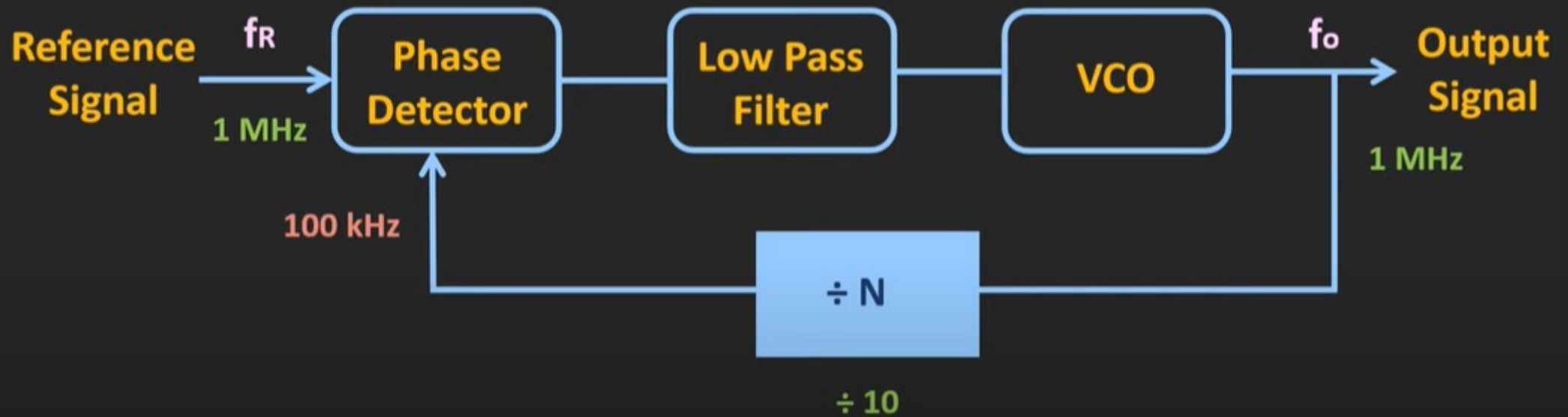

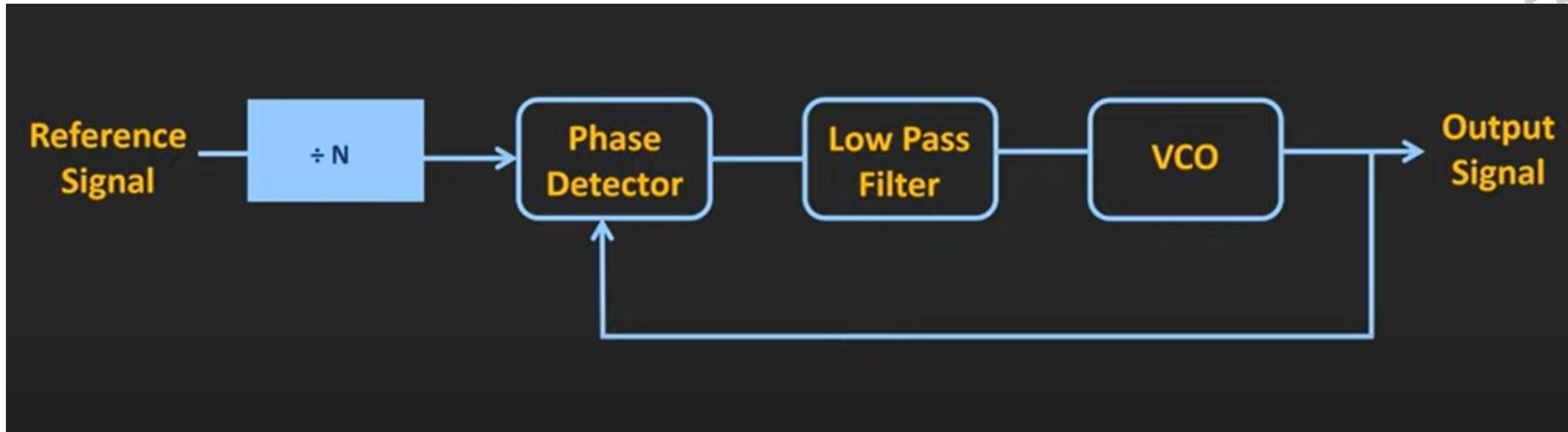
# 1. Freq synthesizer(freq multiplier & freq divider)

- Using Frequency divider (
- Lets say i/p freq = 1MHz & VCO freq = 1MHz
- When we introduce divide by 10 counter in the f/b, o/p = 100KHz.
- Now PLL controls VCO in such a way that o/p of divider  $n/w = 1\text{MHz}$
- That means VCO o/p should be = 10 MHz.
- That is o/p of PLL is 10 times the i/p freq. **(freq multiplier )**  $f_0 = Nf_R$



Here i/p freq is divided by a factor of N (freq divider)  $f_0 = f_R/N$

## 2. Frequency translation

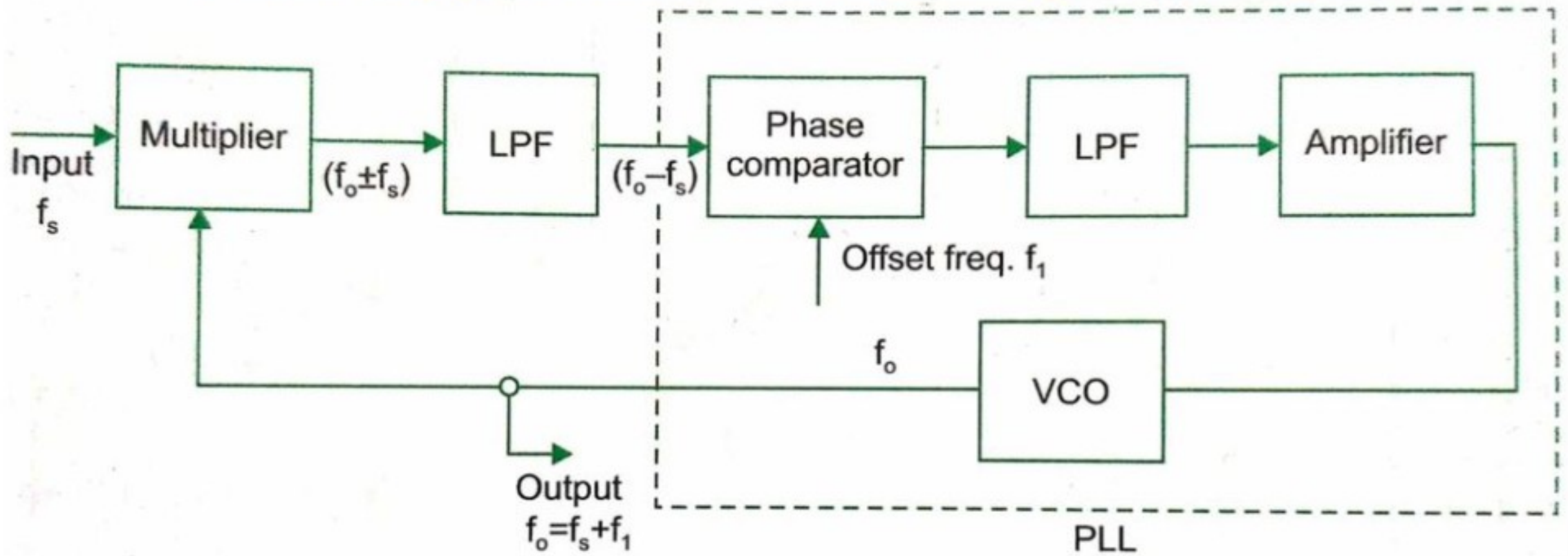


- Shifting the freq of an oscr by a small factor.
- Mixer (or multiplier) and a LPF is connected externally to PLL.
- s/g  $f_s$  which has to be shifted and o/p freq  $f_0$  of VCO are applied as i/ps to mixer.
- o/p of LPF ---  $(f_0 - f_s)$
- Translation / offset freq  $f_1$  ( $f_1 \ll f_s$ ) is applied to phase comparator.
- When PLL is in lock state,  $f_0 - f_s = f_1$

$$f_0 = f_s + f_1$$

- Thus it is possible to shift the incoming freq  $f$  by  $f$

### 3. AM Detection

ECE, GCEK

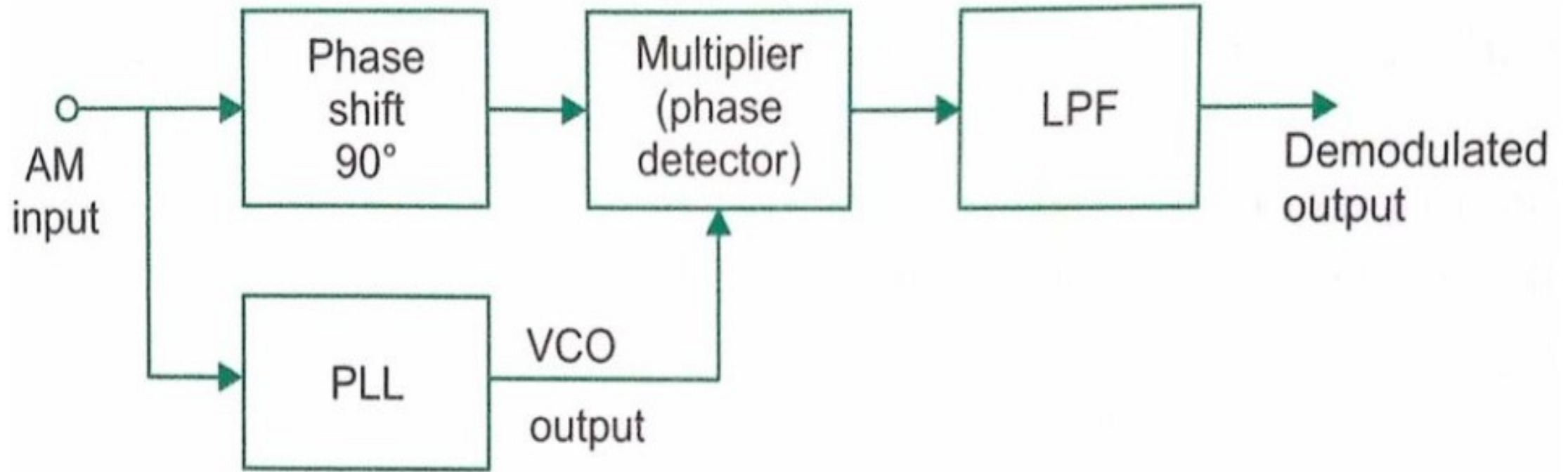

PREPARED

AM ---  $f_s + f_c$

VCO ---  $f_0 = f_c$

Demodulated o/p =  $f_s + f_c - f_c = f_s$

- PLL is locked to the carrier freq of the incoming AM s/g.
- o/p of VCO which has the same freq of carrier but unmodulated is fed to the multiplier.
- Since VCO o/p is always  $90^\circ$  out of phase with incoming AM s/g under locked condition, AM i/p is also shifted in phase by  $90^\circ$  before being fed to multiplier.
- So both s/gs to multiplier are in same phase
- o/p of multiplier contains both sum & diff terms
- Demodulated o/p is obtained after filtering high freq components by LPF.

- Since PLL responds only to carrier freqs which are very close to VCO o/p, a PLL AM detector exhibits a high degree of selectivity and noise immunity which is not possible with a conventional peak detector type AM modulators.



## 4. FM Demodulation

- If PLL is locked to an FM s/g, the VCO tracks the instantaneous freq of i/p s/g.
- Filtered error  $V$  which controls VCO and maintains lock with i/p s/g is demodulated FM o/p.
- VCO transfer chara determine the linearity of demodulated o/p.
- Since VCO used in IC PLL is highly linear, it is possible to realize highly linear FM demodulators.

## 5. FSK demodulators

- In digital commn, binary data is transmitted by means of a carrier freq which is shifted btw 2 preset freqs.
- This type of data txn is called freq shift keying technique.
- As the s/g appears at i/p, loop locks to i/p freq and tracks it btw 2 freqs with a corresponding dc shift at the o/p.
- Filter removes carrier component.