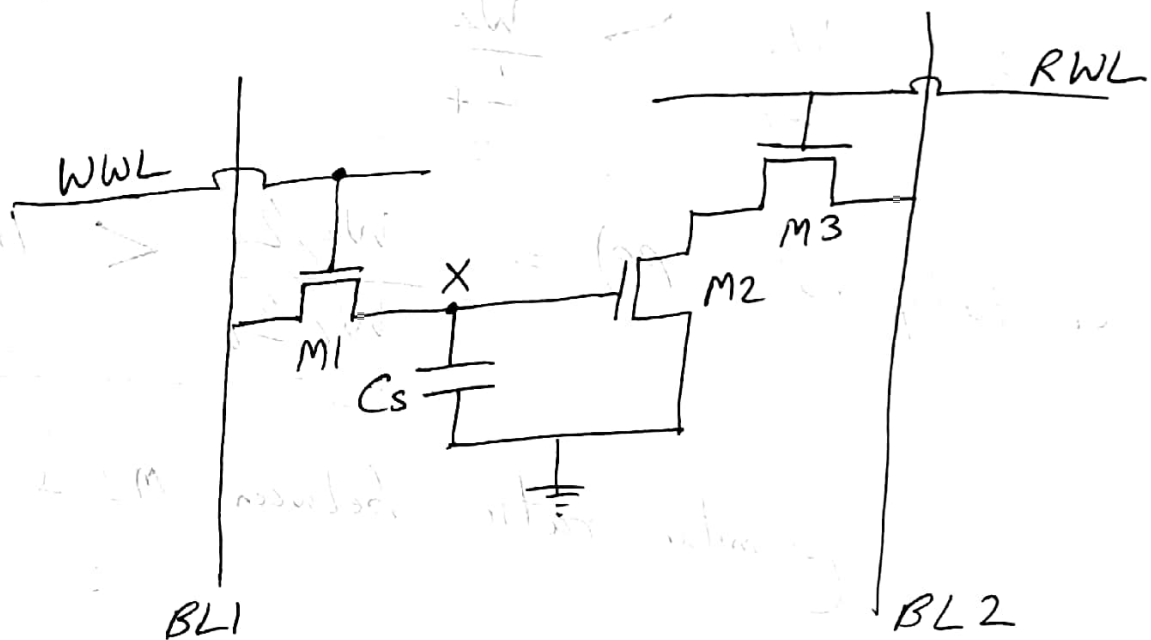


# DRAM (Dynamic RAM)

→ Data is stored in the form of charge stored in a capacitor. Since, this charge can decrease over time due to leakage, it is called dynamic RAM.

→ Periodic refreshing is required to maintain data inside DRAM.

## 3-Transistor DRAM cell



→ Logic 1  $\Rightarrow$  Cs is charged  
Logic 0  $\Rightarrow$  Cs is discharged.

WWL  $\rightarrow$  Write Word Line

RWL  $\rightarrow$  Read Word Line

$\rightarrow$  BL1 is used to write data into cell &  
BL2 is used to read data from cell.


### Write operation

$\rightarrow$  Assume that 0 is stored in cell. So voltage at  $X = 0$  V.

$\rightarrow$  We want to write 1 into the cell.

$\rightarrow$  BL1 is made high  $(V_{DD})$  & then WWL is enabled. ( $RWL = 0$ ).

 $\rightarrow$  M1 turns on &  $C_s$  charges towards  $V_{DD}$ .



$\rightarrow$  Max voltage that can be stored  $= V_{DD} - V_{Tn}$   
(Threshold of M1)

$\rightarrow$  At this time, even though gate voltage of M2 is high current will not flow because M3 is off & hence there is no connection.

→ Similarly, to write 0 to the cell, BL1 is made 0 & WWL is enabled, thus turning on M1. So C5 will discharge to 0.


### Read operation

→ Assume that a 1 is stored in cell.

→ BL2 is precharged to  $V_{DD}$  & RWL is ~~enable~~ made high.

→ M2 is on & M3 is also on.

 → BL2 ~~will~~ will discharge through M3 & M2 to 0.




→ BL2 voltage change is sensed. If BL2 decreases, it is recognized as logic 1.

→ Instead, if 0 was stored in cell, then M2 will be off. So BL2 cannot discharge. So it will be read as logic 0.

## Refresh operation

→ Data is read <sup>from the cell</sup> & it is again written back to the cell through write operation. This must take place at a certain frequency such that data do not get corrupted.


## One-Transistor DRAM cell

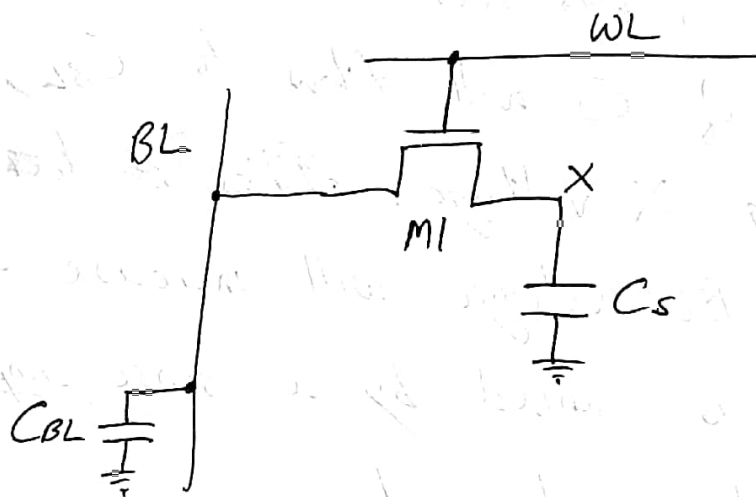
 
## → Write operation

→ Assume that 0 is stored in cell, so capacitor is not charged.

→ To write a 1 into the cell, BL is made high ( $V_{DD}$ ) & M1 is turned on using WL. So Cs charged through M1, thus storing 1.



← Write operation

→ Similarly, to store a 0, BL is made 0 & M1 is turned on.  
Read operation


→ BL is precharged to  $V_{DD}/2$  & WL is enabled.

→ Assume that 1 was stored in cell. Then some charge of  $C_s$  will flow to  $C_{BL}$ , thus reducing X voltage. ~~This decrease in X~~ So BL voltage will increase & this increase is sensed by a sense amplifier. It is recognized as logic 1.

Since there is a decrease in X voltage associated with read (destructive readout), a refresh operation should be done along with read.

→ ~~Instead~~



 

Read operation  
of  
logic 1

→ Instead, if logic 0 was stored in cell, the BL will decrease upon read & this will be sensed as logic 0.