

Roll. No.: S2.....

No. of pages: .....

Name: Melvin P. S.

**GOVT. COLLEGE OF ENGINEERING KANNUR**

**Department of Electronics and Communication Engineering**

Third Semester First Series Examination November- 2022 (2019 Scheme)

**Course code: ECT203**

**Course Name: LOGIC CIRCUIT DESIGN**

Max. Marks: 50

Duration: 90 Minutes

**PART A**

**Answer all questions. Each question Carries 3 marks**

1. Express  $(6820)_{10}$  in NBCD, XS3 and 2421 codes. (3 Marks)
2. Find x if  $(211)_x = (152)_8$ . (3 Marks)
3. Express the switching function  $f(A,B,C) = (A+B'+C)(A'+B'+C)(A+B'+C')$  in Canonical SOP and Canonical POS notations. (3 Marks)
4. State the principle of duality? Write the dual of the Boolean identity  $X(Y+Z) = XY + XZ$  (3 Marks)
5. Realize a two input X-NOR function using a 2:1 Mux. (3 Marks)

**PART B**

6. Design a 4bit binary to gray code converter and implement the circuit using EX-OR gates. (14 Mark)

**OR**

7. Design a 4 bit 84-2-1 to 8421 code converter and implement the circuit using 2 level AND-OR gates (14 Marks)
8. a) Simplify the Boolean function  $F(A,B,C,D,E) = \sum m(0,2,5,8,13,15,18,21,24,29,31)$  Using Karnaugh map. (7 Marks)
- b) Write the gate level Verilog code for the above simplified expression (7 Marks)

**OR**

9. a) Simplify the Boolean function  $F(A,B,C,D,E,F) = \sum m(6,9,13,18,19,25,27,29,41,45,57,61)$  Using Karnaugh map. (8 Marks)
- b) Write the gate level Verilog code for the above simplified expression. (6 Marks)
10. Show that 2:1 Mux is a universal multiplexer (7 Marks)

**OR**

11. Implement the Boolean function  $F(A,B,C,D) = \sum m(1,3, 4,11, 12,13,14,15)$  using 4:1 Mux using A and B as select lines. (7 Marks)