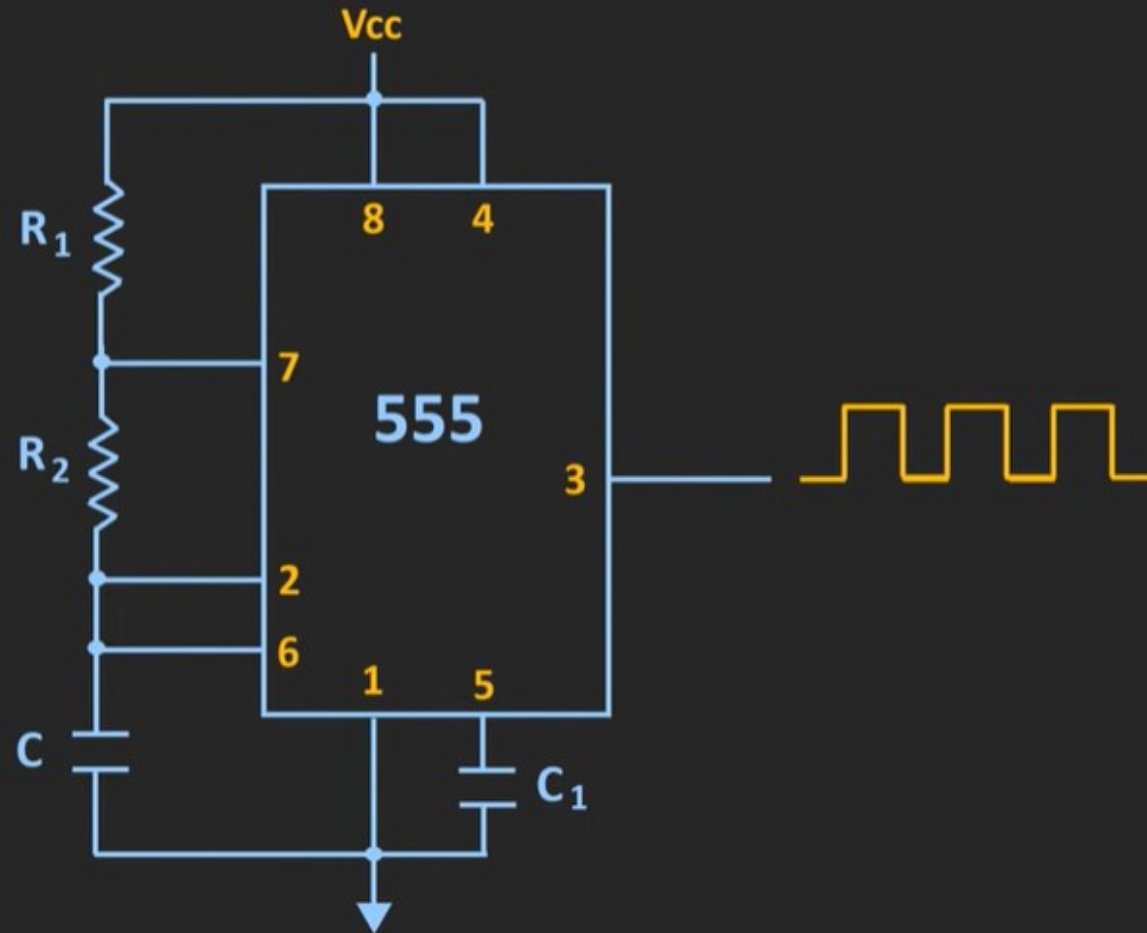


ASTABLE MULTIVIBRATOR USING 555 TIMER


PREPARED BY RINJU RAVINDRAN, ID#OC ASST. PROFESSOR-ECE, GCEK

555 Timer as Astable Multivibrator

- 1 - Ground
- 2 - Trigger
- 3 - Output
- 4 - Reset
- 5 - Control
- 6 - Threshold
- 7 - Discharge
- 8 - Vcc




555 Timer as Astable Multivibrator

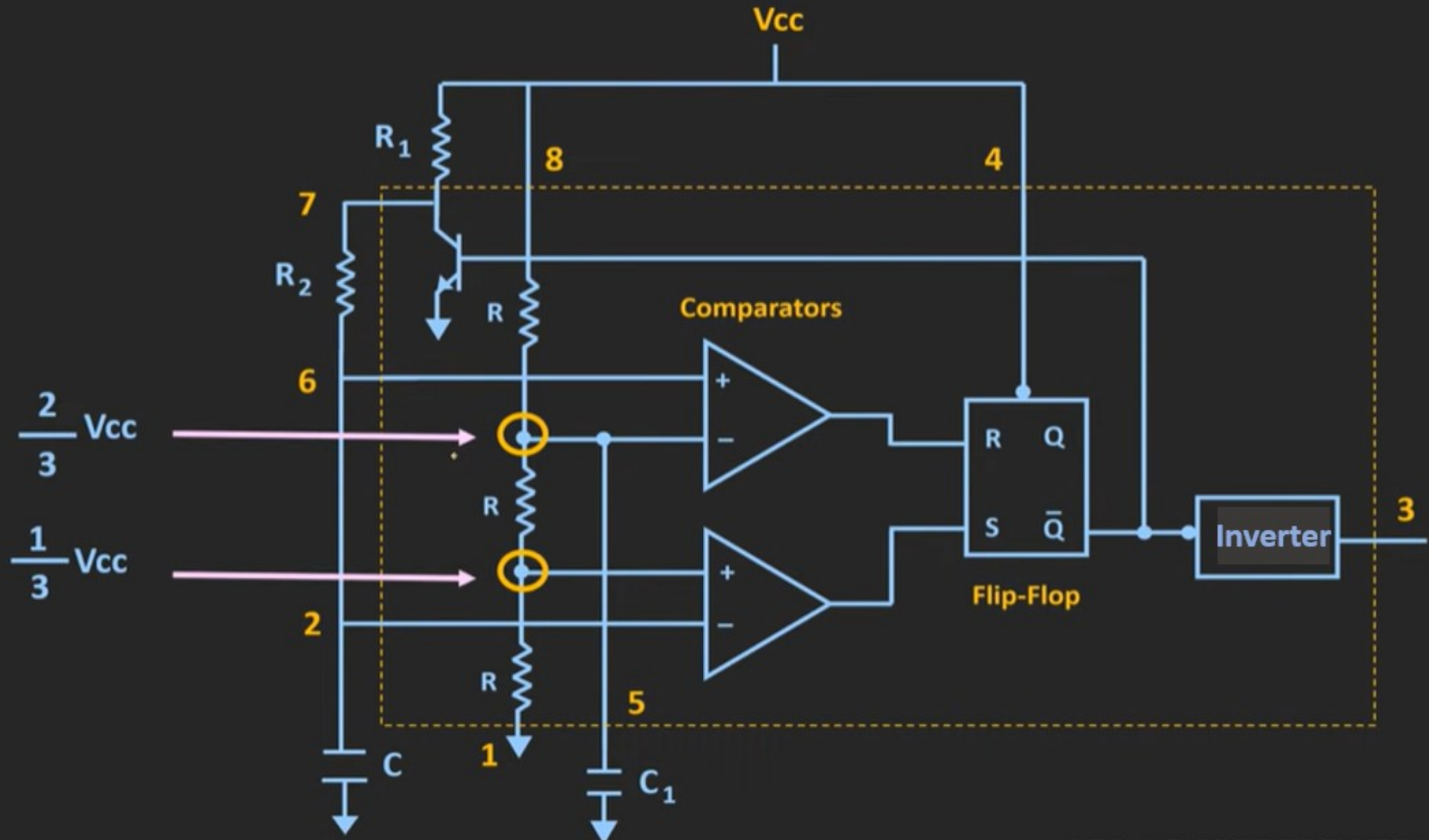


Case 1: $V_2=V_6=0$

- Whenever the ckt is jz turned on, cap C will be fully uncharged.
- ie V at pin 2 & 6 will be =0.
- so upper comparator(UC) o/p = 0
- Lower comparator(LC) o/p = 1
- S=1 and R=0 -----o/p Q=1-----o/p of 555 timer = logic HIGH (1)
- When Q=1, so transistor Q1 will be in OFF condition.
So cap C starts charging thru R1 and R2.

Case 1: $V_2 = V_6 = 0$

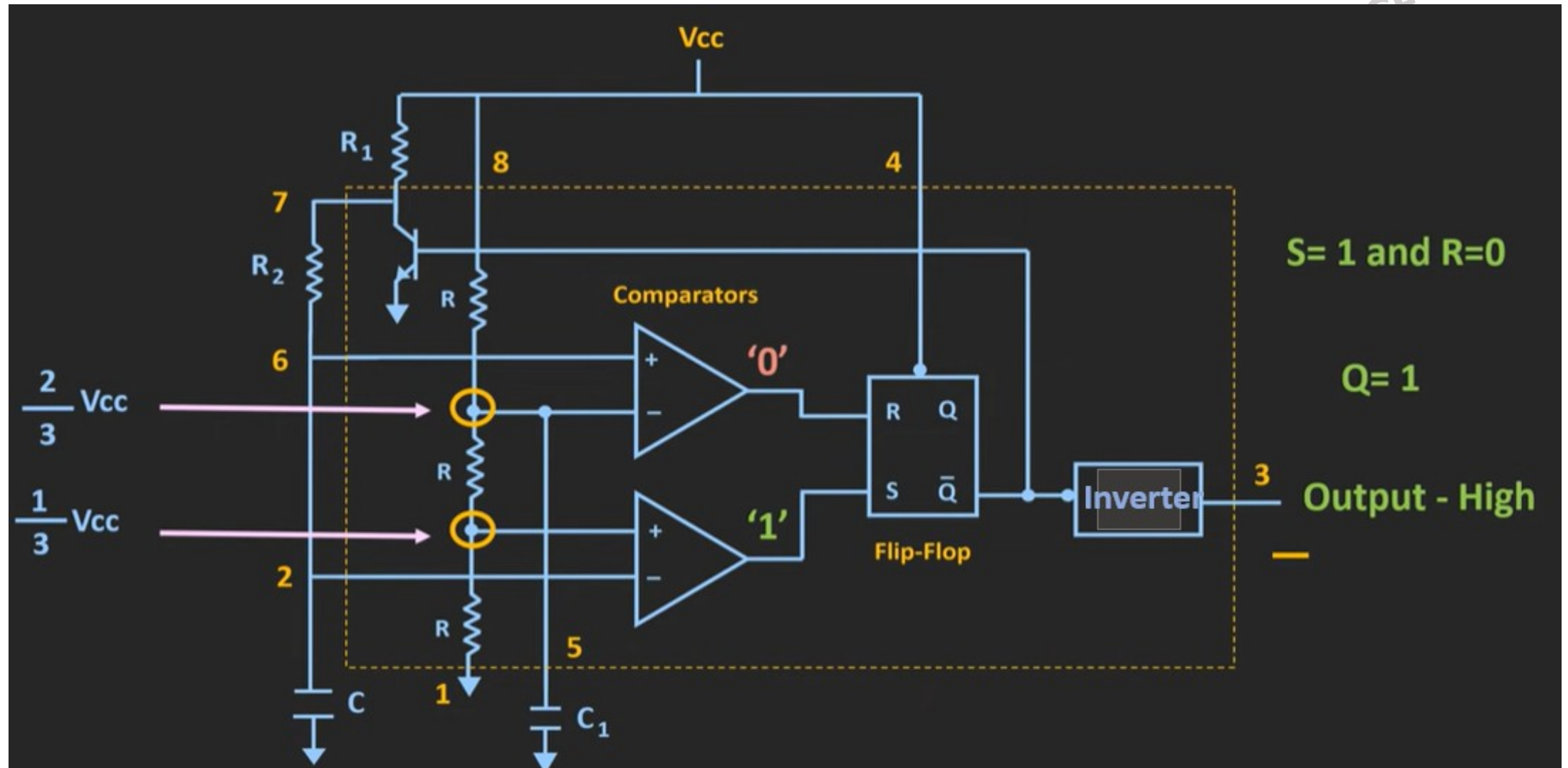

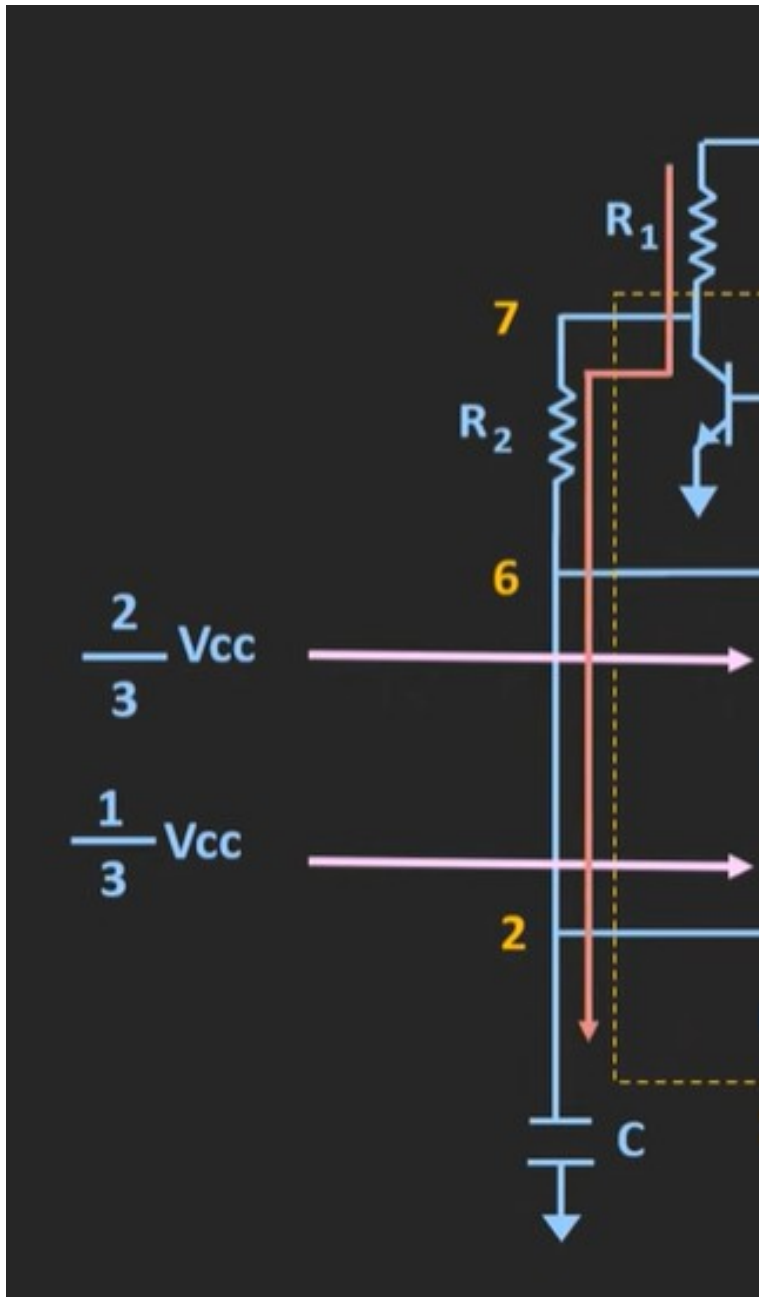

Gradually V at pin 2 & 6 will start increasing.


Case 2: $\frac{1}{3} V_{CC} < V_2 = V_6 < \frac{2}{3} V_{CC}$

Whenever V at pin 2 $> \frac{1}{3} V_{CC}$, o/p of LC = 0.


Let V at pin 6 $< \frac{2}{3} V_{CC}$, then o/p of UC = 0.

$S=0$ and $R=0$ ---- o/p $Q = 1$ (previous state). Timer o/p = High.

Case 2: $\frac{1}{3} V_{cc} < V_2 = V_6 < \frac{2}{3} V_{cc}$

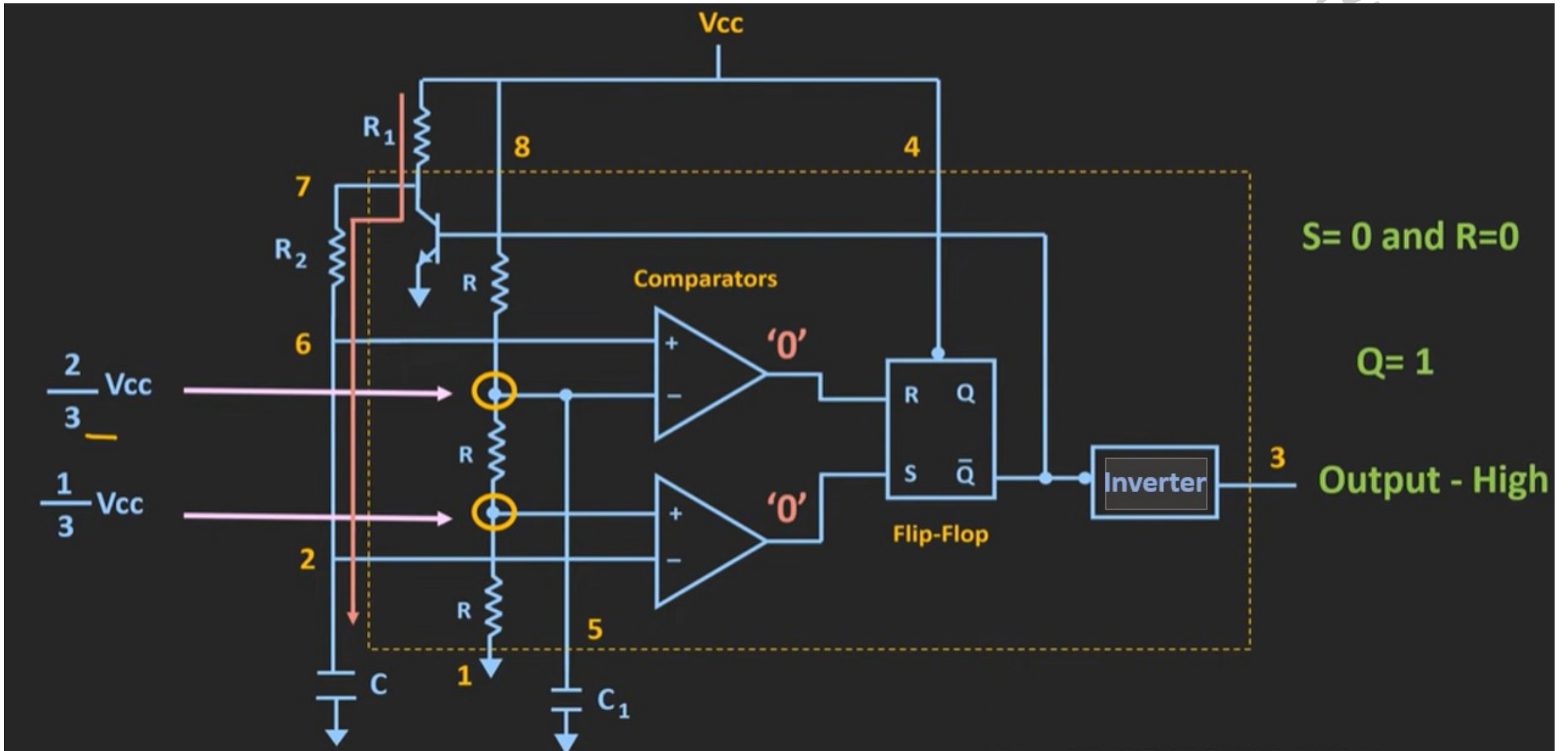


Case 3: $V_c > \frac{2}{3} V_{cc}$

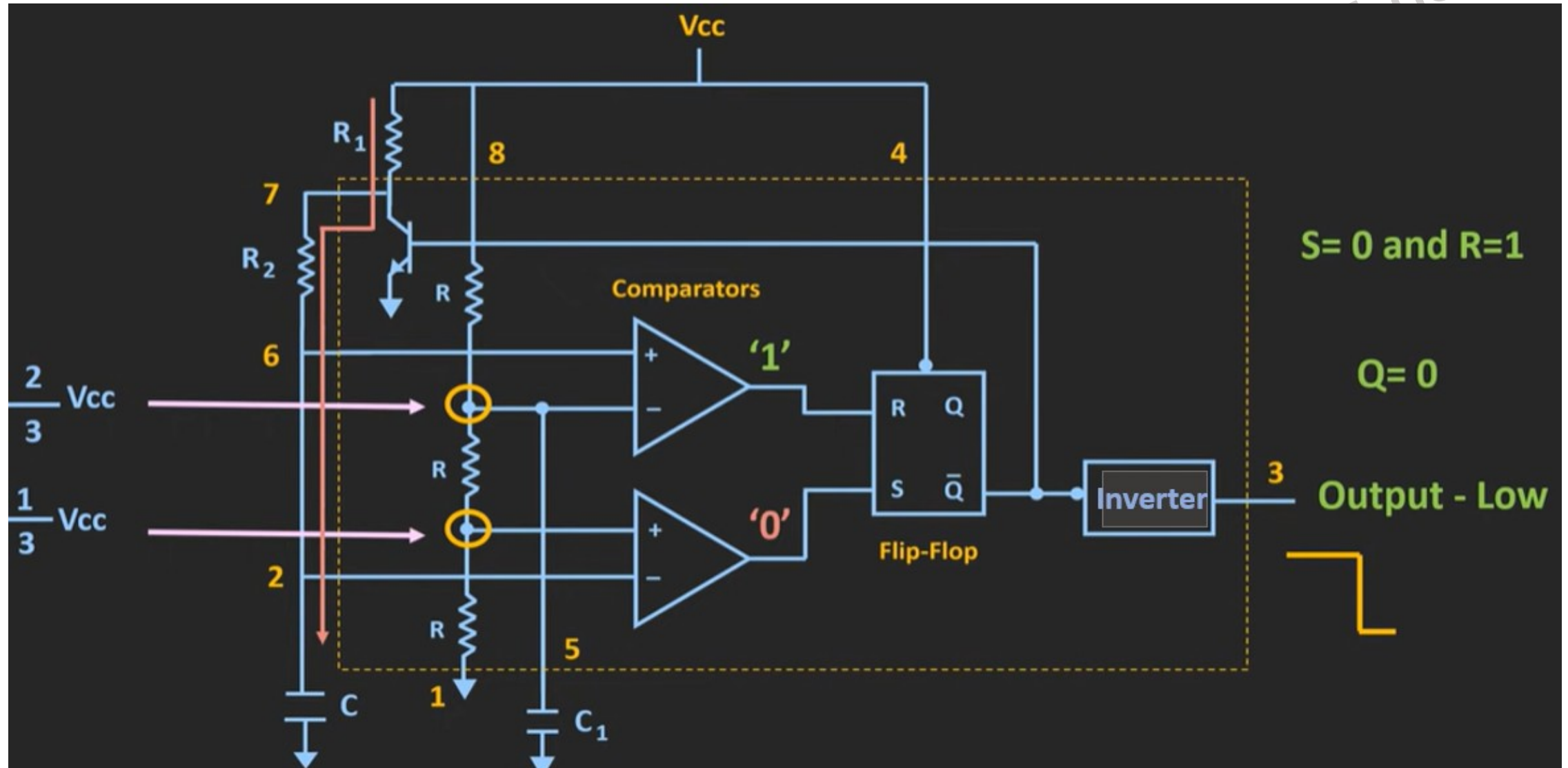

- When o/p $Q=0$, so transistor $Q1$ will be in ON condition. So cap C starts discharging thru $Q1$.
- V_c starts decreasing.

Case 4:

- As soon as V goes $jz < \frac{2}{3} V_{cc}$, then o/p of UC = 0.
- o/p of LC = 0
- $S=0, R=0$ --- $Q=0$ (previous)
- o/p of timer = 0
- $Q1$ still ON.

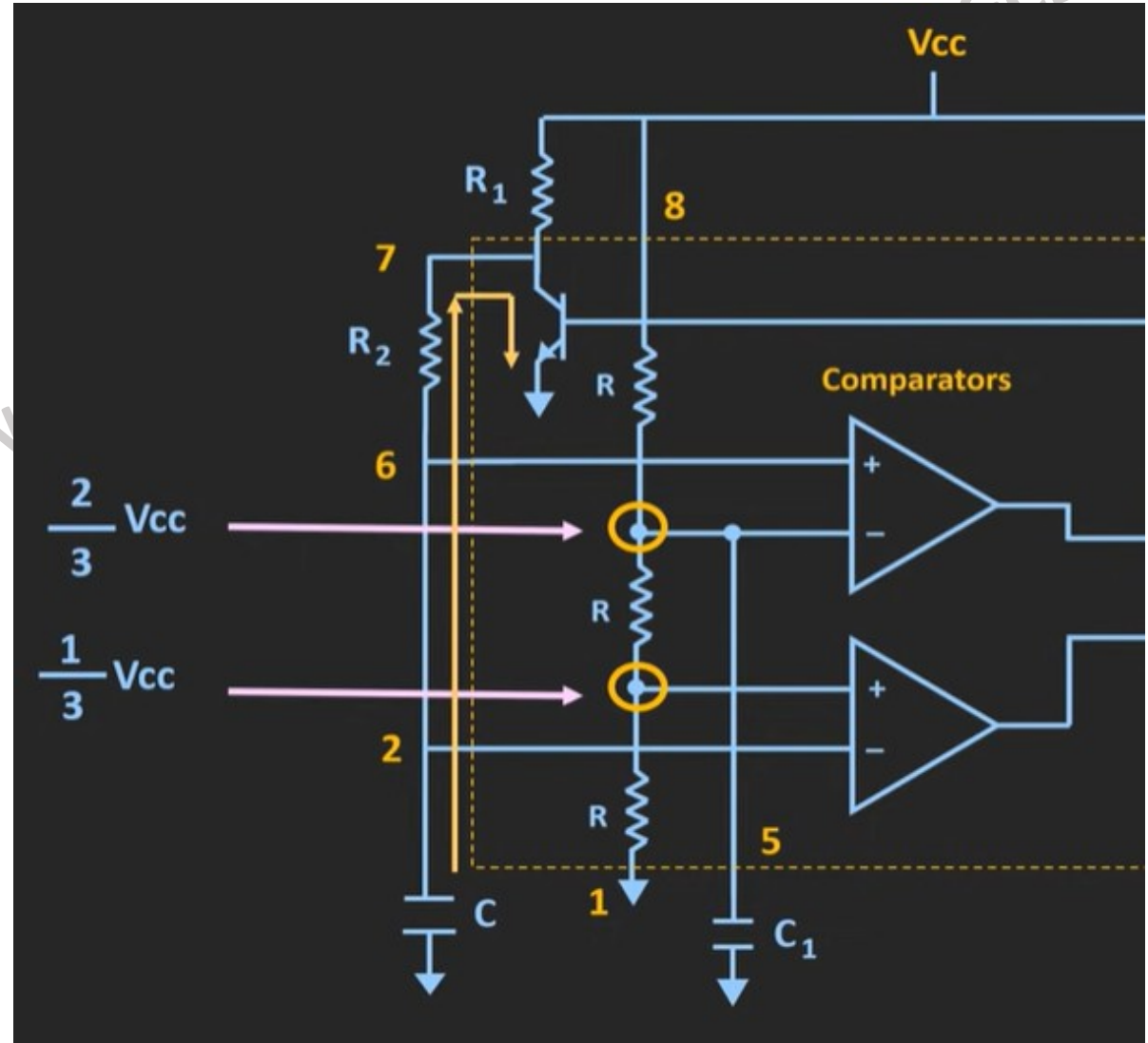

Case 5: when V_c goes $jz < 1/3 V_{cc}$

- o/p of LC = 1
- o/p of UC = 0
- S=1, R=0 ---- Q=1 .
- o/p of timer = logic High.
- When o/p Q=1, so transistor Q1 will be in OFF condition. So cap C starts charging thru R1 & R2.


S= 1 and R=0

Q= 1

Output - High



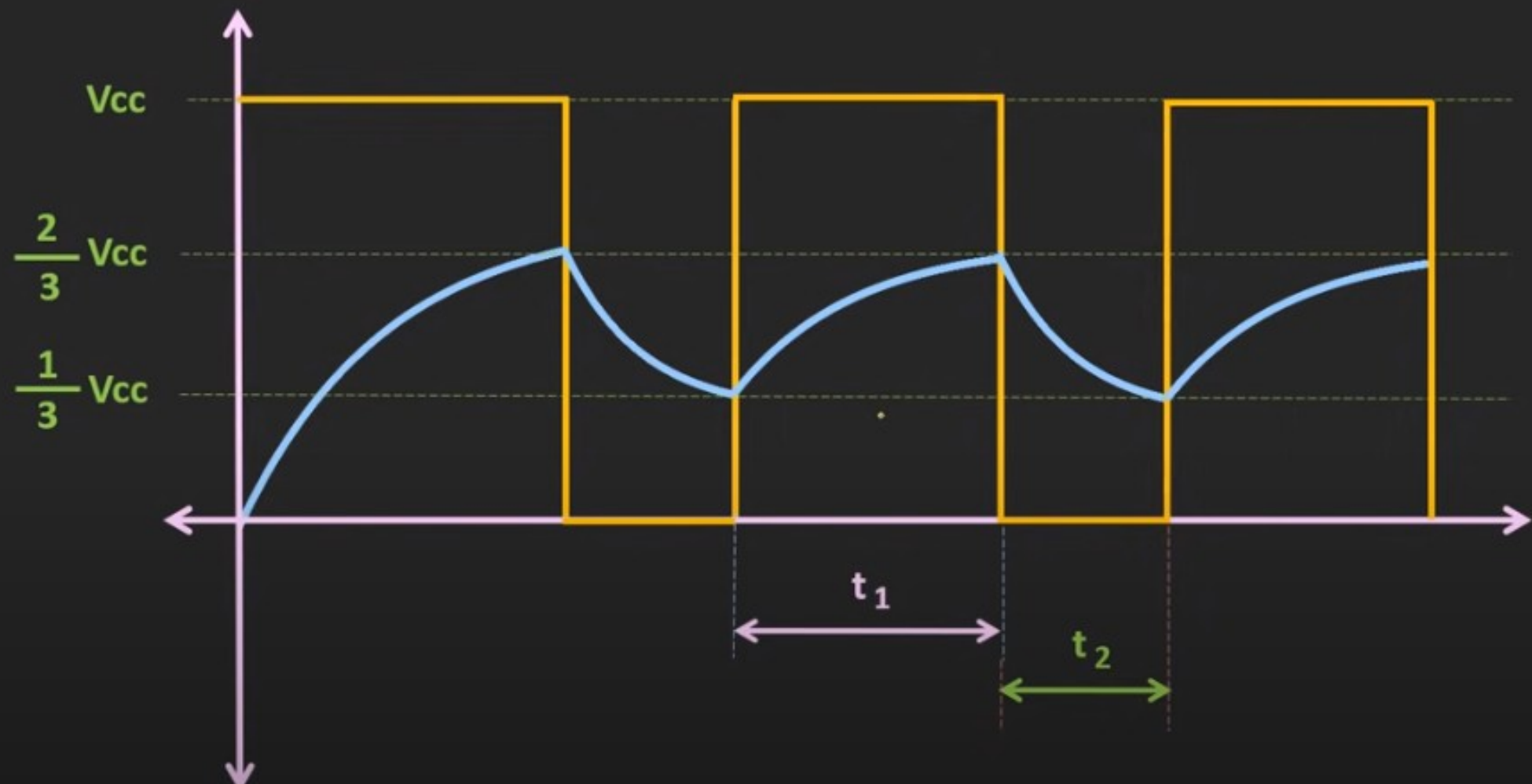- In this way, cap is charging btw $1/3 V_{cc}$ and $2/3 V_{cc}$.
- Bcoz of this charging & discharging of cap, we will see a transition in the o/p V.
- During charging process, whenever $V_c > 2/3 V_{cc}$, there is a transition in the o/p from logic high to logic low.
- During discharging process, whenever $V_c < 1/3 V_{cc}$, there is a transition in the o/p from logic low to logic high.



- Time t_1 – time for which o/p of timer remains HIGH
- Time t_2 – time for which o/p of timer remains LOW

$$t_1 > t_2$$

- Time t_1 - time taken by cap to charge from $1/3 V_{cc}$ to $2/3 V_{cc}$
- Time t_2 - time taken by cap to discharge from $2/3 V_{cc}$ to $1/3 V_{cc}$

$$t_1 = 0.693 (R1 + R2) C$$

$$t_2 = 0.693 R2 C$$

$$T = t_1 + t_2 = 0.693 (R1 + 2R2) C$$

$$t_1 > t_2$$

- Charging is thru R1 and R2
- Discharging thru R2 only.
- **Duty cycle is always > 50%**

- For 50 % duty cycle (symmetrical square wave), R1 should be = 0. But in this case, pin 7 is directly connected to Vcc and extra current will flow thru Q1 when it is ON. This may damage Q1 and hence the timer.

$$t_1 = 0.693 (R1 + R2) C$$

$$t_2 = 0.693 R2 C$$


$$T = t_1 + t_2 = 0.693 (R1 + 2R2) C$$

$$\text{Duty Cycle} = \frac{t_1}{T}$$

$$\text{Duty Cycle} = \frac{R1 + R2}{R1 + 2R2}$$

Astable Multivibrator (50 % Duty Cycle)

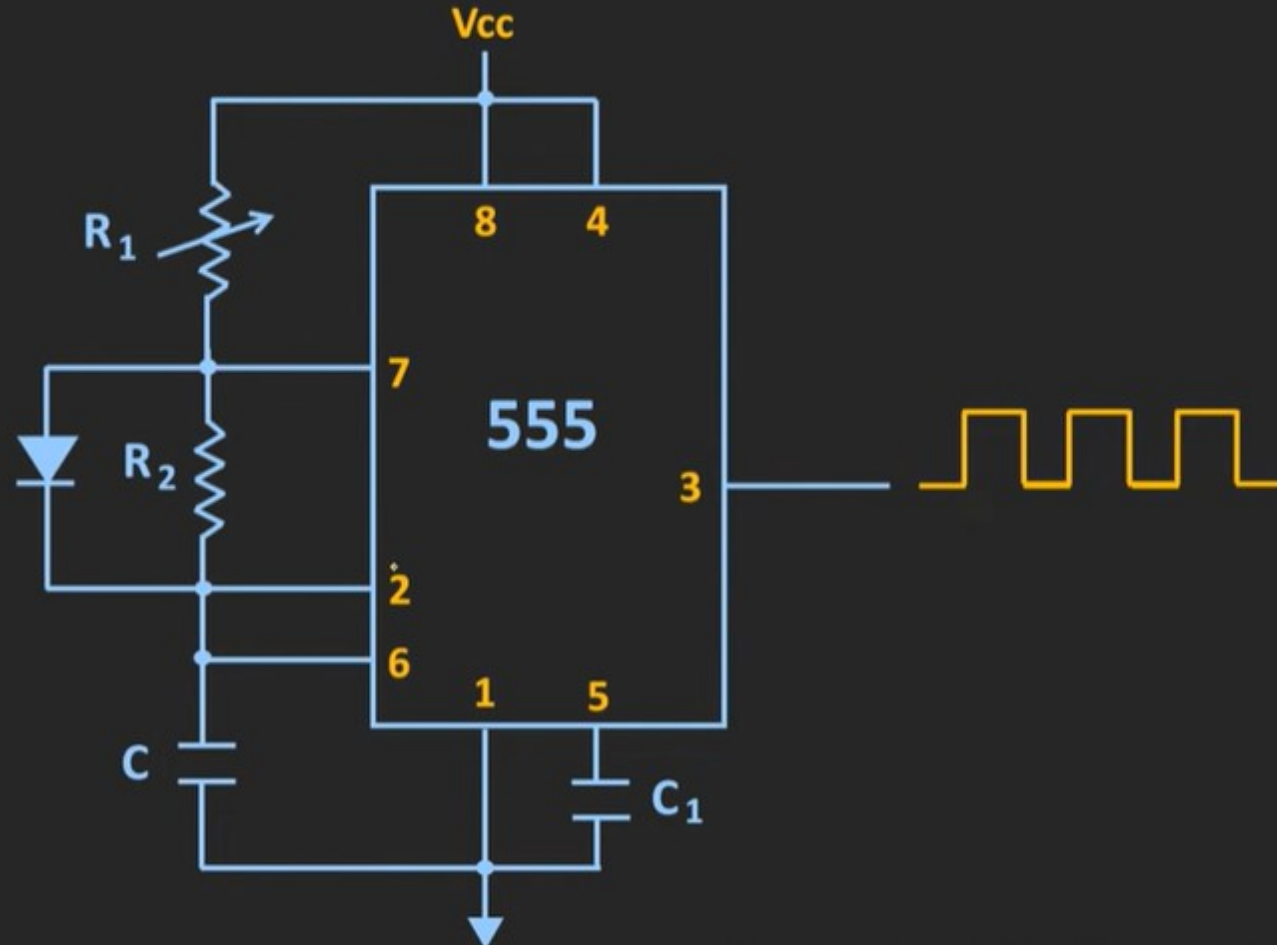- 1 - Ground
- 2 - Trigger
- 3 - Output
- 4 - Reset
- 5 - Control
- 6 - Threshold
- 7 - Discharge
- 8 - Vcc



- During the charging of this capr, diode will be ON.
- Fwd res of diode $R_D < R_2$. so C will charge thru R1 and D.

$$t_1 = 0.693(R_1 + R_D)C$$

- During the discharging of this capr, diode will be OFF.
- C will discharge thru R_2 .

$$t_2 = 0.693R_2C$$

- If we adjz R1 value such that $(R_1 + R_D) = R_2$, then duty cycle = 50%

- Or if we assume diode is ideal, $R_D = 0$.

$$t_1 = 0.693R_1C$$

$$t_2 = 0.693R_2C$$

- Duty cycle = $R_1 / (R_1 + R_2)$
- If we take $R_1 = R_2$, then duty cycle = 50%
- If we take $R_1 > R_2$, then duty cycle > 50%
- If we take $R_1 < R_2$, then duty cycle < 50%

Design

$$V_c(t) = V_F + (V_I - V_F)$$


To find t_1

$$V_I = \frac{1}{3} V_{cc}$$

$$V_F = V_{cc}$$

$$V_c(t) = \frac{2}{3} V_{cc}$$

$$R' = R_1 + R_2$$

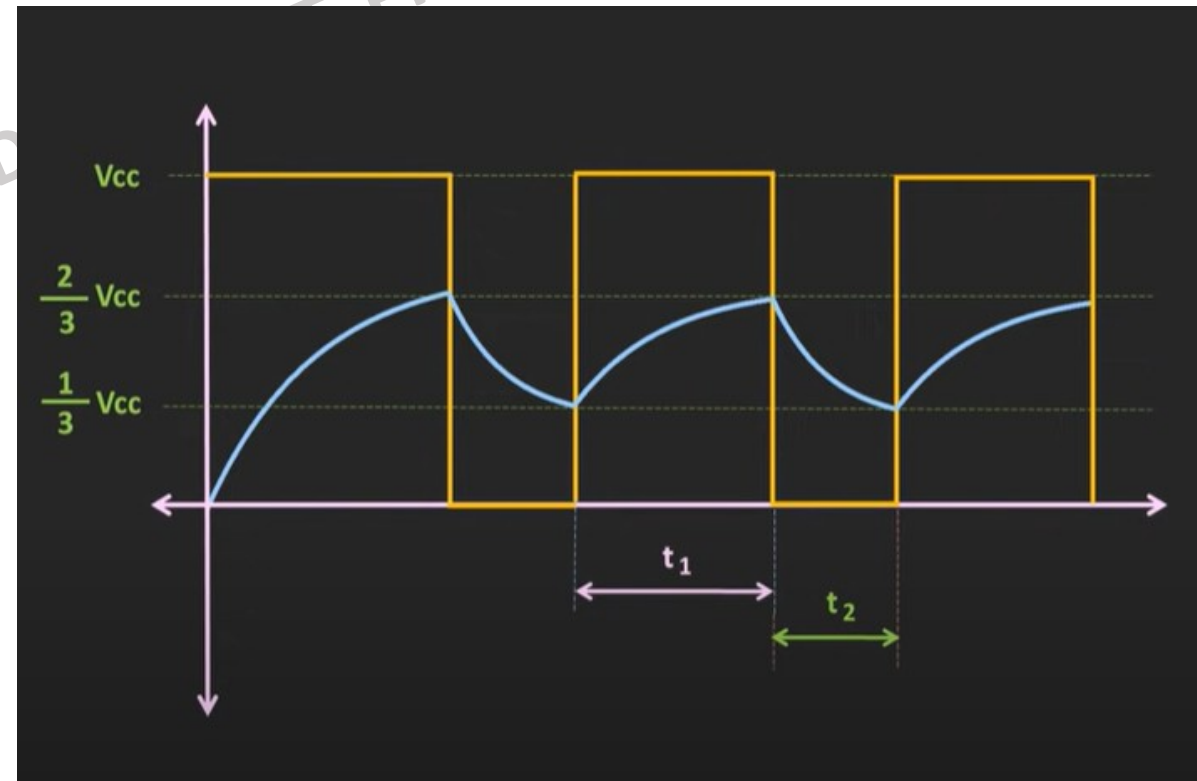

$$t_1 = 0.693 (R_1 + R_2) C$$

To find t_2

$$V_I = 2/3 V_{cc}$$

$$V_F = 0$$

$$V_c(t) = 1/3 V_{cc}$$

$$R' = R_2$$

$$t_2 = 0.693 R_2 C$$

PREPARED BY RINJU RAVINDRAN, ADHOC ASST. PROFESSOR-ECE, GCEK

- Total time $T = t_1 + t_2$

$$T = 0.693 (R_1 + 2R_2) C$$

- Frequency $f =$

- Duty cycle = = =

$$\text{Duty cycle} =$$

PREPARED BY KUNJU RAVINDRAN, ADHOC ASST. PROFESSOR-ECE, GCEK