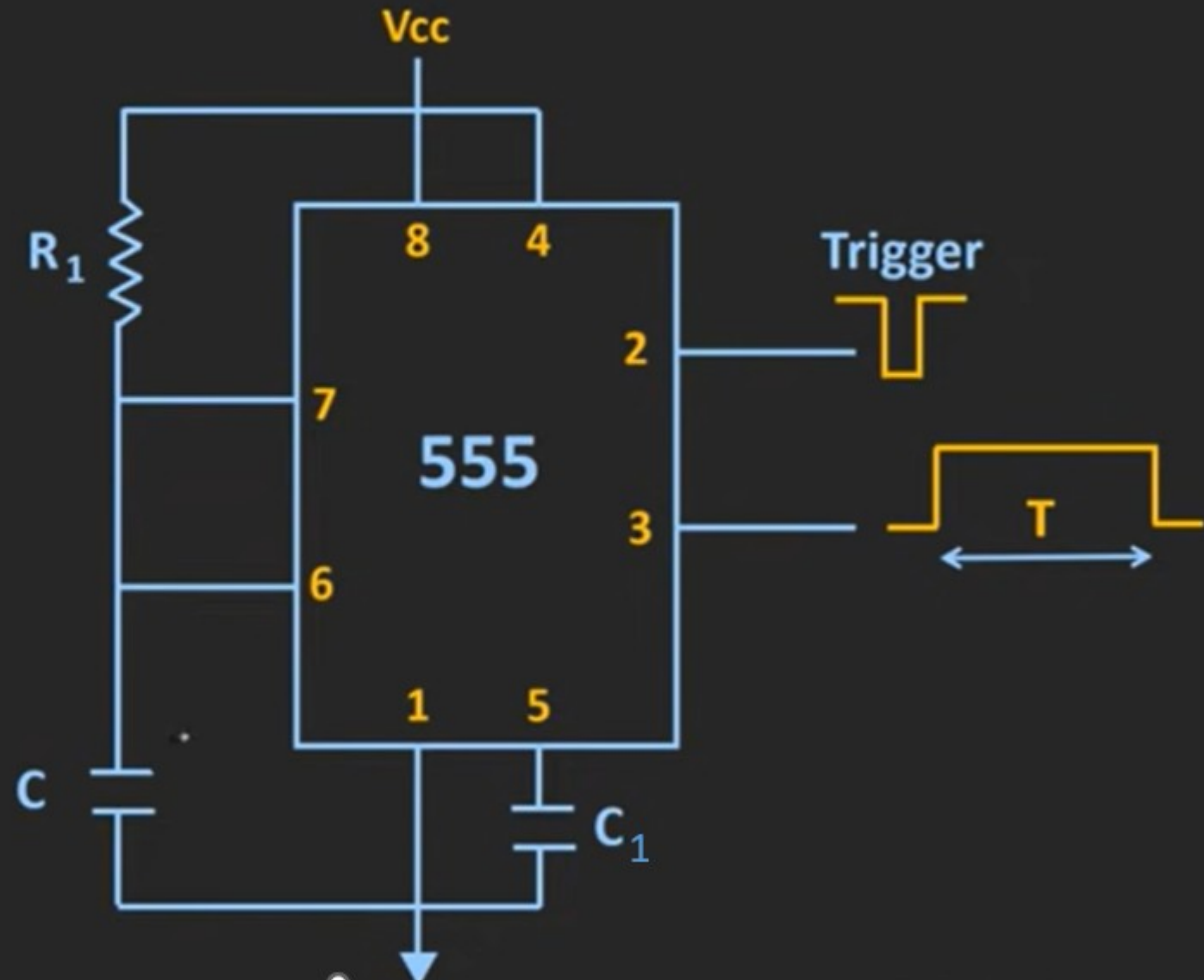


MONOSTABLE MULTIVIBRATOR USING 555 TIMER


PREPARED BY RINJU RAVINDRAN, ID NO: 19EE001, ASST. PROFESSOR-ECE, GCEK

555 Timer as Monostable Multivibrator

- 1 - Ground
- 2 - Trigger
- 3 - Output
- 4 - Reset
- 5 - Control
- 6 - Threshold
- 7 - Discharge
- 8 - V_{cc}



555 Timer as Monostable Multivibrator

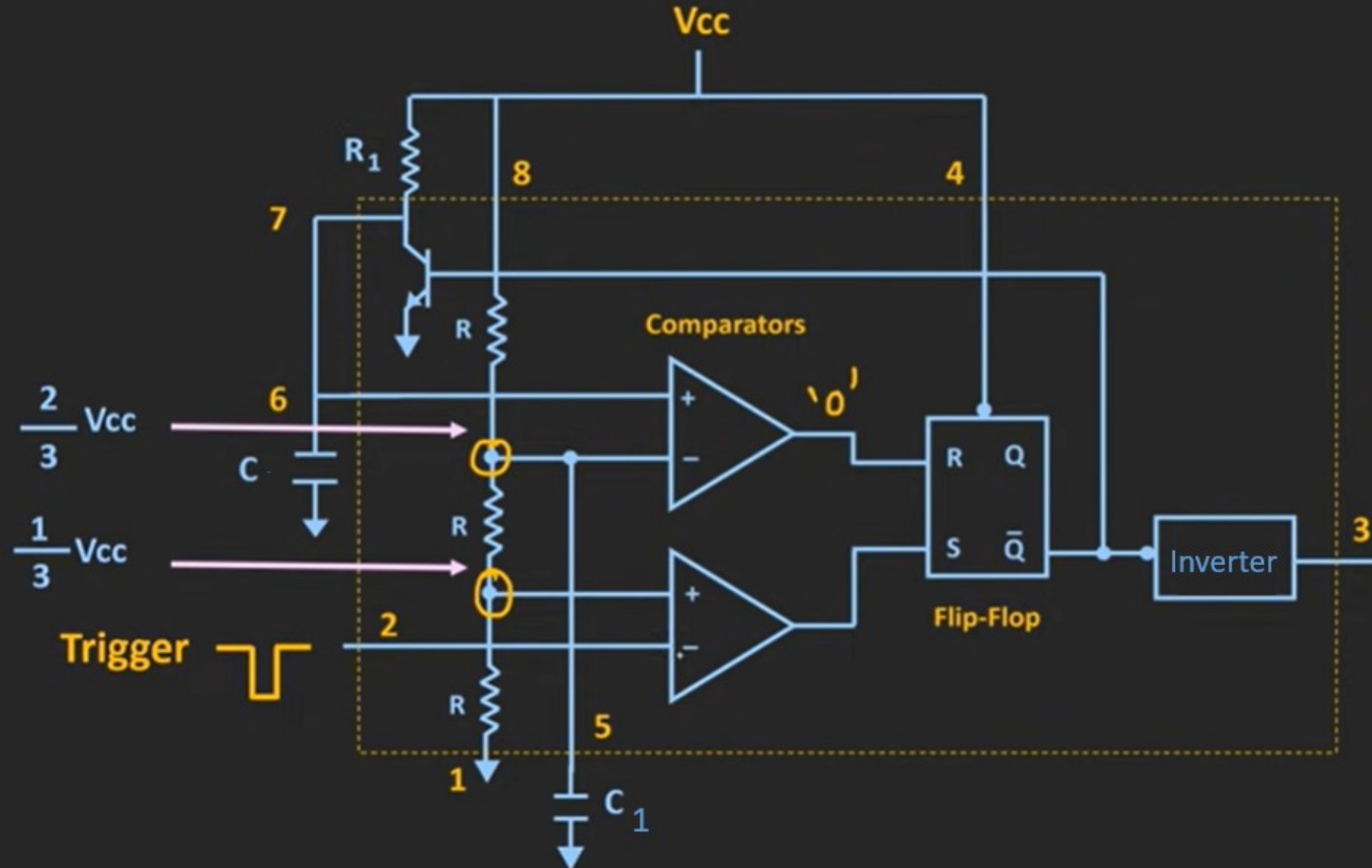

- Initially let's assume timer o/p = 0 (stable state)
- So
- Q1 will become ON
- So $V_c = 0$. V at pin 6 = 0.
- So o/p of UC = 0
- When no trigger is given, trigger pin is connected to V_{cc} .
- So o/p of LC = 0
- $S=R=0$ ----- O/p of FF = previous state = 0 (stable state)
- Timer o/p = 0

When trigger is applied

- Trigger s/g is applied such that o/p of pin 2 goes below $\frac{1}{3} V_{cc}$.
- Hence o/p of LC = 1
- o/p of UC is still at 0
- $S=1, R=0$ ---- $Q=1$. Timer o/p goes HIGH(**unstable state**)
- Q1 is OFF.
- C will charge thru R1 towards V_{cc} .
- **So once triggering happens, C starts charging towards**

- After triggering action, V at pin 2 is again V_{cc} .
- So now again o/p of LC becomes 0
- During charging, whenever V at pin 6 $> \frac{2}{3} V_{cc}$, o/p of UC = 1
- $S=0, R=1$ ----- $Q=0$. Timer o/p = 0 (stable)
- Q1 will become ON
- So C will start discharging thru Q1.
- So again o/p of both UC & LC = 0. so timer o/p = previous state = 0 (stable state)

$$T = 1.1 R_1 C$$



- When trigger is applied, a pulse is obtained for a short duration.
- Duration of pulse depends upon charging of the capacitor.

$$T = 1.1 R_1 C$$

- In this way, by changing R_1 and C , we can design a MMV and we can change the timing of the pulse.

Applications of MMV

1. For generating timing delays.

(By changing R_1 and C , we can design a MMV and we can change the timing of the pulse.)


2. For frequency division.

(If we are applying a periodic trigger s/g at pin 2)

Time duration of o/p pulse T shud be slightly more than that of triggering s/g t . ($T > t$).

In that case o/p s/g freq will be half than the trigger s/g freq.

Frequency Division

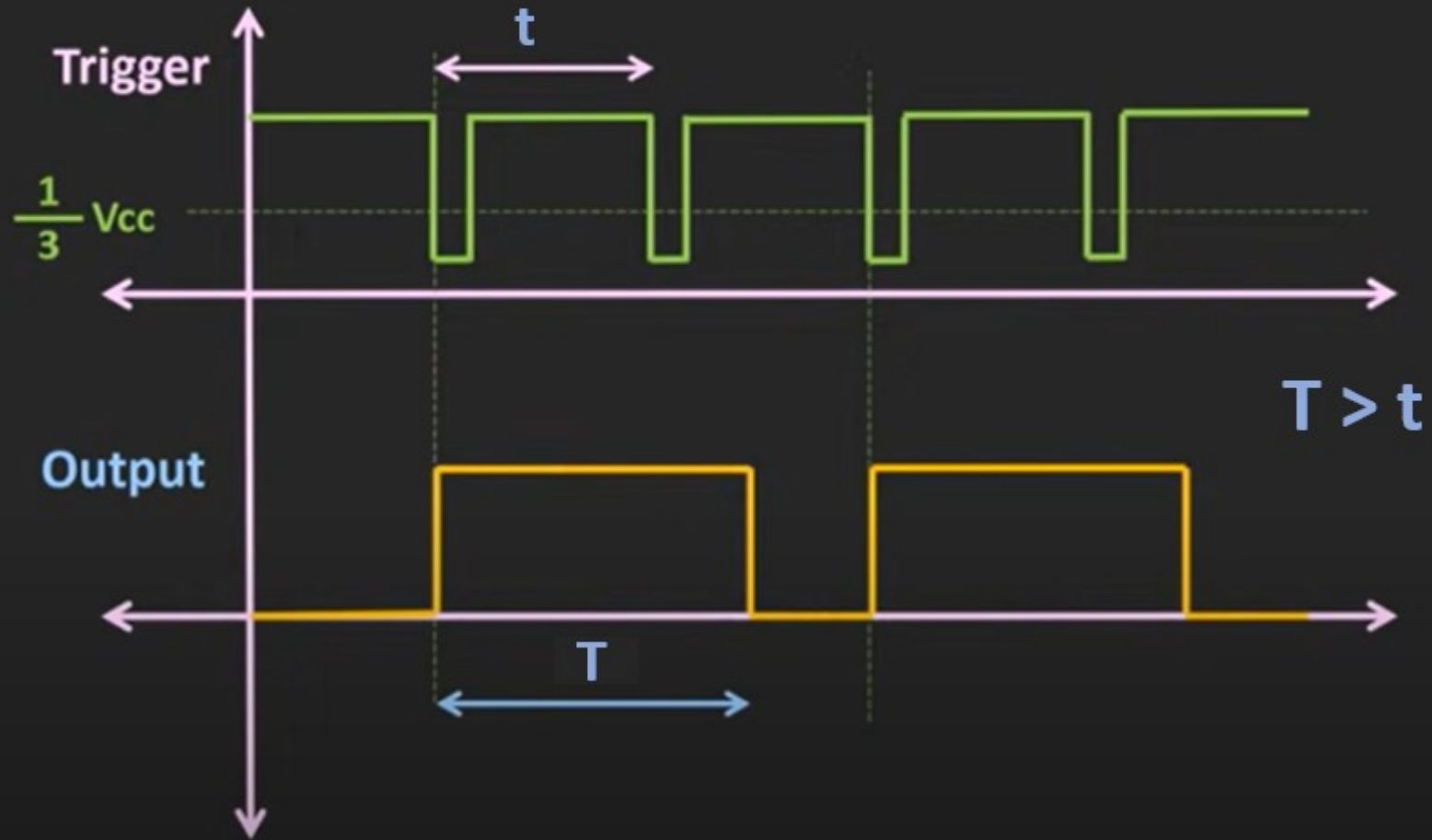

3. For pulse width modulation (PWM)


Till now we used only internal reference voltages.

If we apply a modulating s/g at control pin, it is possible to generate PW modulated o/p.

Here ref V will continuously change based on this modulating s/g.

Depending on that o/p PW will continuously change.

Pulse Width Modulation (PWM)

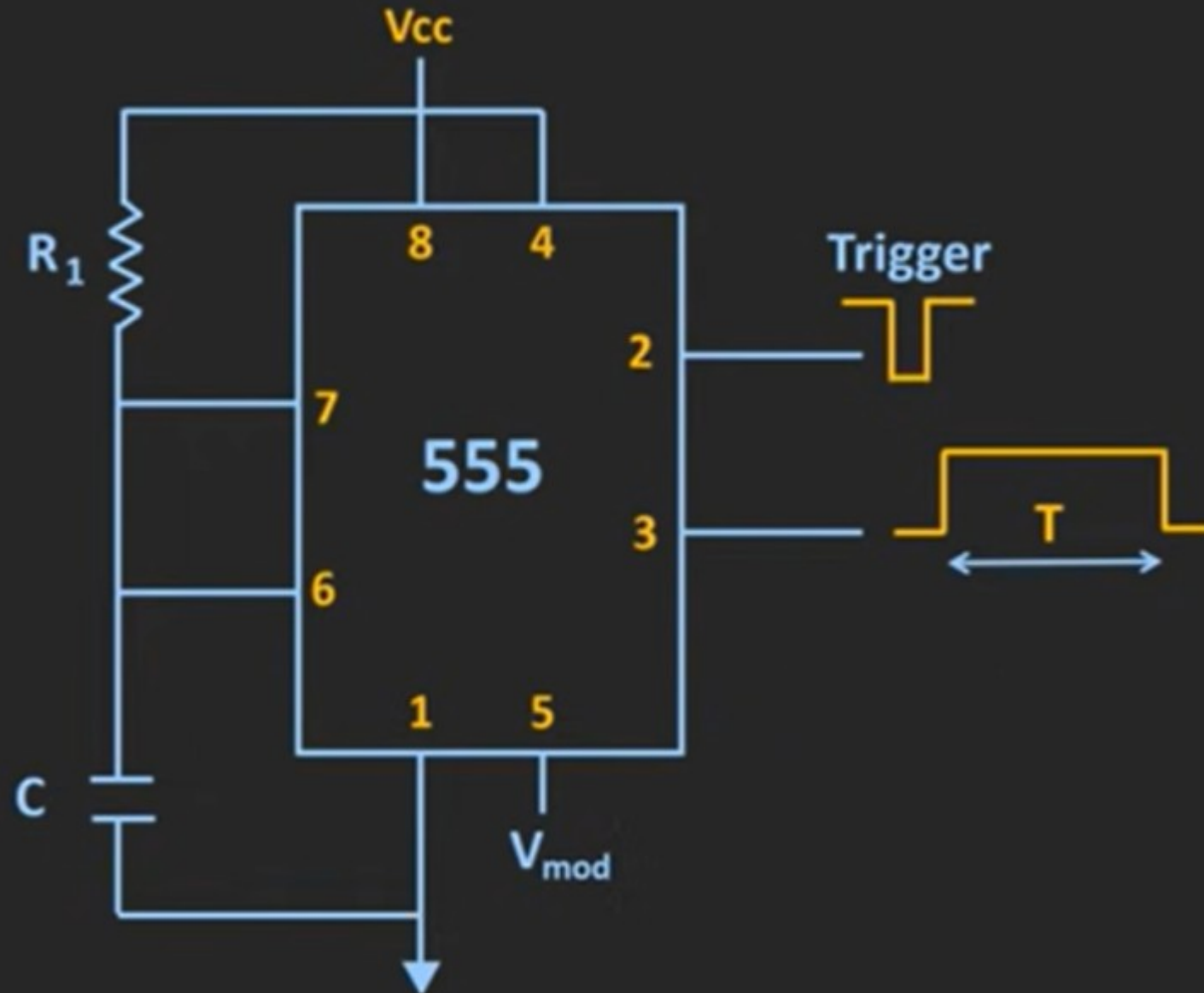

DESIGN

$$V_c(t) = V_F + (V_I - V_F)$$


To find T

$$V_I = 0$$

$$V_F = V_{cc}$$

$$V_c(t) = \frac{2}{3} V_{cc}$$

$$R' = R_1$$

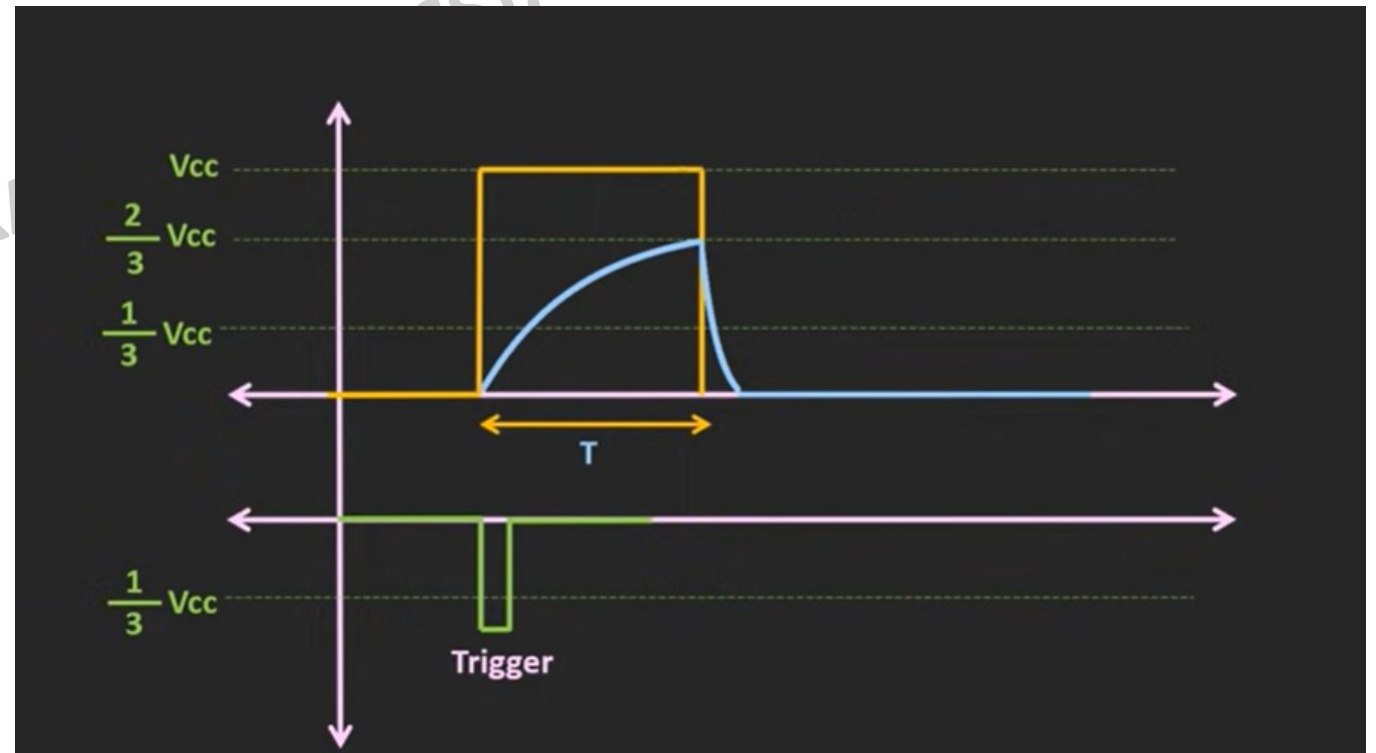

$$T = 1.1 R_1 C$$

PREPARED BY RINJU RAVINDRAN, ADHOC ASST. PROFESSOR-ECE, GCEK