


EXPERIMENT .NO.7
DATE:--/--/--

RC PHASE SHIFT OSCILLATOR USING OP-AMPS

AIM

To design and setup an RC Phase shift Oscillator using op-amp for a frequency of oscillation= 1kHz


THEORY

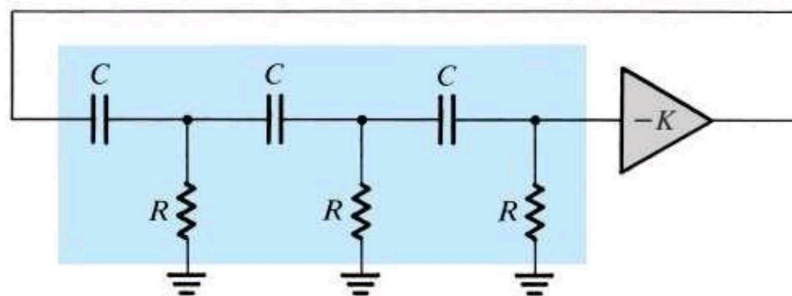

The basic structure of a phase shift oscillator consists of a negative gain amplifier ($-K$) with a 3-section RC ladder network in the feedback.

The circuit will oscillate at the frequency for which the total phase shift of the RC network is 180° . Only at this frequency will the total phase shift around the loop be 0° or 360°

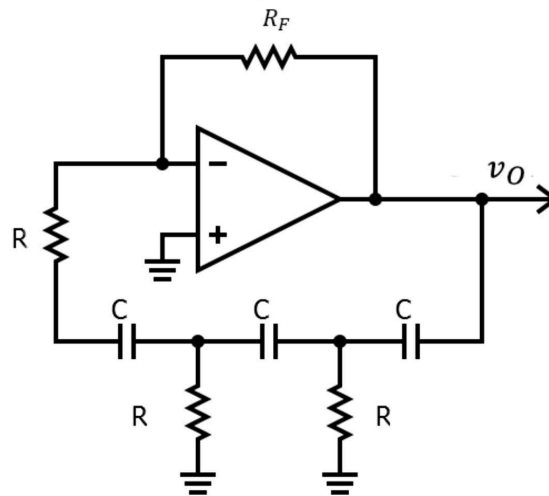The reason for using a three-section RC network is that three is the minimum number of sections (i.e., lowest order) that is capable of producing a 180° phase shift at a finite frequency.



The above circuit shows an RC Phase shift oscillator using an operational amplifier. It consists of an op-amp as the amplifier stage and 3 cascaded RC networks as the feedback circuit.

The op amp is used in the inverting mode \Rightarrow provides 180° phase shift

Additional 180° phase shift required for oscillation is provided by the cascaded RC networks. At some specific frequency f_0 , when the phase shift of the cascaded RC networks is exactly 180° & the gain of the amplifier is sufficiently large, the circuit will oscillate at that frequency.

The frequency of oscillation f_0 is given by, $f_0 = \frac{1}{2\pi RC\sqrt{6}} \cong \frac{0.065}{RC}$

At this frequency, the gain, A_v must be at least 29. *i.e.*, $\left|\frac{R_F}{R}\right| = 29$ or $R_F = 29R$

i.e., this circuit will produce a sinusoidal waveform of frequency f_0 if the gain is 29 & the total phase shift around the circuit is exactly 360°

One important feature of an RC Oscillator is its frequency stability. *i.e.*, it is able to provide a constant frequency sine wave output under varying load conditions.

However, RC Oscillators are restricted to low frequency (e.g.: audio frequency) applications because of their bandwidth limitations to produce the desired phase shift at high frequencies.

DESIGN

The attenuation β of the three section RC feedback network is, $\beta = 1/29$

To meet the greater than unity loop gain requirement, the closed loop voltage gain of op-amp must be greater than 29.

Desired frequency of oscillations = $1kHz$

$$\text{We have, } f_0 = \frac{1}{2\pi RC\sqrt{6}} \cong \frac{0.065}{RC}$$


$$\text{Choose } C = 0.01\mu F; \Rightarrow R = \frac{0.065}{0.01\mu F \times 1kHz} = 6.5k; \text{ Choose } 6.8k \text{ Std.}$$

$$\Rightarrow R_F = 29R = 197.2k; \text{ Use } 220k \text{ pot. (Or } 150k \text{ Resistor in series with a } 100k \text{ pot.)}$$

PROCEDURE

- Setup the circuit and provide supply voltages to the op-amp
- Adjust the $220k$ pot until a stable sinusoidal waveform appears at the output of the op-amp
- Observe the waveforms at the output of the op-amp v_o and note down its frequency

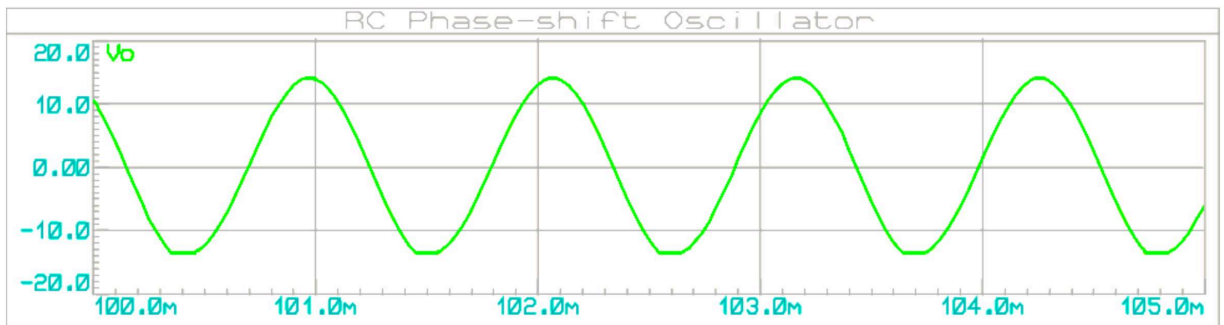Expected Waveforms: RC-Phase shift oscillator



OBSERVATIONS

RESULTS

An RC Phase shift Oscillator using op-amp was designed and setup for a frequency of oscillation = 1kHz

- Observed frequency of oscillations = _____