

# ANALOG CIRCUITS ASSIGNMENT

Submitted By


Arun C-S

ECE SH -B

Roll No: 50

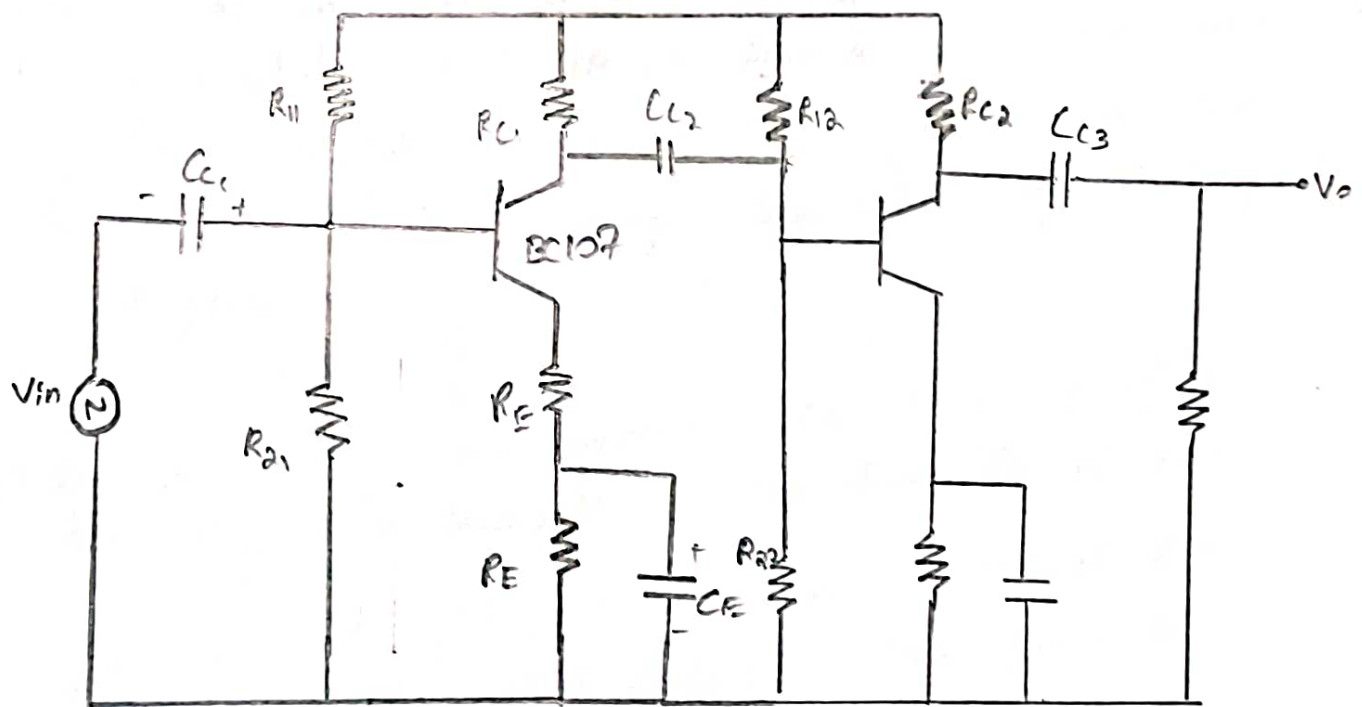Q1 With schematic explain a two stage RC coupled amplifier. what are the effect of cascading in gain and bandwidth of amplifier.

Ans. Multistage amplifiers are used for cascading to improve parameters such as voltage/current gain, input/output resistance. A two stage amplifier provides an overall voltage gain of  $A_1$  and  $A_2$  which are the <sup>gains</sup> of first and second respectively. Since each stage provides a phase reversal. the input and output signal will be in phase.



The input of second stage is in parallel with  $RC_1$  of the first stage. The voltage gain of the first stage is

$$A_1 = \frac{RC_1 \parallel R_{i2}}{r_e}$$

where  $R_{i2}$  is the input resistance of the second stage

$$R_{i2} = R_{12} \parallel R_{22} \parallel (1 + h_{fe}) r_e$$

$$h_{fe} = 100$$


$$A_2 = \frac{R_{C2} \parallel R_L}{r_e}$$

care must be taken while selecting  $A_2$  and  $A_1$ . If  $A_1$  is large, the input to the second stage will become too high. The gain of the first stage can be controlled by a negative feedback in series with emitter, this is achieved by unbypassed resistor  $R_e$ .

Effects of cascading is that, single stage amplifier is not able to provide enough power and fulfill all the requirement of an ideal amplifier, so multistage amplifier is required. In multistage amplifier, a number of single amplifiers are connected in cascade arrangement i.e., output of first stage is connected to input of second stage, hence increasing voltage and current gain.

Q. With circuit schematic explain the working of cascade amplifier. How wide bandwidth is obtained in cascade amplifier?

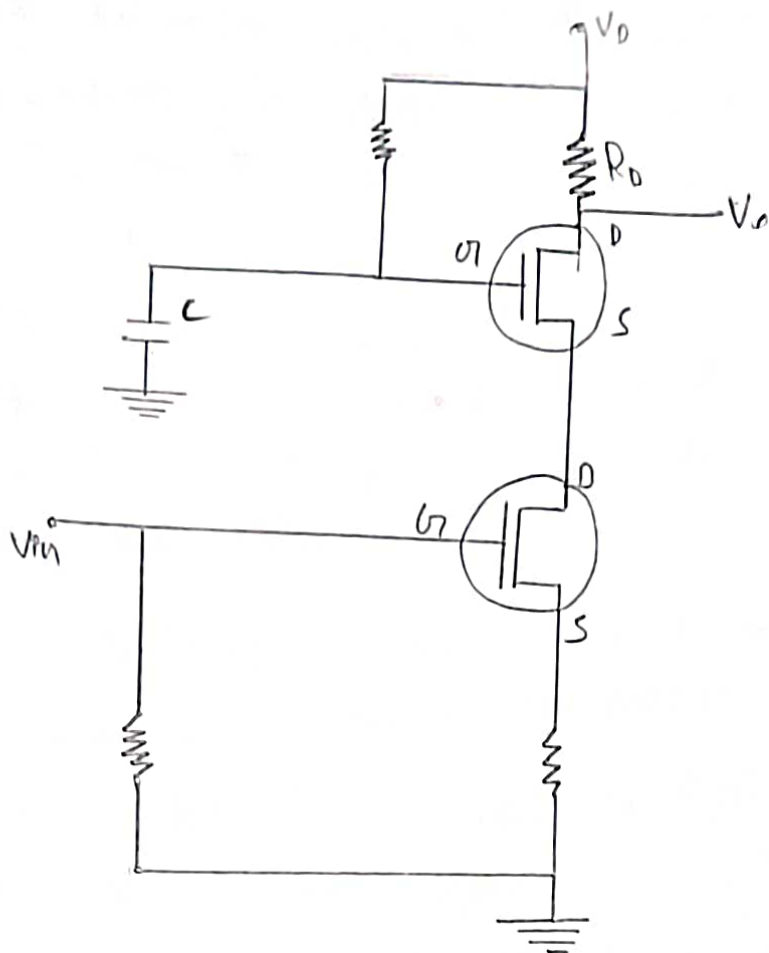A) A cascade amplifier is a double staged circuit with a buffer amplifier that follows the transconductance amplifier.



If an amplifier comprises of BJT, then the input stage is C-E configuration that leads to the common base at which output is collected. This type of amplifier is known as cascode amplifier.

The input signal is applied at the terminal gate of initial stage. The second stage that is output stage that is driven from the output of the ~~individual stage~~ initial stage's configuration. Common drain. The final output is collected from the drain terminal at which the resistor  $R_D$  is connected. The gate of the FET at the second stage is grounded. So the values of the source voltage of the second stage FET has remained equivalent to the drain voltage of the first stage FET.

FET at the second stage offers a low resistance path. The gain of the FET as the broad page is reduced.




which indirectly reduces miller effect, hence increase bandwidth. The overall gain does not get affected because it is compensated by the FET in second stage.

As the voltage at the source and drain of the first stage FET, gate and the source terminals of second stage FET is almost constant. Hence there is nothing to be traded. This leads to isolation and the condition is called miller effect.

**High Bandwidth:** A cascade amplifier uses 2 mismatched stages in order to minimize the reverse voltage feed. No negative feedback technique is useful at high frequencies. Next because of CB stage, the miller capacitance of transistor is minimised by limiting voltage gain of amplifier to 1. Avoiding the miller capacitance boosting is biggest advantage.

30) Derive expression for voltage gain, input impedance and output impedance of current series and current shunt amplifiers with feedback.

i) Current series feedback:-

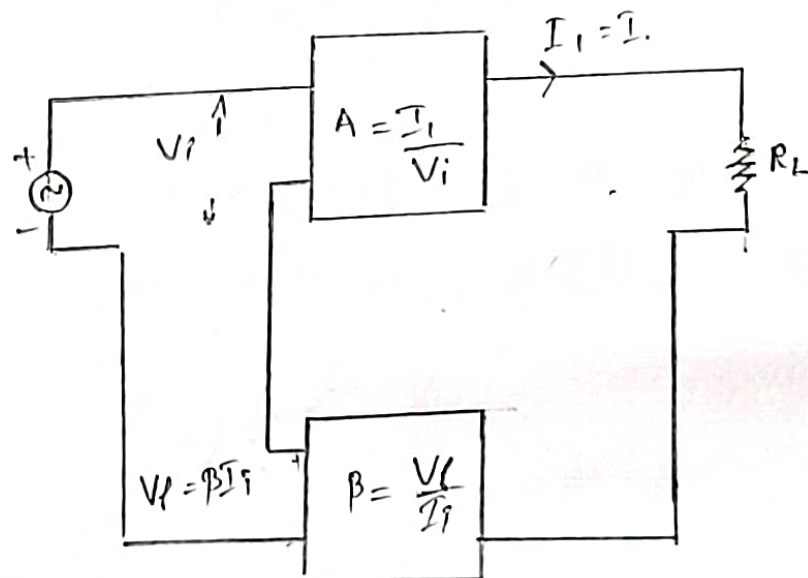

i) Input impedance of current series feedback

$$R_{if} = \frac{V_s}{I_i}$$

we know  $V_s = V_i + V_f$

$$\Rightarrow R_{if} = \frac{V_i + V_f}{I_i}$$

$$V_f = \beta V_o \Rightarrow R_{if} = \frac{V_i + \beta V_o}{I_i} = \frac{V_i}{I_i} \left( 1 + \frac{\beta V_o}{V_i} \right)$$

$$\frac{V_o}{V_i} = A \Rightarrow R_{if} = (1 + \beta A) \frac{V_i}{I_i}$$

$$\frac{V_i}{I_i} = R_i \Rightarrow R_{if} = R_i (1 + \beta A)$$

ii) Output impedance of current series amplifier and output impedance of current-shunt amplifier with feedback

Total current,  $I = \frac{V}{R_o} + A I_i$

$$= V = (I - A I_i) R_o \rightarrow (1)$$

Source current  $I_s = I_i + I_f$

$$I_s = 0$$

$$I_i = -I_f$$

$$I_f = \beta I_o$$

$$I_i = -\beta I_o$$


$$\Rightarrow I_i = \beta I_o \Rightarrow I_i = \beta I \rightarrow (2)$$

$$\Rightarrow V_s = (I + \beta A I) R_o \rightarrow (3)$$

$$\therefore R_{of} = \frac{V}{I}$$

$$= \frac{(I + \beta A I) R_o}{I} = \frac{I (1 + \beta A) R_o}{I} = (1 + \beta A) R_o$$

2) Current shunt feedback:

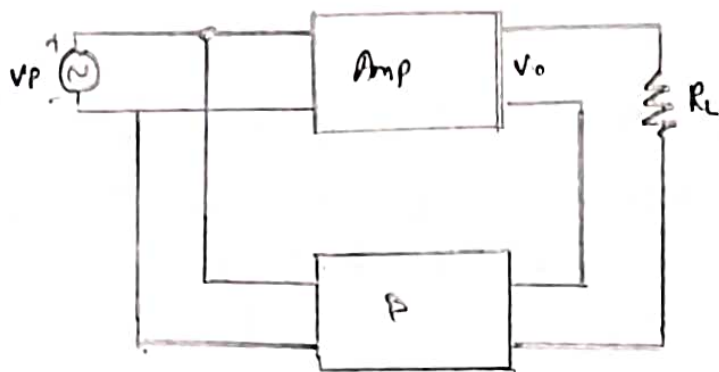

iii) Current shunt feedback:

$$R_{if} = \frac{V_i}{I_B}$$

$$I_s = I_i + I_f$$

$$I_f = \beta I_o$$


$$\Rightarrow R_{if} = \frac{V_i}{I_i + \beta I_o} = \frac{V_i}{I_i \left(1 + \frac{\beta I_o}{I_i}\right)}$$

$$A_{vif} = \frac{I_o}{I_i} = A \Rightarrow R_{if} = \frac{V_i}{I_i (1 + A\beta)}$$

$$\therefore \frac{V_i}{I_i} = R_i \Rightarrow R_{if} = \frac{R_i}{(1 + A\beta)}$$

- \* Gain with feedback of current series  $A_f = I_o/V_i$
- \* Gain with feedback for current shunt  $A_i = I_o/I_i$

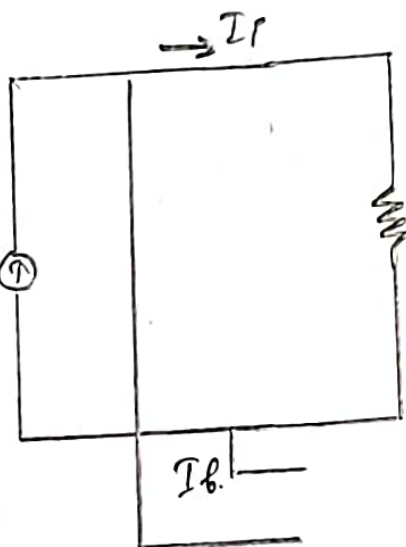Source current  $\rightarrow I_s$   
Input current  $\rightarrow I_i$   
Input Resistance  $\rightarrow R_i$




$$I_f = \beta I_o$$

Q. Define piezo electric effect, with circuit schematic explain the working principle of crystal oscillator

piezo electric effect: piezo electric effect is the ability of certain material to generate an electric charge in response to applied stress.

When a piezoelectric crystal is placed under mechanical stress, a shifting of positive and negative charge centres in the material takes place, which results in an external field. When reversed, an outer electrical field either stretches or compresses the piezoelectric material.

Crystal oscillator: -

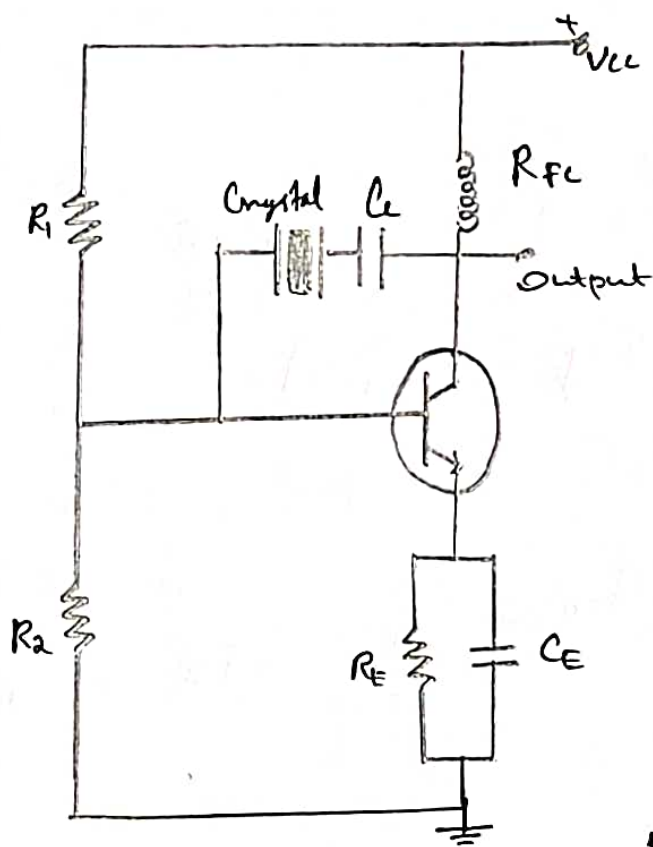

- Crystal oscillator is basically a tuned circuit using piezoelectric crystal as the resonant tank circuit.
- These oscillators are used where a higher frequency stability is required such as in communication transmitters and receivers.
- piezoelectric crystal exhibits piezoelectric property: the ability to transform mechanical deformation into electrical charge, and vice versa.
- If a piezoelectric material is squeezed it develops a voltage and if a voltage is applied across



If a mechanical dimension occurs,

- Crystal oscillator operate on the principle of inverse piezo electric effect, in which alternating voltage is applied causing it to vibrate at its natural frequency.
- It's these vibrations which eventually get converted into oscillation,
- These oscillators are usually made of quartz crystal.