

EXPERIMENT NO. 4

DATE: -- / -- /----

## SCHMITT TRIGGER CIRCUITS USING OP-AMPS

### AIM


To design and setup,

- 1 Inverting Schmitt trigger circuits using op-amp IC 741
  - a) For Symmetric Trigger Points,  $v_{TH} = 6.5V$  and  $v_{TL} = -6.5V$
  - b) For Asymmetric Trigger Points,  $v_{TH} = 8V$  and  $v_{TL} = 3V$
2. A non-inverting Schmitt trigger circuit using op-amp IC 741
  - a) For Symmetric Trigger Points,  $v_{TH} = 6.5V$  and  $v_{TL} = -6.5V$

### THEORY

Schmitt triggers are special type of comparators with hysteresis, which can be implemented by providing operational amplifiers/comparators with positive feedback. Its output voltage has two stable states namely  $v_O = V_{OH}$  and  $v_O = V_{OL}$ . For an op-amp  $V_{OH} = +V_{sat}$  and  $V_{OL} = -V_{sat}$  respectively

### INVERTING SCHMITT TRIGGER

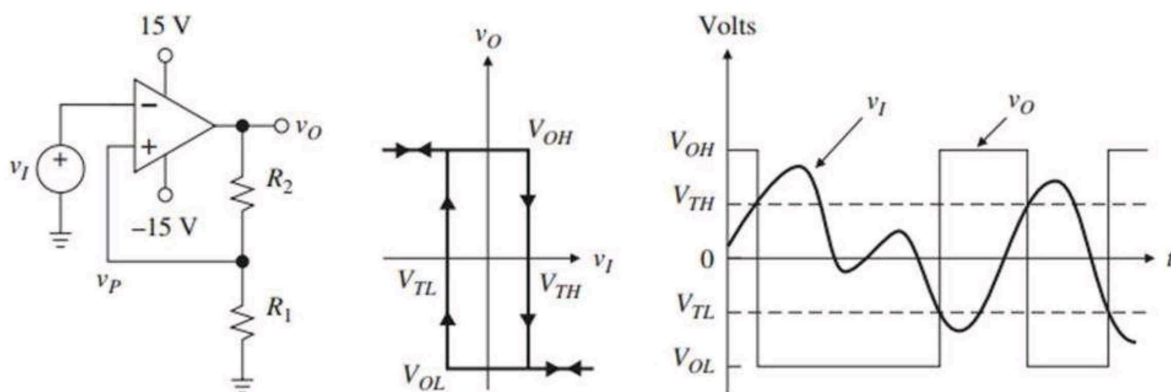

The inverting Schmitt trigger circuit can be viewed as an inverting-type threshold detector whose threshold is controlled by the output. Since the output has two stable states, this threshold has two possible values, namely  $V_{TH} = \frac{R_1}{R_1+R_2} \cdot V_{OH}$  &  $V_{TL} = \frac{R_1}{R_1+R_2} \cdot V_{OL}$


For  $v_I \ll 0$ , the amplifier saturates at  $V_{OH}$ , giving  $v_O = V_{OH}$  and  $v_P = V_{TH}$ . Increasing  $v_I$  moves the operating point along the upper segment of the Voltage Transfer Curve (VTC) until  $v_I$  reaches  $V_{TH}$ . At this point, the regenerative action of positive feedback causes  $v_O$  to snap from  $V_{OH}$  to  $V_{OL}$ . This, in turn, causes  $v_P$  to snap from  $V_{TH}$  to  $V_{TL}$ . If we wish to change the output state again to  $V_{OH}$ , we must now lower  $v_I$  all the way down to  $v_P = V_{TL}$ .

Thus, the Voltage Transfer Curve of an Inverting Schmitt trigger exhibits hysteresis (i.e., has two separate tripping points). When coming from the left, the threshold is  $V_{TH}$ , and when coming from the right, it is  $V_{TL}$ . The horizontal portions of the VTC can be traveled in either direction, but the vertical portions can be traveled only clockwise.

The hysteresis width,  $\Delta V_T = V_{TH} - V_{TL} = \frac{R_1}{R_1+R_2} \cdot (V_{OH} - V_{OL})$

$\Delta V_T$  can be varied by changing the ratio  $R_1/R_2$ . Decreasing  $R_1/R_2$  will bring  $V_{TH}$  and  $V_{TL}$  closer together.

## NON-INVERTING SCHMITT TRIGGER

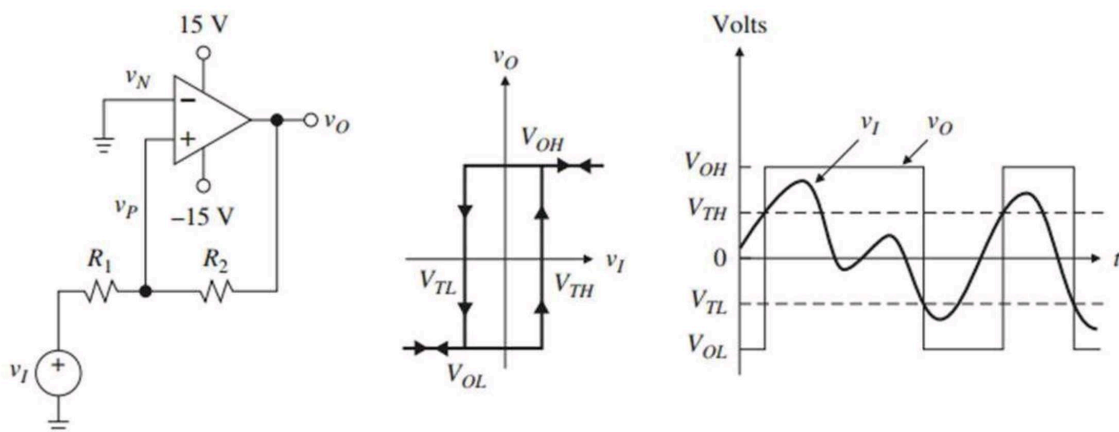

For  $v_I \ll 0$ , the op-amp saturates at  $V_{OL}$ . For  $v_O$  to switch state,  $v_I$  must be raised to a high enough value (called  $V_{TH}$ ) to cause  $v_P > v_N (= 0V)$

$$\Rightarrow \frac{V_{TH}-0}{R_1} = \frac{0-V_{OL}}{R_2} \quad \Rightarrow V_{TH} = -\frac{R_1}{R_2} \cdot V_{OL}$$

Once  $v_O$  has reached  $V_{OH}$ , in order to step it back to  $V_{OL}$ ,  $v_I$  must be lowered below  $V_{TL}$

$$\Rightarrow \frac{V_{OH}-0}{R_2} = \frac{0-V_{TL}}{R_1} \quad \Rightarrow V_{TL} = -\frac{R_1}{R_2} \cdot V_{OH}$$


The hysteresis width is  $\Delta V_T = \frac{R_1}{R_2} \cdot (V_{OH} - V_{OL})$ . It can be varied by changing the ratio  $\frac{R_1}{R_2}$

Thus, the Voltage Transfer Curve of a Non-inverting Schmitt trigger exhibits hysteresis (i.e., has two separate tripping points). When coming from the left, the threshold is  $V_{TH}$ , and when coming from the right, it is  $V_{TL}$ . The horizontal portions of the VTC can be traveled in either direction, but the vertical portions can be traveled only counter-clockwise
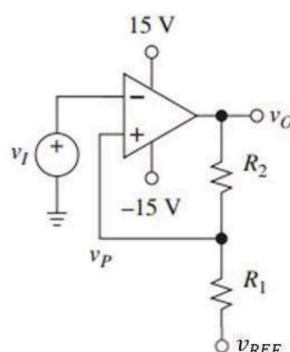
## SCHMITT TRIGGERS WITH ASYMMETRICAL TRIGGER POINTS

The hysteresis loop can be shifted to either side of zero point by connecting a reference voltage source as shown.

The following circuit shows an inverting Schmitt trigger with asymmetric trigger points.



For the above circuit,

$$v_P = \frac{R_1}{R_1 + R_2} \cdot v_O + \frac{R_2}{R_1 + R_2} \cdot v_{REF}$$

$$\text{Hence, } V_{TH} = \frac{R_1}{R_1 + R_2} \cdot V_{OH} + \frac{R_2}{R_1 + R_2} \cdot v_{REF}$$

$$\text{And } V_{TL} = \frac{R_1}{R_1 + R_2} \cdot V_{OL} + \frac{R_2}{R_1 + R_2} \cdot v_{REF}$$

$$\Delta V_T = V_{TH} - V_{TL} = \frac{R_1}{R_1 + R_2} \cdot (V_{OH} - V_{OL}) \text{ i.e., the hysteresis width remains the same}$$

If  $v_{REF}$  is positive, the hysteresis loop is shifted to right side; if  $v_{REF}$  is negative, the loop is shifted to the left side.

## DESIGN

### INVERTING SCHMITT TRIGGER

$$V_{TH} = \frac{R_1}{R_1 + R_2} \cdot V_{sat} \quad \& \quad V_{TL} = \frac{R_1}{R_1 + R_2} \cdot (-V_{sat})$$

For  $\pm 15V$  supply for uA741,  $V_{sat} \cong +13V$  and  $-V_{sat} \cong -13V$

$$\text{Required } v_{TH} = 6.5V = \frac{R_1}{R_1 + R_2} \cdot (+13V) \Rightarrow \frac{R_1}{R_1 + R_2} = \frac{1}{2}$$

$$\text{Choose } R_1 = 10k, R_2 = 10k \text{ so that, } V_{TH} = \frac{V_{sat}}{2} \cong 6.5V \text{ and } V_{TL} = \frac{-V_{sat}}{2} \cong -6.5V$$

$$\text{Hysteresis width} = \Delta V_T = V_{TH} - V_{TL} \cong 13V$$

### NON-INVERTING SCHMITT TRIGGER

$$V_{TH} = -\frac{R_1}{R_2} \cdot V_{OL} = -\frac{R_1}{R_2} \cdot (-V_{sat})$$

$$V_{TL} = -\frac{R_1}{R_2} \cdot V_{OH} = -\frac{R_1}{R_2} \cdot (V_{sat})$$

$$\Delta V_T = \frac{R_1}{R_2} \cdot (V_{OH} - V_{OL}) = \frac{R_1}{R_2} (V_{sat} - (-V_{sat}))$$

For  $\pm 15V$  supply for uA741,  $V_{sat} \cong +13V$  and  $-V_{sat} \cong -13V$

$$\text{Required } v_{TH} = 6.5V = \frac{R_1}{R_2} \cdot (13V) \Rightarrow \frac{R_1}{R_2} = \frac{1}{2}$$

Take  $R_1 = 10k$  and  $R_2 = 20k$  (Use two  $10k$  in series) so that  $V_{TH} \cong 6.5V$  and  $V_{TL} \cong -6.5V$

### **INVERTING SCHMITT TRIGGER WITH ASYMMETRICAL TRIGGER POINTS**

Required value of  $v_{TH} = 8V$ ,  $v_{TL} = 3V$

$$\text{Hence required } \Delta V_T = V_{TH} - V_{TL} = \frac{R_1}{R_1 + R_2} \cdot (V_{OH} - V_{OL}) = 8 - 3 = 5V$$

For  $\pm 15V$  supply for uA741,  $V_{sat} \cong +13V$  and  $-V_{sat} \cong -13V$

$$\Rightarrow 5V = \frac{R_1}{R_1 + R_2} (V_{sat} - (-V_{sat})) = \frac{R_1}{R_1 + R_2} \times 26V$$

$$\Rightarrow \frac{R_1}{R_1 + R_2} = \frac{5}{26}$$

Take  $R_1 = 8.2k$ ;  $\Rightarrow R_2 = 33k$  std.

$$\text{Now } V_{TH} = \frac{R_1}{R_1 + R_2} \cdot V_{sat} + \frac{R_2}{R_1 + R_2} \cdot v_{REF}$$

$$\Rightarrow 8V = \frac{R_1}{R_1 + R_2} \cdot V_{sat} + \frac{R_2}{R_1 + R_2} \cdot v_{REF} = \frac{8.2k}{41.2k} \times 13 + \frac{33k}{41.2k} v_{REF}$$


$$\Rightarrow v_{REF} \cong 6.8V$$

### **PROCEDURE (Common For all three circuits)**


- Setup the circuit and apply supply voltages to the op-amp terminals
- Give a  $20V_{pp}$  sinewave with a frequency of  $200Hz$  as  $v_I$

- Observe the input waveform  $v_i$  and the output waveform  $v_o$  simultaneously on the CRO
- Draw the observed waveforms and note down the upper and lower threshold voltages for the inputs
- Draw the transfer curve(  $v_o$  vs.  $v_i$  ) from the above observations and compute the hysteresis width

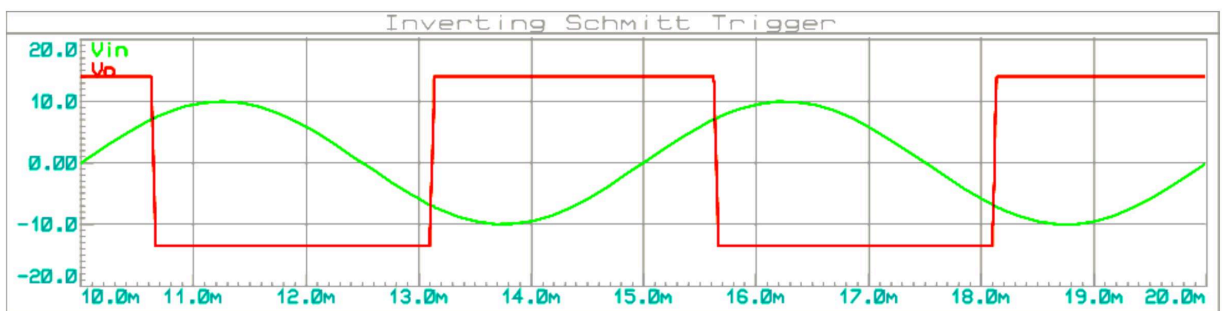
Expected Waveforms: Inverting Schmitt Trigger Circuit(Symmetric Trigger Points)



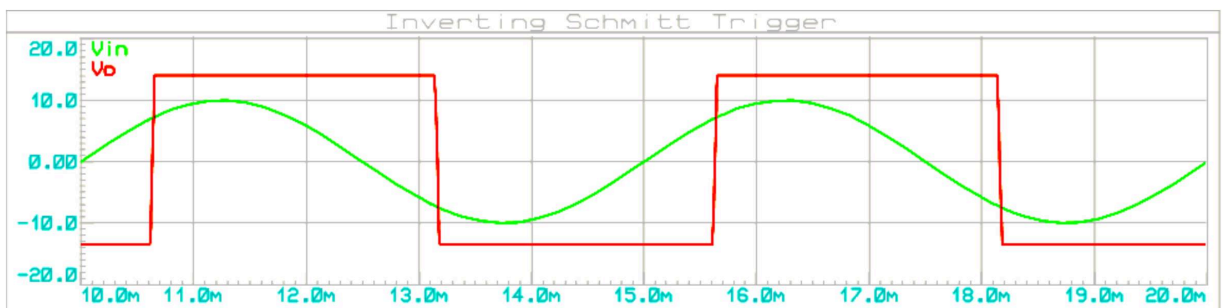Expected Waveforms: Non-inverting Schmitt Trigger Circuit(Symmetric Trigger Points)



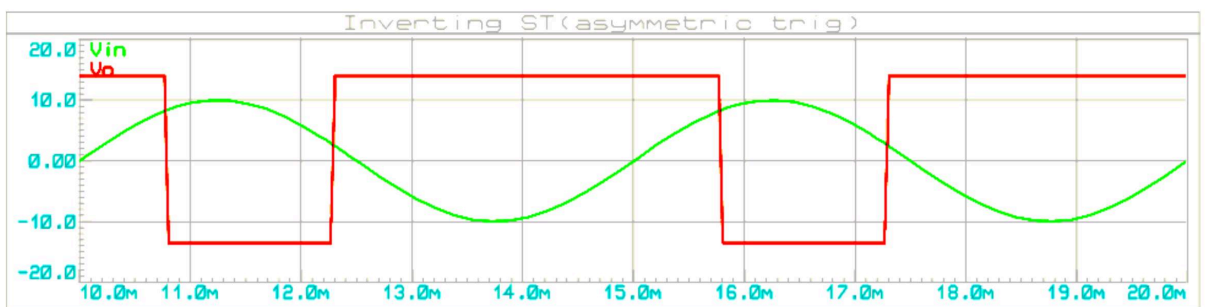Expected Waveforms: Inverting Schmitt Trigger Circuit (Asymmetric Trigger Points)



## OBSERVATIONS

....

## RESULTS

The following Schmitt trigger circuits were designed and setup using op-amp IC 741  
The transfer characteristics were plotted.

1. An inverting Schmitt trigger with symmetric threshold points
  - Designed threshold voltages:  $V_{TH} = \text{—}$  and  $V_{TL} = \text{—}$
  - Designed Hysteresis width:  $\Delta V_T = \text{—}$
  - Observed threshold voltages:  $V_{TH} = \text{—}$  and  $V_{TL} = \text{—}$
  - Observed Hysteresis width:  $\Delta V_T = \text{—}$
2. A non-inverting Schmitt trigger with symmetric threshold points
  - Designed threshold voltages:  $V_{TH} = \text{—}$  and  $V_{TL} = \text{—}$
  - Designed Hysteresis width:  $\Delta V_T = \text{—}$
  - Observed threshold voltages:  $V_{TH} = \text{—}$  and  $V_{TL} = \text{—}$
  - Observed Hysteresis width:  $\Delta V_T = \text{—}$
3. An inverting Schmitt trigger with asymmetric threshold points
  - Designed threshold voltages:  $V_{TH} = \text{—}$  and  $V_{TL} = \text{—}$
  - Designed Hysteresis width:  $\Delta V_T = \text{—}$
  - Observed threshold voltages:  $V_{TH} = \text{—}$  and  $V_{TL} = \text{—}$
  - Observed Hysteresis width:  $\Delta V_T = \text{—}$