

Reg No.: LKNR 21EC105Name: Arum. C. J**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

Third Semester B.Tech Degree Regular and Supplementary Examination December 2022 (2019 Scheme)

Course Code: ECT203**Course Name: LOGIC CIRCUIT DESIGN**

Max. Marks: 100

Duration: 3 Hours

PART A*Answer all questions. Each question carries 3 marks*

Marks

- 1 Convert the decimal number 215 to following codes (3)
(i)BCD code (ii)Excess 3 code (iii) Gray code
- 2 Convert the decimal number 18.6875 into binary and hexadecimal. (3)
- 3 Write Verilog Code for a XOR gate (3)
- 4 Express $f(A,B,C) = AB + AC' + BC$ in standard SOP form. (3)
- 5 Design a 1-bit comparator circuit using logic gates. (3)
- 6 Realize an 8:1 multiplexer using 4:1 multiplexers and gates. (3)
- 7 Convert a JK flip-flop to D flip-flop. (3)
- 8 Realize D latch using gates and write the Verilog code. (3)
- 9 Define the following in terms of Logical families i) Propagation delay ii) fan out (3)
iii) Noise margin
- 10 Draw the circuit diagram of a CMOS- NOT gate and explain the working with truth table. (3)

PART B*Answer any one full question from each module. Each question carries 14 marks***Module 1**

- a) Find the sum of two hexadecimal numbers $(85C)_{16}$ and $(23C6)_{16}$ (2)
- b) Convert each decimal number to binary and perform the subtraction $21.5_{10} - 13.25_{10}$ using (i)1's complement method(ii)2's complement method (4)
- c) Explain the main differences between the Verilog terms (8)
(i)Wire and Reg
(ii)Task and Function

- 12 a) How is the Hamming code word generated? The message "1001001" is coded in 7-bit even parity Hamming code, which is transmitted through a noisy channel. Decode the message, assuming that at most a single error occurred in each code word. (8)
- b) Explain Verilog operators with examples. (6)

Module 2

- ✓ 13 ✓ a) Simplify the Boolean expression $F(A, B, C, D) = \sum m(0, 1, 2, 6, 8, 9, 10, 11) + d(3, 7, 14, 15)$ using K-Map and implement the simplified expression using universal gates. (8)
- ✓ b) Prove the following Boolean rules (6)
- i. $A + AB = A$
- ii. $A + A'B = A + B$ (8)
- 14 a) Reduce the following function using Karnaugh map technique $f(A, B, C, D) = \pi M(0, 2, 4, 10, 11, 14, 15)$ and implement the simplified expression using NAND gates. (6)
- b) Explain the significance of duality principle in Boolean algebra (6)

Module 3

- 15 a) Implement the following functions using MUX (9)
- (i) AND (5)
- (ii) XOR
- iii) $f(A, B, C) = \sum m(0, 3, 5, 6)$
- ✓ b) Write a verilog code to implement 4:1 multiplexer. (9)
- 16 a) Implement a Full adder circuit using (9)
- (i) 3: 8 decoder (ii) 1:8 demultiplexer (5)
- b) Write a Verilog description for a one-bit full adder circuit

Module 4

- ✓ 17 ✓ a) Design a 3-bit synchronous up counter using T flip-flop. (9)
- ✓ b) Explain the operation of a 4-bit Ring counter. (5)
- 18 a) Design a divide by 2N circuit using N number of flip-flops. Draw the truth table and waveforms. (7)
- b) What is a race around condition related to JK Flip Flop? Explain how to eliminate the problem. (7)

Module 5

- 19 a) Describe the working of a 2-bit TTL NAND gate with Totem pole configuration. (8)
- b) Explain the working of a transistor level CMOS NOR gate. (6)
- ✓ 20 ✓ a) Describe the working of a tristate TTL inverter (8)
- ✓ b) Explain the working of a transistor level CMOS NAND gate. (6)
