
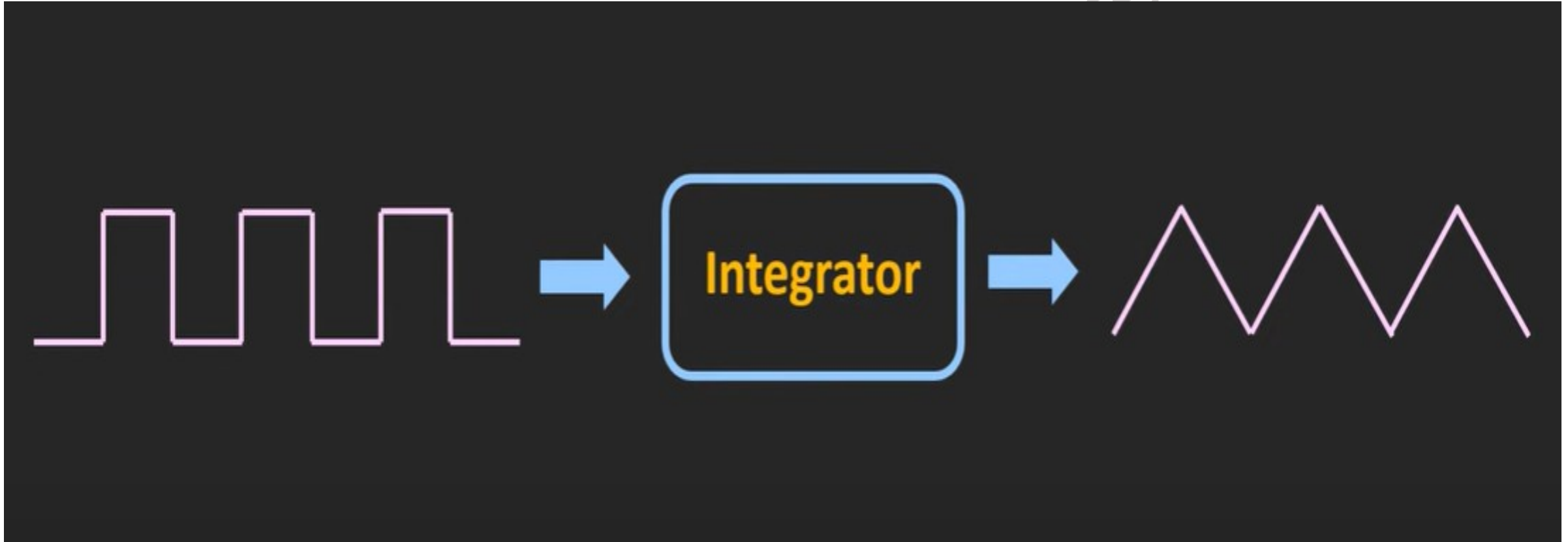



# TRIANGULAR WAVE GENERATOR

PROFESSOR-ECE, GCEK

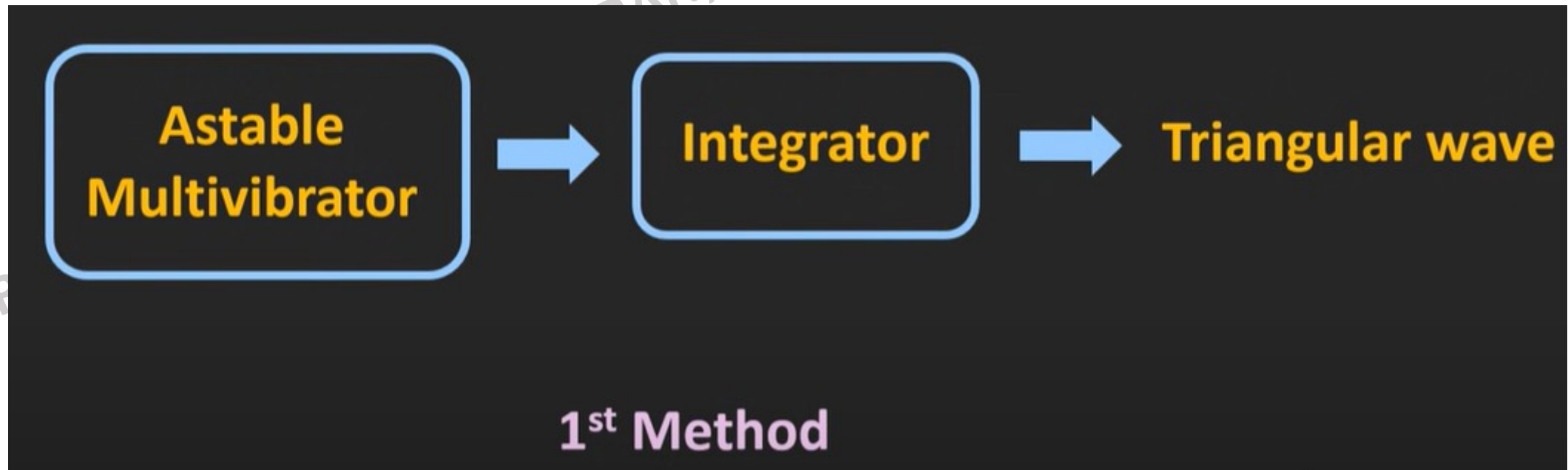





## 2<sup>nd</sup> Method

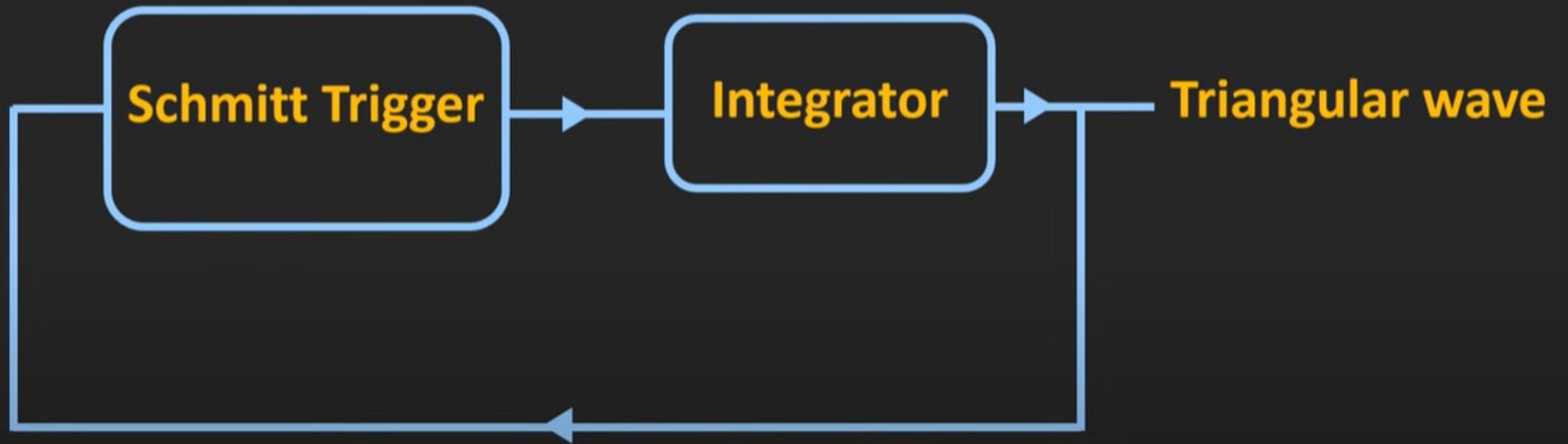

# TRIANGULAR WAVE GENERATOR METHOD 1

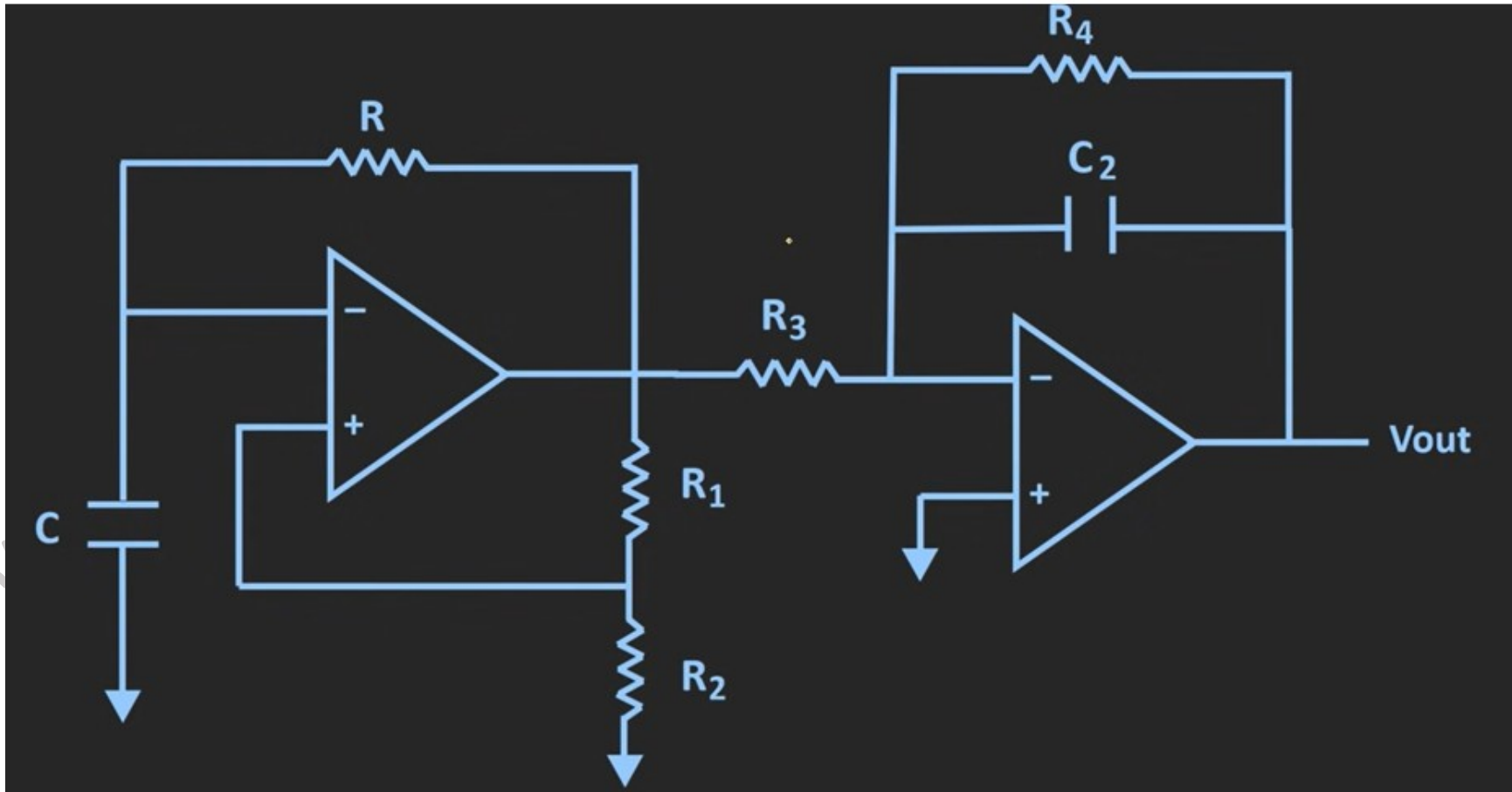

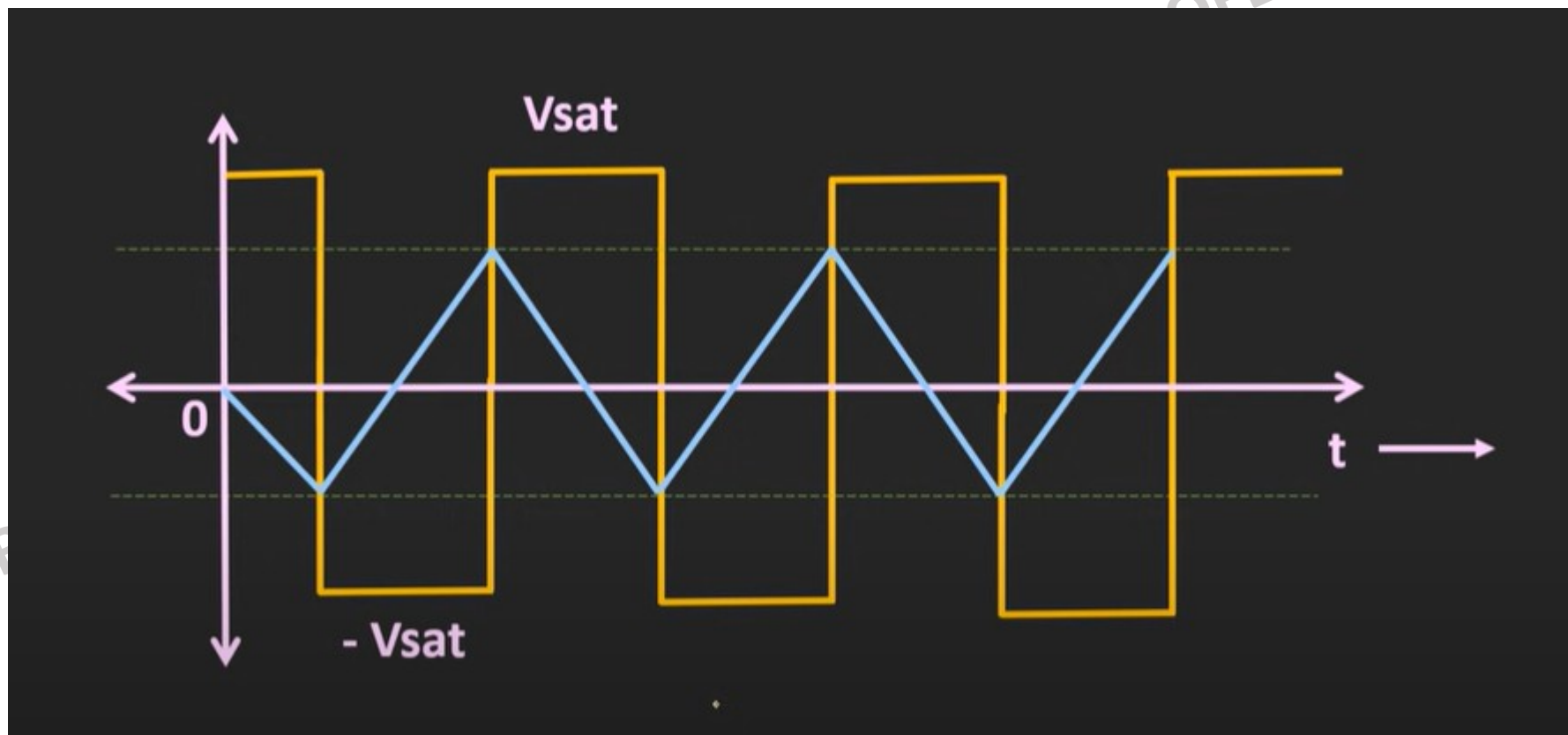


- It is clear that freq of square & triangle wave is same.
- Amp of square wave is constant at  $\pm V_{\text{sat}}$
- But the amp of triangle wave will decrease as freq increases.

It is bcoz of reactance of  $C_2$  in f/b ckt decreases at high freqs.

- $R_4$  to avoid saturation problem at low freq (practical integratr).

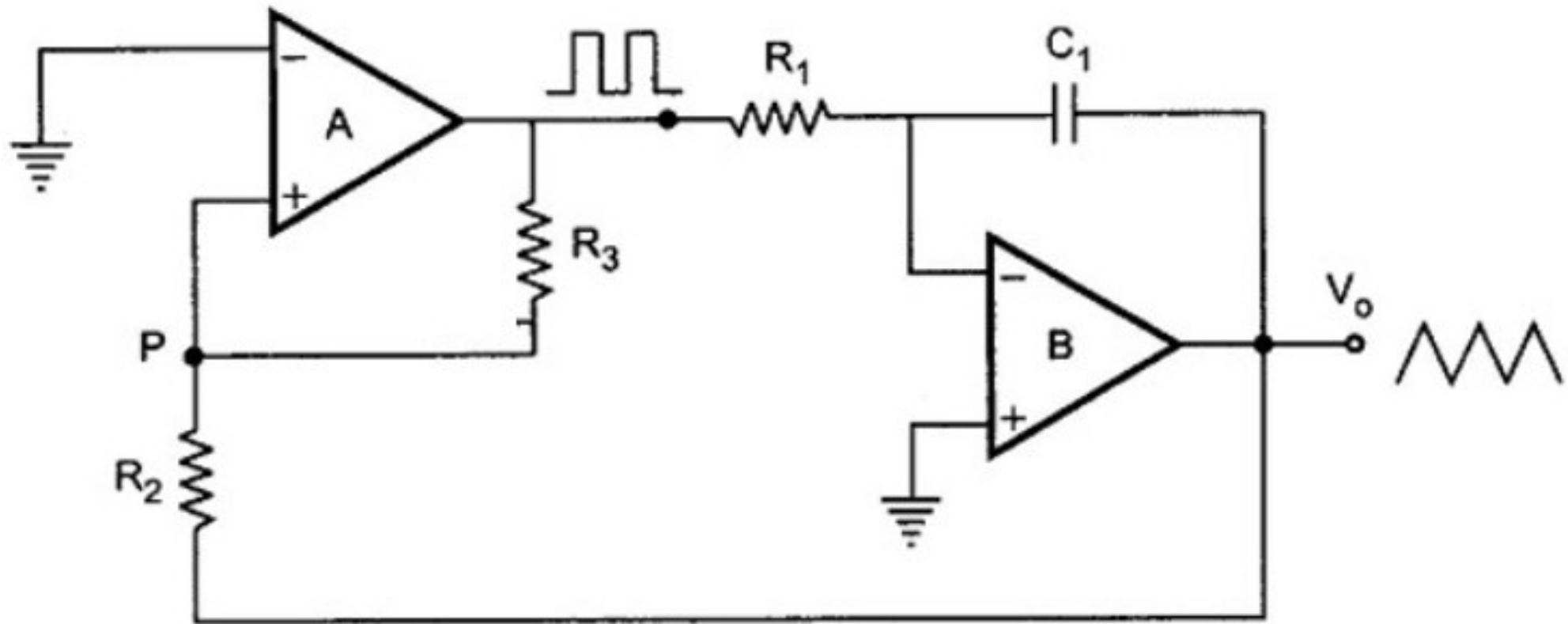
# Triangular Wave Generator Using Lesser Components (Method 2)



- Consists of 2 level comparator (Schmitt Trigger) followed by an integrator.
- o/p of comparator A is a square wave of amp  $\pm V_{\text{sat}}$
- This is applied to integrator B producing triangle wave.
- This triangle wave is fed back as i/p to comparator A thru a voltage divider R2R3.
- Initially let o/p of A is at  $+V_{\text{sat}}$ .
- o/p of B will be a –ve going ramp .



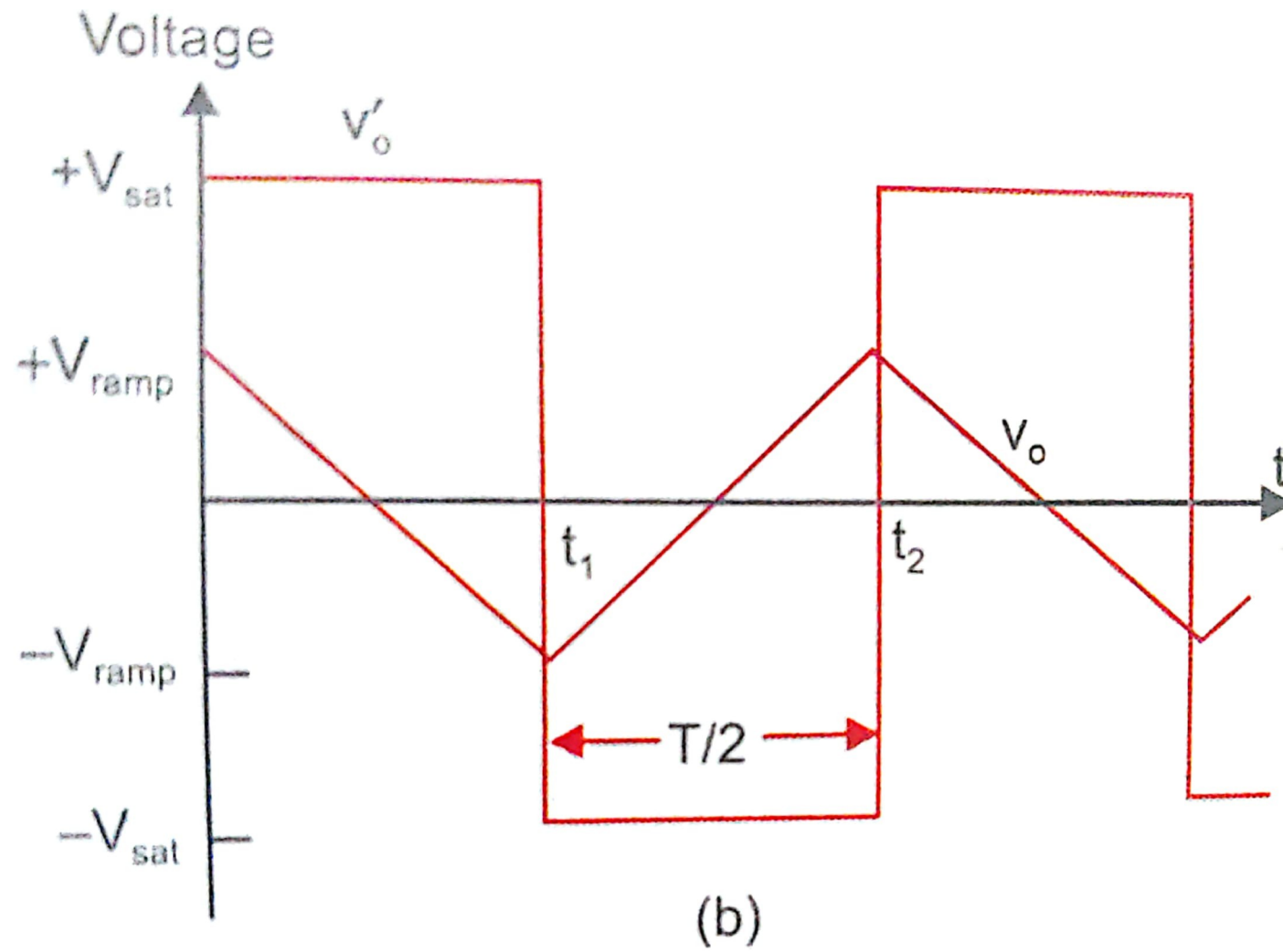- Initially R3 will be at the positive end of the A and it's another end will be at the negative due to the B negative going Ramp.
- So one end of V divider R2R3 is at  $+V_{sat}$  and other end at  $-ve$  going ramp.
- So at a certain point, the P will fall below the 0.
- Due to this the output of the square wave generator falls to the negative saturation voltage.



- At  $t=t_1$ , when  $-ve$  gng ramp attains a value of  $-V_{\text{ramp}}$ , effective  $V$  at pt  $P$  becomes slightly less than 0.
- o/p of  $A$  switches to  $-V_{\text{sat}}$ .
- o/p of  $B$  starts increasing in  $+ve$  dir.  $+ve$  gng ramp.
- At  $t=t_2$ ,  $V$  at  $P$  becomes jz above 0.
- So o/p of  $A$  again  $+V_{\text{sat}}$ .
- cycle repeats and generates a triangle wave.
- Freq of both wave same.
- But amp of triangle wave depends on  $RC$  value of integrator and o/p of  $A$ .

# Calculation of freq of triangle wave:

Effective V at P when o/p of A is +V<sub>sat</sub>

$$= V_{\text{sat}} + -V_{\text{ramp}}$$

- At t=t<sub>1</sub>, V at pt P = 0

$$V_{\text{sat}} + -V_{\text{ramp}} = 0$$

$$R_2 V_{\text{sat}} = R_3 V_{\text{ramp}}$$

$$-V_{\text{ramp}} = - (+V_{\text{sat}})$$

PREPARED BY RINJU RAVINDRAN, ADHOC ASST. PROFESSOR-ECE, GCEK

- At  $t=t_2$ , when o/p switches from  $-V_{sat}$  to  $+V_{sat}$

$$+V_{ramp} = -(-V_{sat})$$

$$+V_{ramp} = (V_{sat})$$

Peak to peak amp of tri wave

$$V_o(pp) = +V_{ramp} - (-V_{ramp})$$

$$V_o(pp) = (V_{sat})$$

- o/p switches from  $-V_{\text{ramp}}$  to  $+V_{\text{ramp}}$  in half the time period  $T/2$ .
- Putting the values in basic integrator eqn

$$V_o = - \int dt$$

$$V_o(\text{pp}) = -$$

$$V_o(\text{pp}) =$$

$$T = 2R_1C_1$$

We have

$$V_o(\text{pp}) = (V_{\text{sat}})$$

$$T = 4R_1C_1$$

- Freq of oscn

$$f_0 =$$

PREPARED BY RINJU RAVINDRAN, ADHOC ASST. PROFESSOR-ECE, GCEK

## Q: design a 2KHz Triangular wave generator circuit


### Hint:

- Consider **Op-Amp IC741** with supply voltage  $\pm 12\text{V}$ .  
Let's expect output peak to peak voltage to be 7 volts.
- Assume  $R_2 = 10\text{K ohm}$ , Capacitor  $C = 0.05\mu\text{F}$




Ans:

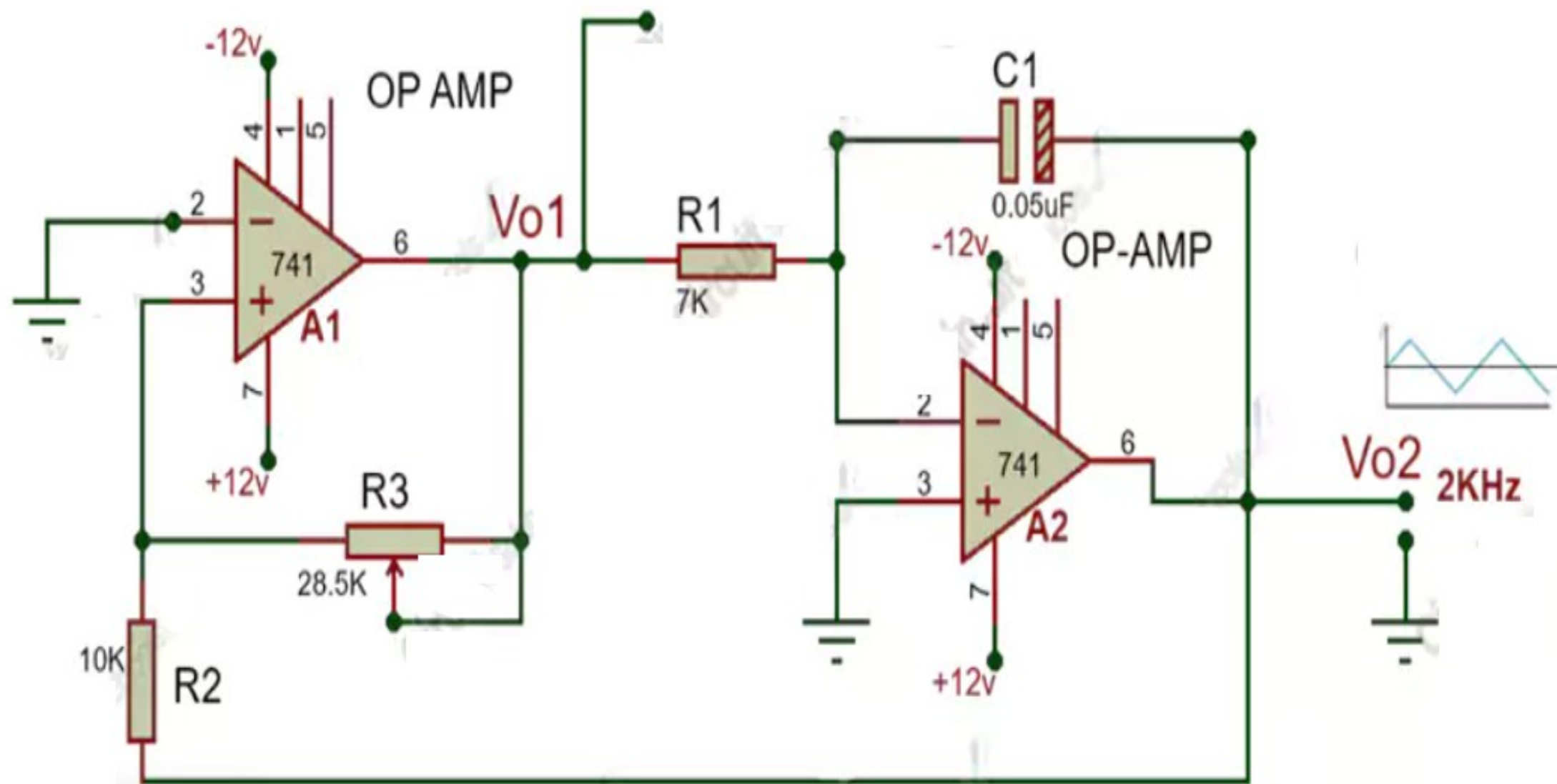- $R3 = 28.5\text{Kohm}$
- $R1 = 7\text{ Kohm}$
- We can use a varistor/potentiometer of  $50\text{k ohm}$  to get the  $R3$  as  $28.5\text{Kohm}$ .
- Draw the ckt with designed values.



# SAWTOOTH WAVEFORM GENERATOR

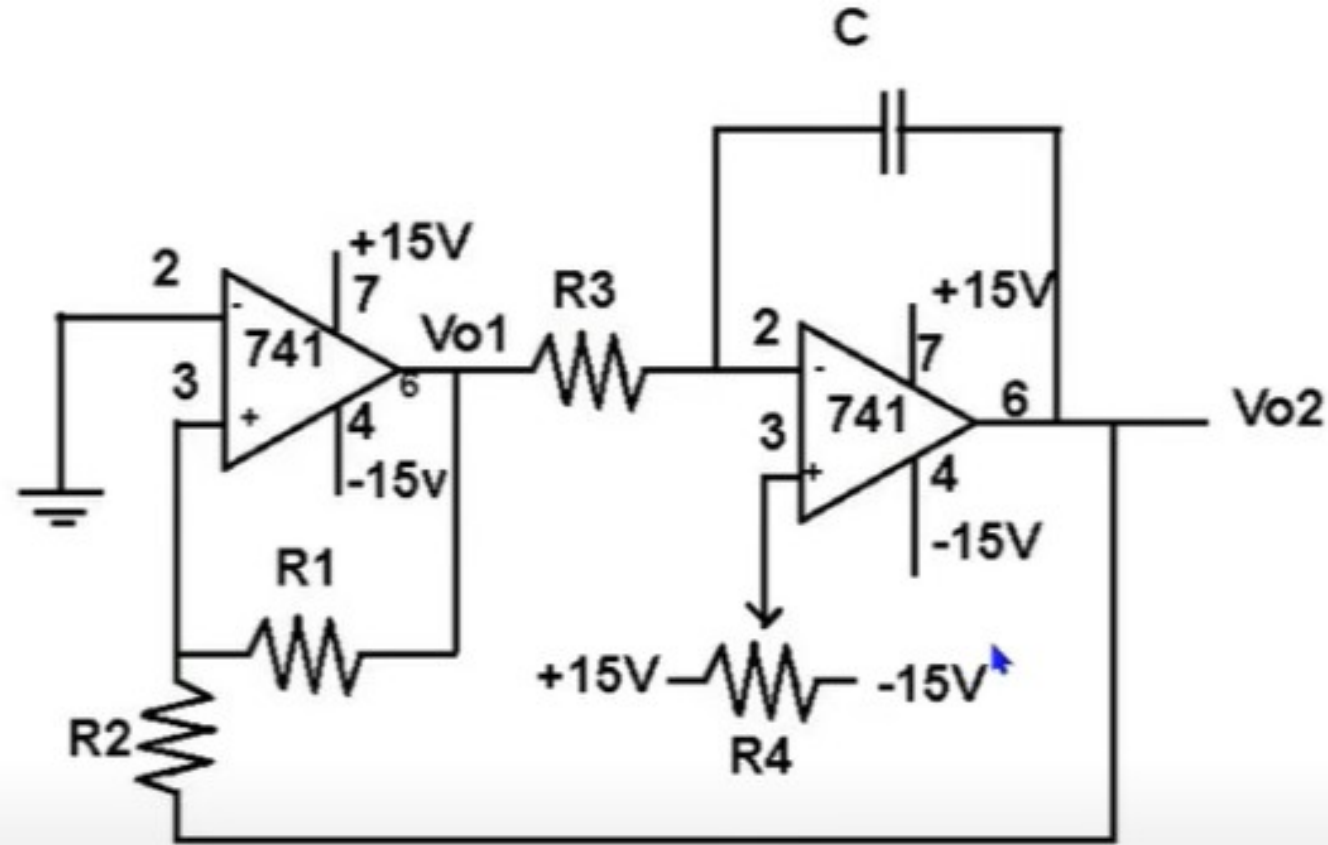

- The sawtooth wave generator is one kind of linear, non-sinusoidal waveform, and the shape of this waveform is a triangular shape in which the fall time and rise time are different.
- The sawtooth waveform can also be named an asymmetric triangular wave.
- The triangular wave generator can be converted in to a sawtooth wave generator by injecting a variable dc voltage into the non-inverting terminal of the integrator.
- A potentiometer is used in this ckt.

- Now the output of integrator is a triangular wave riding on some dc level that is a function of R4 setting.
- The duty cycle of square wave will be determined by the polarity and amplitude of dc level.
- A duty cycle less than 50% will cause output of integrator be a sawtooth.
- With the wiper at the centre of R4, the output of integrator is a triangular wave.
- Use of the potentiometer is when the wiper moves towards  $-V_{EE}$  and  $+V_{CC}$ .

- When the wiper moves toward negative voltage ( $-V$ ); then the rise time becomes more than the fall time.
- When the wiper moves towards positive voltage ( $+V$ ), then the rise time becomes less than the fall time.
- Freq of sawtooth wave decreases as  $R_4$  is adjusted towards  $+V_{CC}$  or  $-V_{EE}$ .
- However amp of sawtooth is independent of  $R_4$  settings.

Fig: Output of sawtooth wave generator when noninverting of integrator is at some negative dc level.

