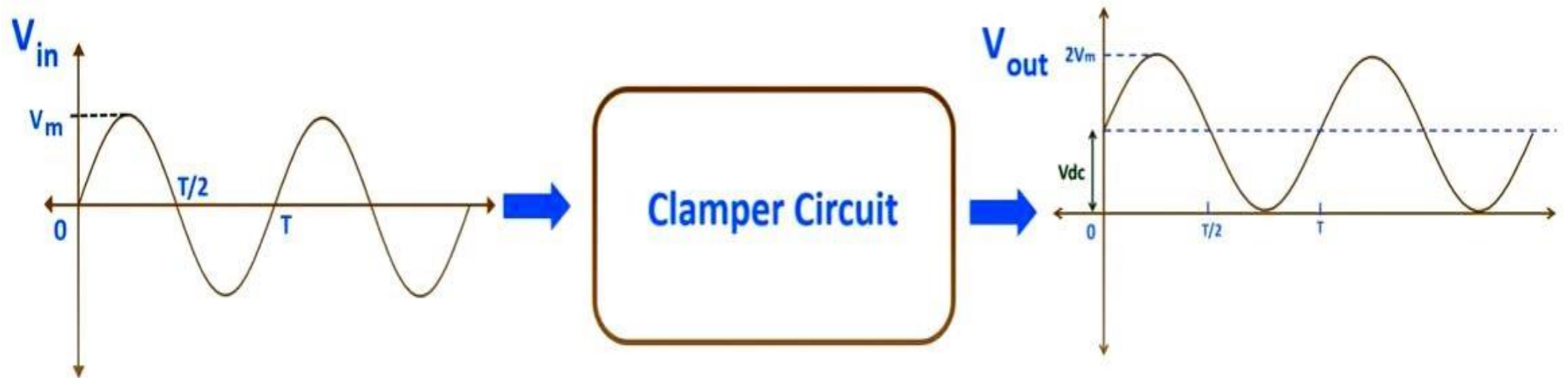


CLAMPER CIRCUIT

- A Clamper circuit is a circuit that shifts the waveform to a desired DC level without changing the actual appearance of the applied signal.
- consists of a diode, a resistor and a capacitor
- Clamper circuits consist of energy storage elements like capacitors
- Clamper circuit changes the DC level of the signal to the desired level without changing the shape of the signal. (**DC Restorers**)




CLAMPER CIRCUIT - CLASSIFICATION

- POSITIVE CLAMPER
- NEGATIVE CLAMPER
- BIASED CLAMPER


POSITIVE CLAMPER

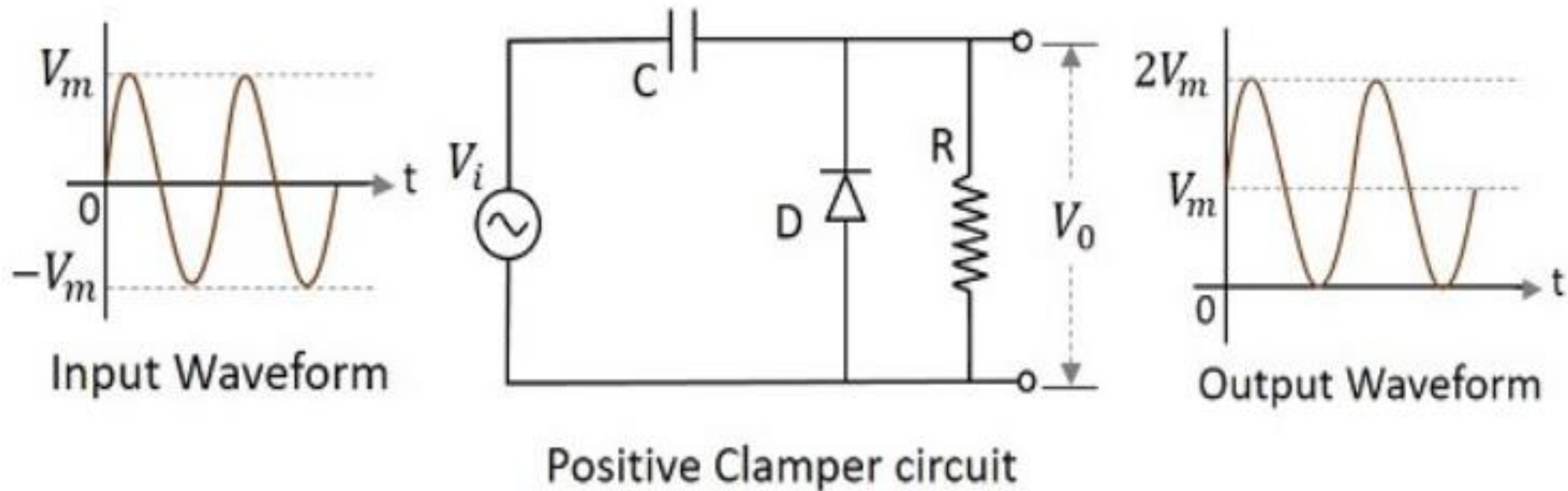- A Clamper circuit that shifts the input waveform **above** the input DC reference level or voltage



NEGATIVE CLAMPER

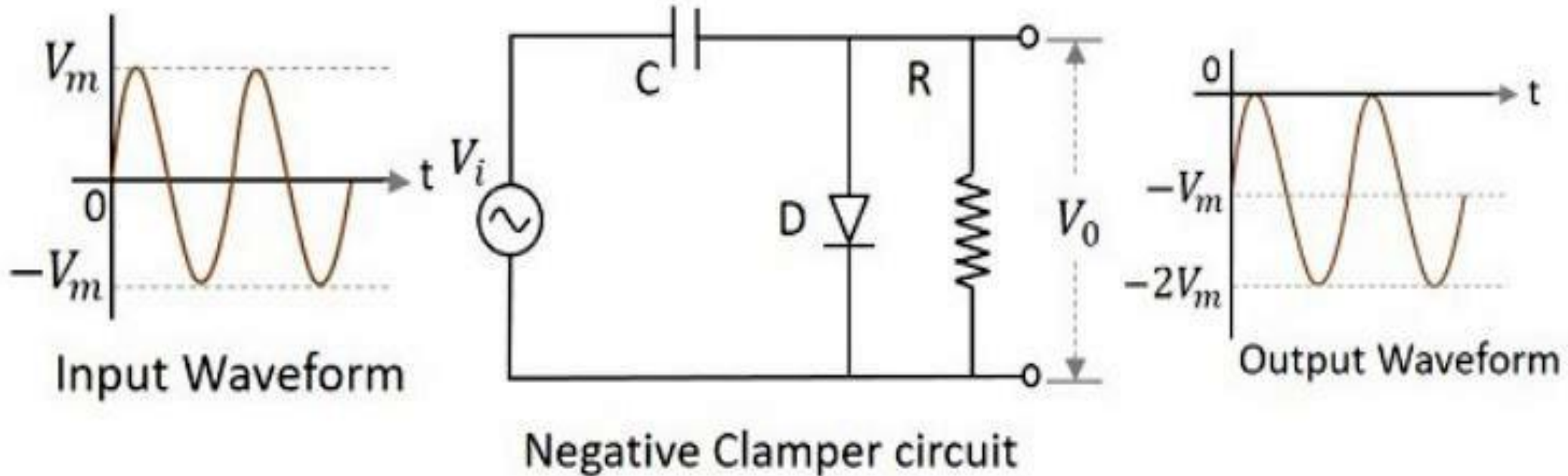
- A Clamper circuit that shifts the input waveform **below** the input DC reference level or voltage



BIASED CLAMPER

- Positive or Negative Clamper circuit with a Biased Voltage.
- contains Diode, Resistor, Capacitor with a Biased Voltage source.
- Biased clampers are divided into
 - Biased Positive Clamper with Positive Bias
 - Biased Positive Clamper with Negative Bias
 - Biased Negative Clamper with Positive Bias
 - Biased Negative Clamper with Negative Bias

NEGATIVE CLAMPER

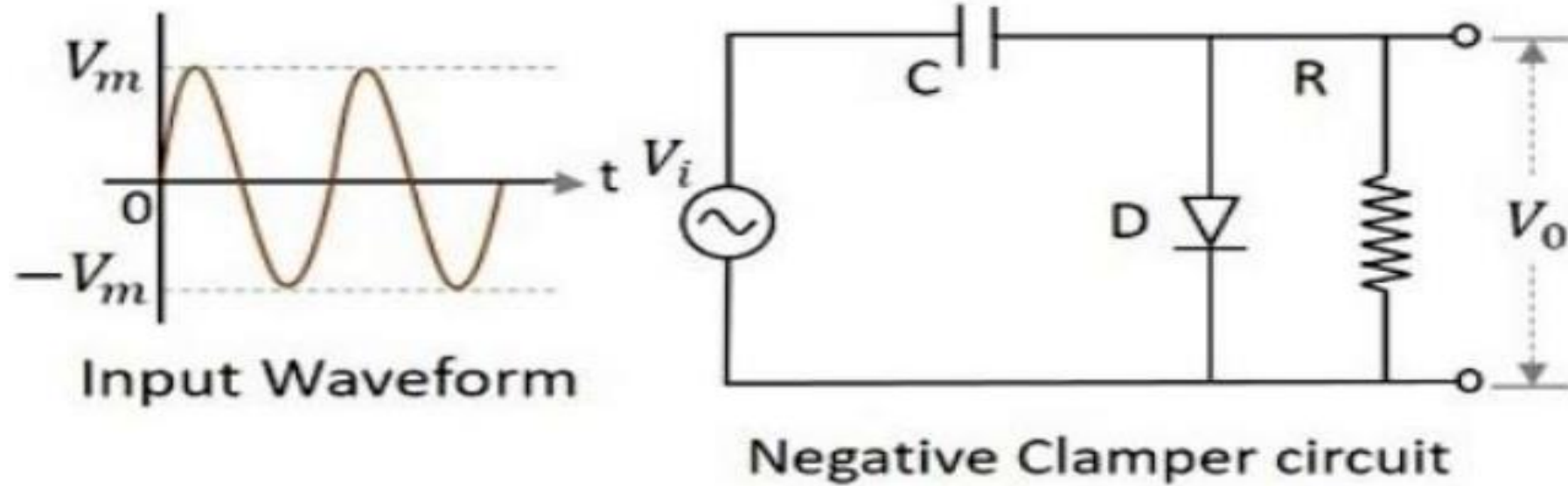


- Assume Diode is Ideal
- Time Constant (RC) very much larger than input Time period



NEGATIVE CLAMPER

POSITIVE HALF CYCLE

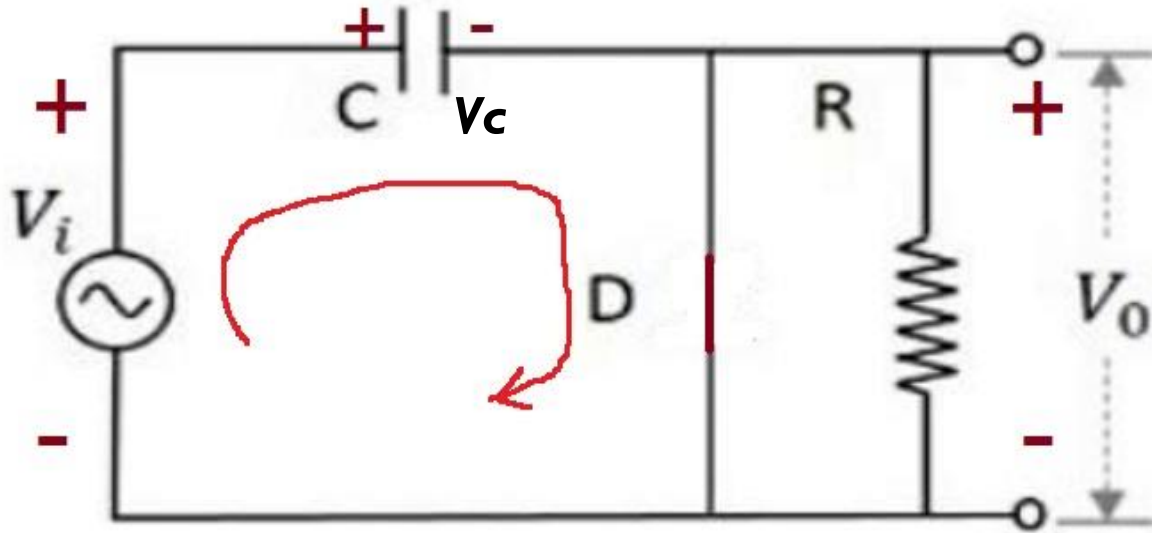

- Diode FB, Short Circuited
- No voltage across output
- Capacitor Charges to V_m voltage.

From Circuit

$$V_o = \mathbf{0}$$

From KVL

$$V_i - V_c = 0$$

$$V_c = V_i = V_m$$

NEGATIVE CLAMPER


POSITIVE HALF CYCLE

- During the positive half cycle of the input AC signal, the diode is forward biased and hence no signal appears at the output.
- In forward biased condition, the diode allows electric current through it. This current will flow to the capacitor & charges it to the peak value of input voltage in inverse polarity $-V_m$
- As input current or voltage decreases after attaining its maximum value V_m , the capacitor holds the charge until the diode remains forward biased.



NEGATIVE CLAMPER

NEGATIVE HALF CYCLE

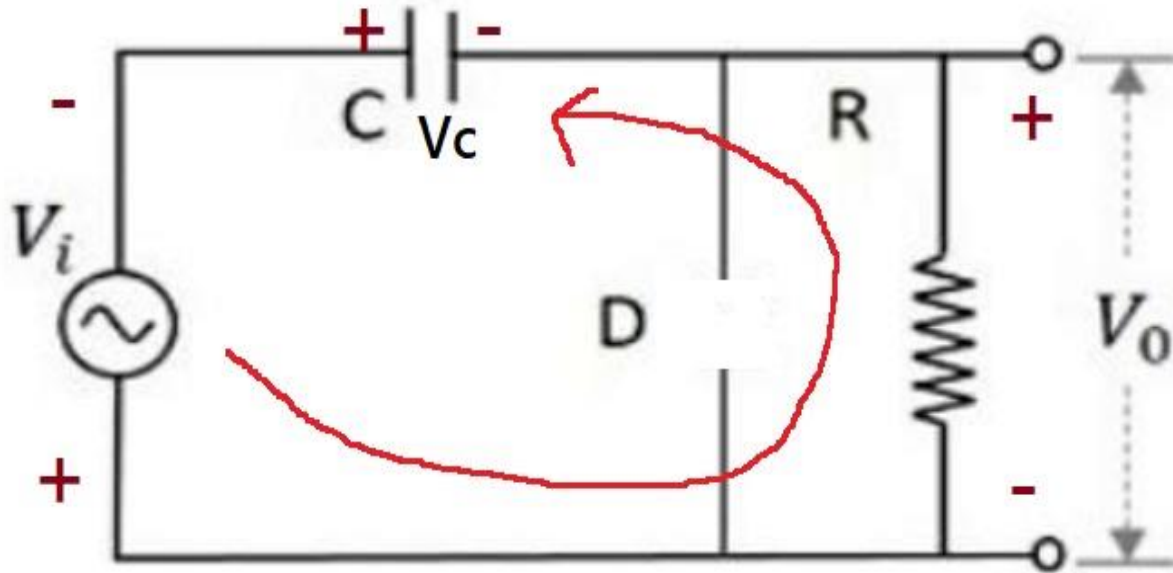

- Diode RB, Open Circuited
- Capacitor Discharges V_m voltage across the resistor
- voltage across output is $-2V_m$

We know

$$V_c = V_i = V_m$$

From KVL

$$V_i + V_o + V_c = 0$$

$$V_o = -V_i - V_c = \mathbf{-2V_m}$$


NEGATIVE CLAMPER

NEGATIVE HALF CYCLE


- During the negative half cycle of the input AC signal, the diode is reverse biased and hence the signal appears at the output.
- In reverse biased condition, the diode does not allow electric current through it. So the input current directly flows towards the output.
- When the negative half cycle begins, the diode is in the non-conducting state and the charge stored in the capacitor is discharged (released).
- Therefore, the voltage appeared at the output is equal to the sum of the voltage stored in the capacitor ($-V_m$) and the input voltage ($-V_m$) {i.e. $V_o = -V_m - V_m = -2V_m$ }
- As a result, the signal shifted downwards.




NEGATIVE CLAMPER

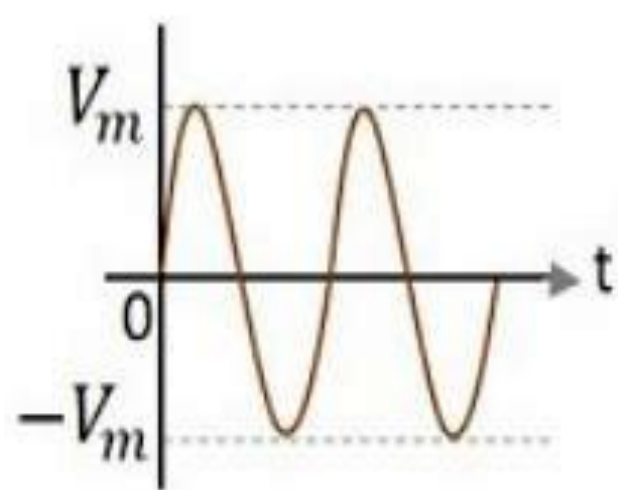

Input Waveform

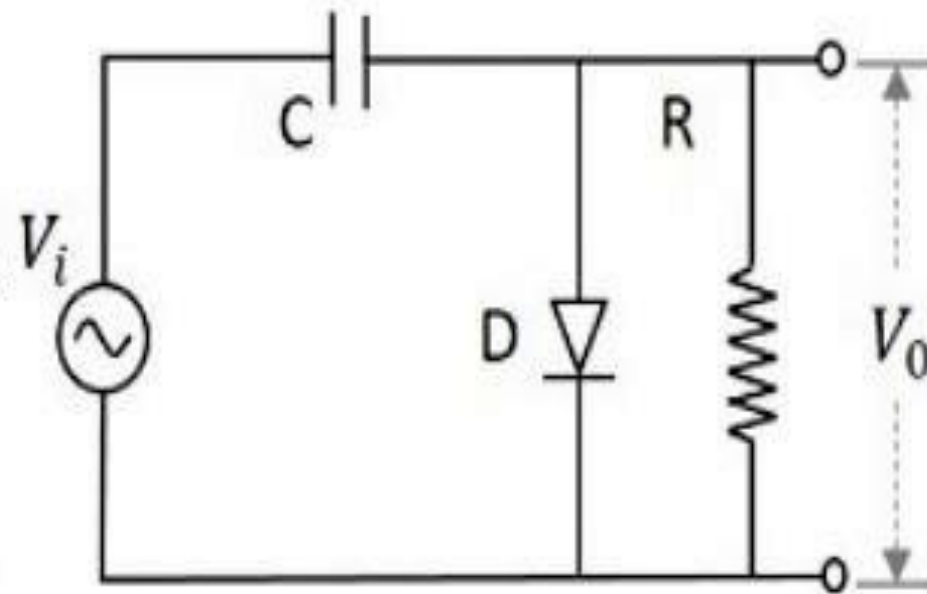


Negative Clamper circuit

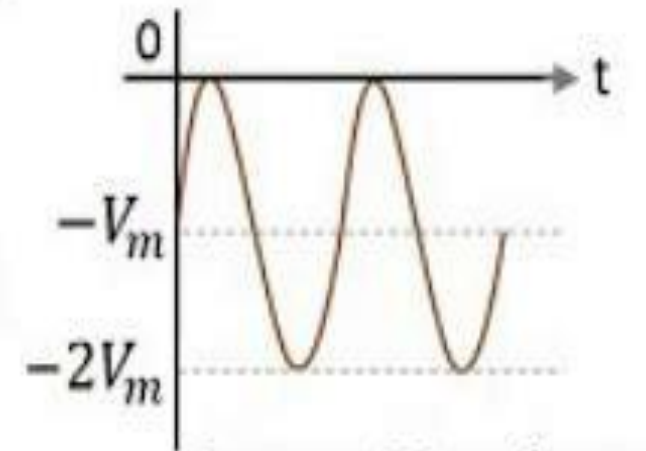


Output Waveform

NEGATIVE CLAMPER

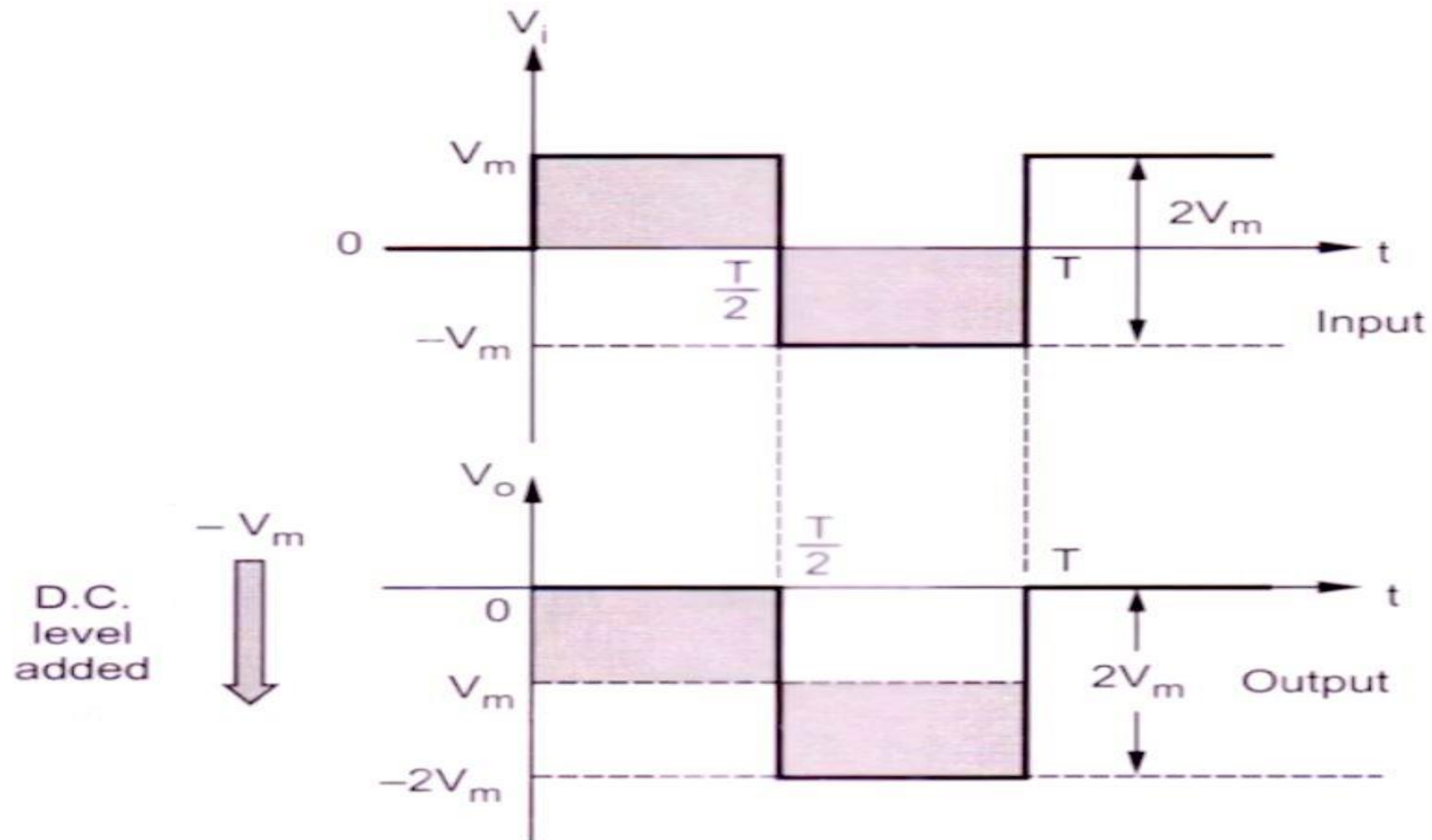

POSITIVE CLAMPER

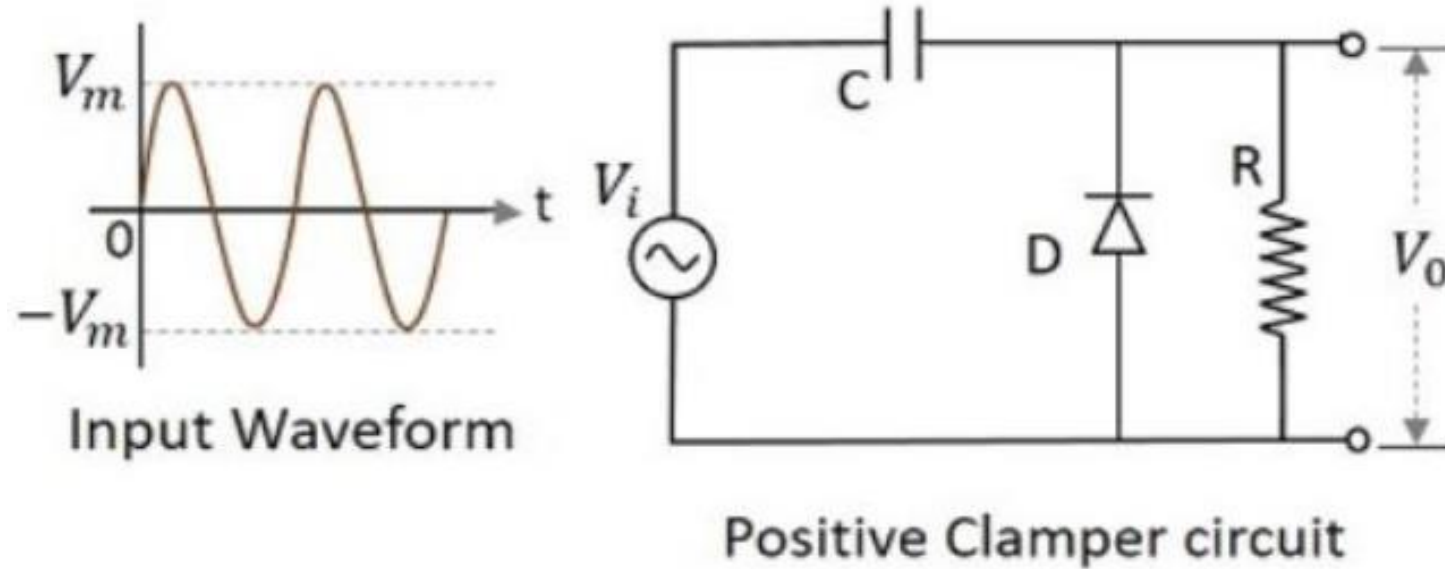


- Assume Diode is Ideal
- Time Constant (RC) very much larger than input Time period



POSITIVE CLAMPER

NEGATIVE HALF CYCLE

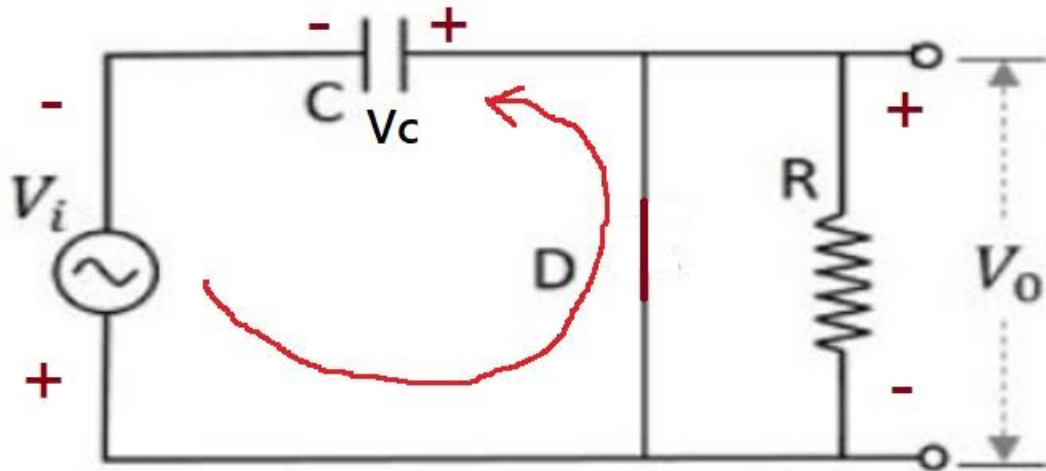

- Diode FB, Short Circuited
- No voltage across output
- Capacitor Charges to V_m voltage.

From Circuit

$$V_o = \mathbf{0}$$

From KVL

$$V_i - V_c = 0$$

$$V_c = V_i = V_m$$

POSITIVE CLAMPER


NEGATIVE HALF CYCLE

- During the negative half cycle of the input AC signal, the diode is forward biased and hence no signal appears at the output.
- In forward biased condition, the diode allows electric current through it. This current will flow to the capacitor and charges it to the peak value of input voltage V_m .
- The capacitor charged in inverse polarity (positive) with the input voltage.
- As input current or voltage decreases after attaining its maximum value $-V_m$, the capacitor holds the charge until the diode remains forward biased.



POSITIVE CLAMPER

POSITIVE HALF CYCLE

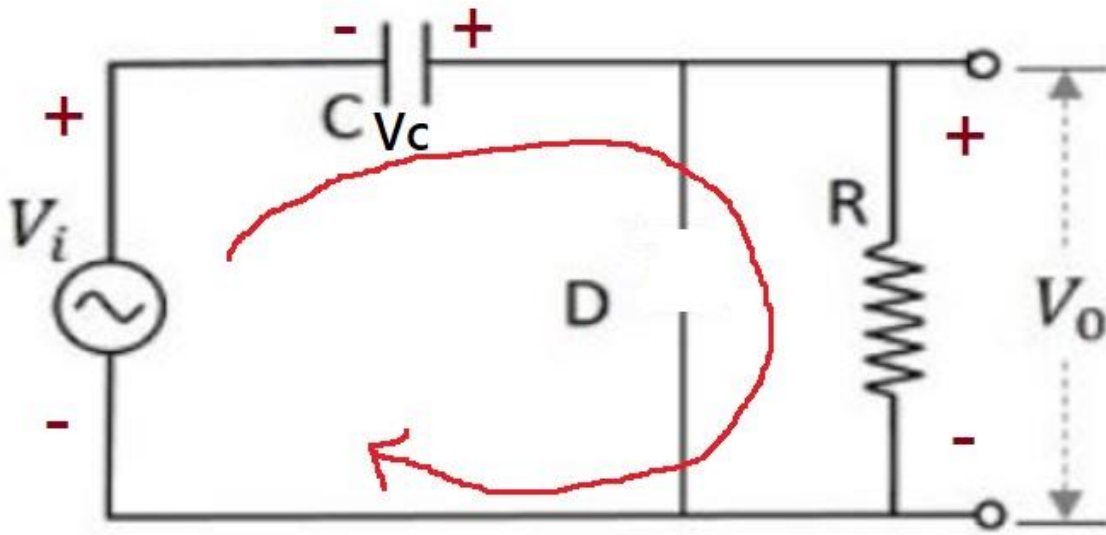

- Diode RB, Open Circuited
- Capacitor Discharges V_m voltage across the resistor
- voltage across output is $+2V_m$

We know

$$V_c = V_i = V_m$$

From KVL

$$V_i + V_c - V_o = 0$$

$$V_o = V_i + V_c = \mathbf{2V_m}$$


POSITIVE CLAMPER

POSITIVE HALF CYCLE

- During the positive half cycle of the input AC signal, the diode is reverse biased and hence the signal appears at the output.
- In reverse biased condition, the diode does not allow electric current through it. So the input current directly flows towards the output.
- When the positive half cycle begins, the diode is in the non-conducting state and the charge stored in the capacitor is discharged (released).
- Therefore, the voltage appeared at the output is equal to the sum of the voltage stored in the capacitor (V_m) and the input voltage (V_m) { i.e. $V_o = V_m + V_m = 2V_m$ }
- As a result, the signal shifted upwards.





POSITIVE CLAMPER

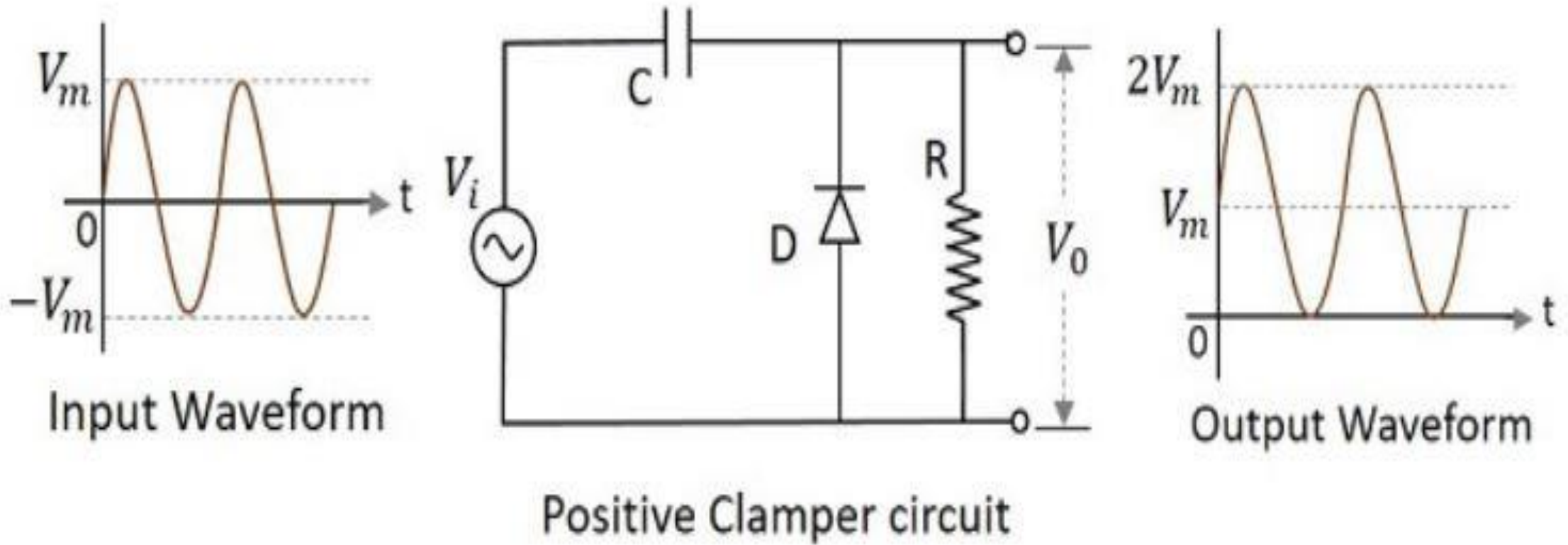



BIASED CLAMPER CIRCUITS

- BIASED POSITIVE CLAMPER WITH POSITIVE BIAS
- BIASED POSITIVE CLAMPER WITH NEGATIVE BIAS
- BIASED NEGATIVE CLAMPER WITH POSITIVE BIAS
- BIASED NEGATIVE CLAMPER WITH NEGATIVE BIAS

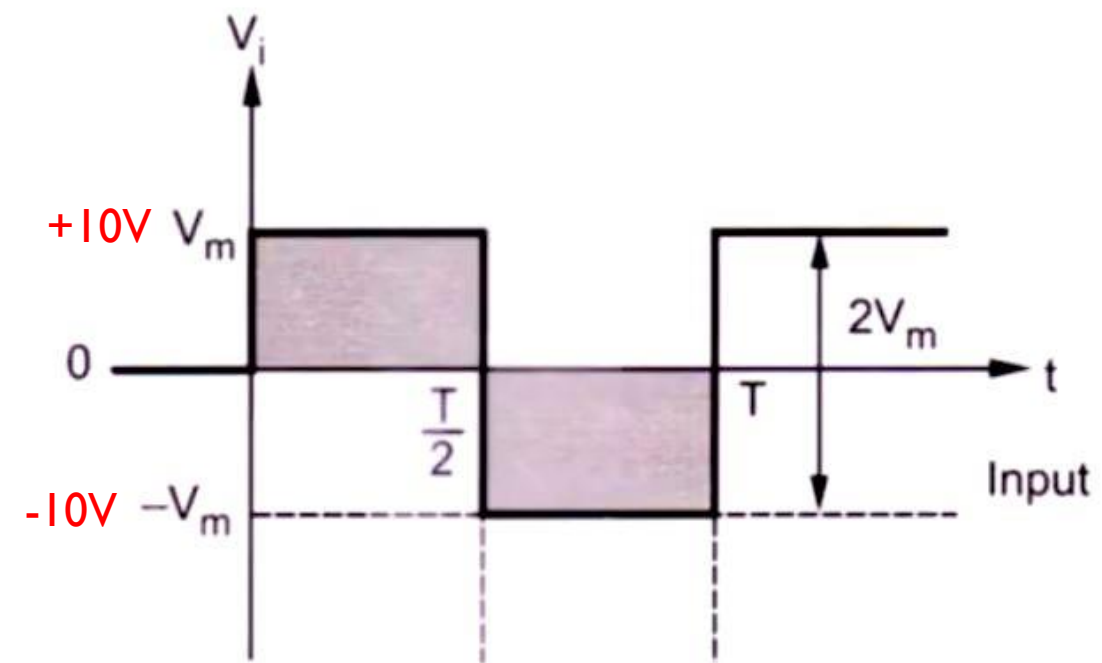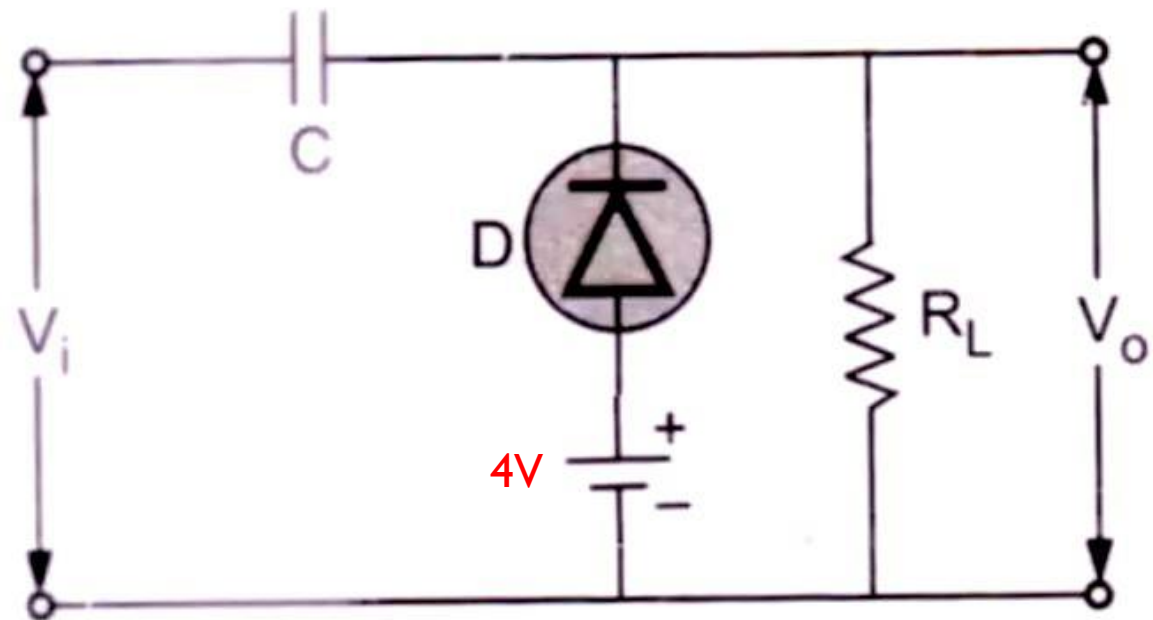BIASED POSITIVE CLAMPER (POSITIVE BIASED)



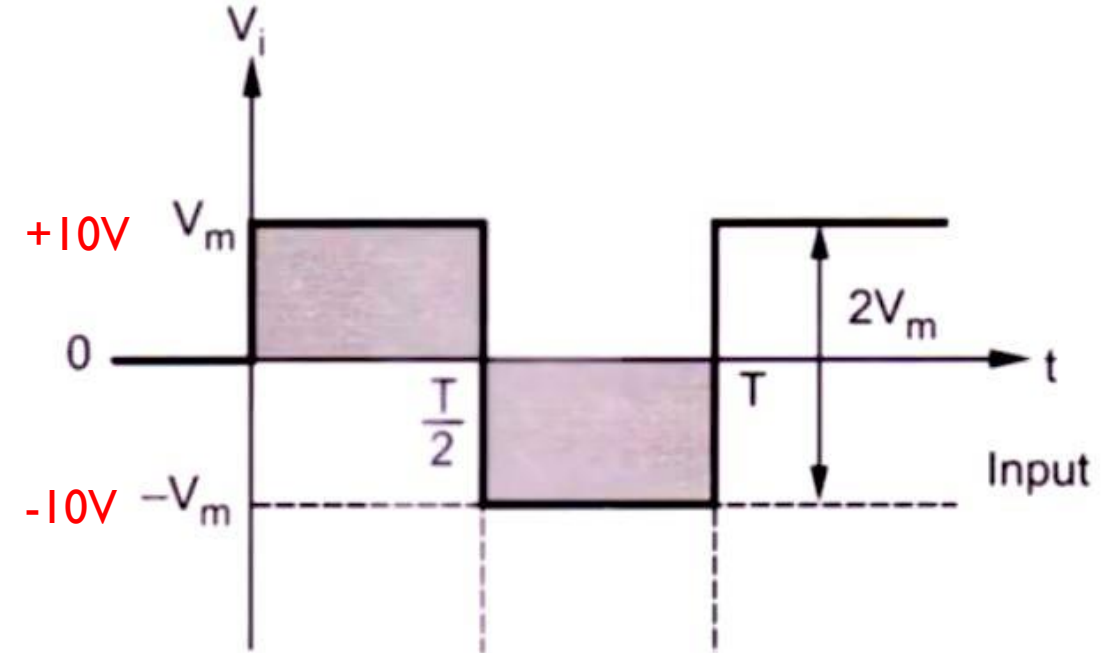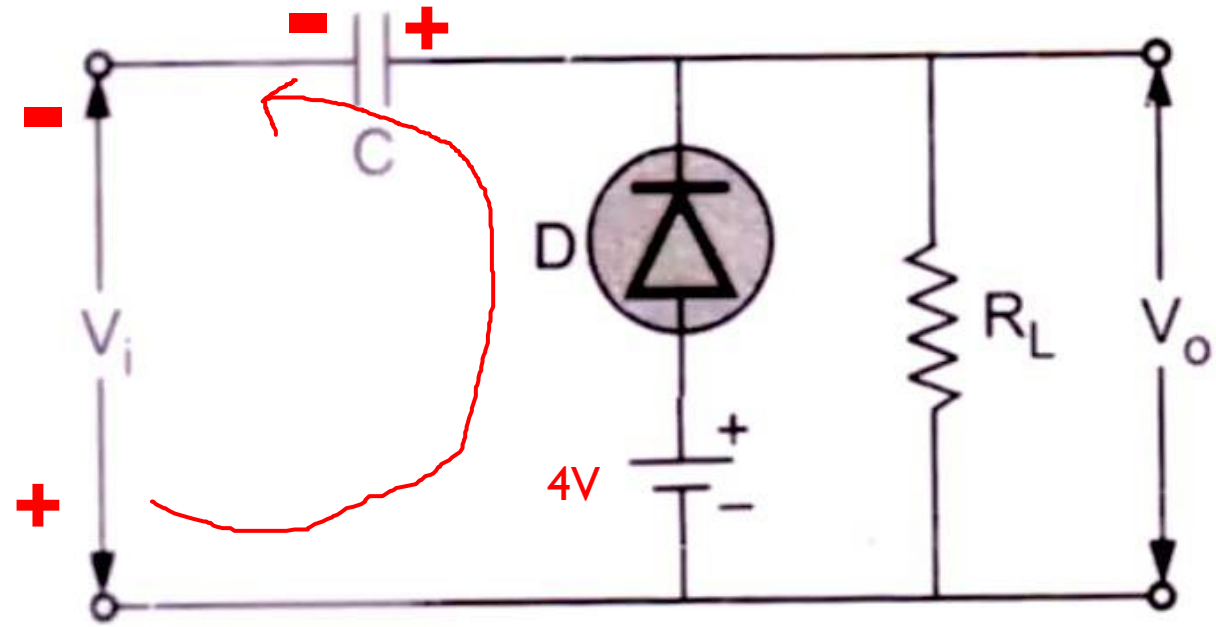BIASED POSITIVE CLAMPER (POSITIVE BIASED)



-ve Half Cycle

0 to -10V ■ Diode FB ■ $V_o = +4V$


KVL:

$$V_i + 4V - V_c = 0$$

$$V_c = V_i + 4V = 10 + 4V = 14V$$

- In Complete Negative Half Cycle Diode will be Forward Biased.
- Output Voltage will be +4V.
- Capacitor charges to $V_m + 4V$

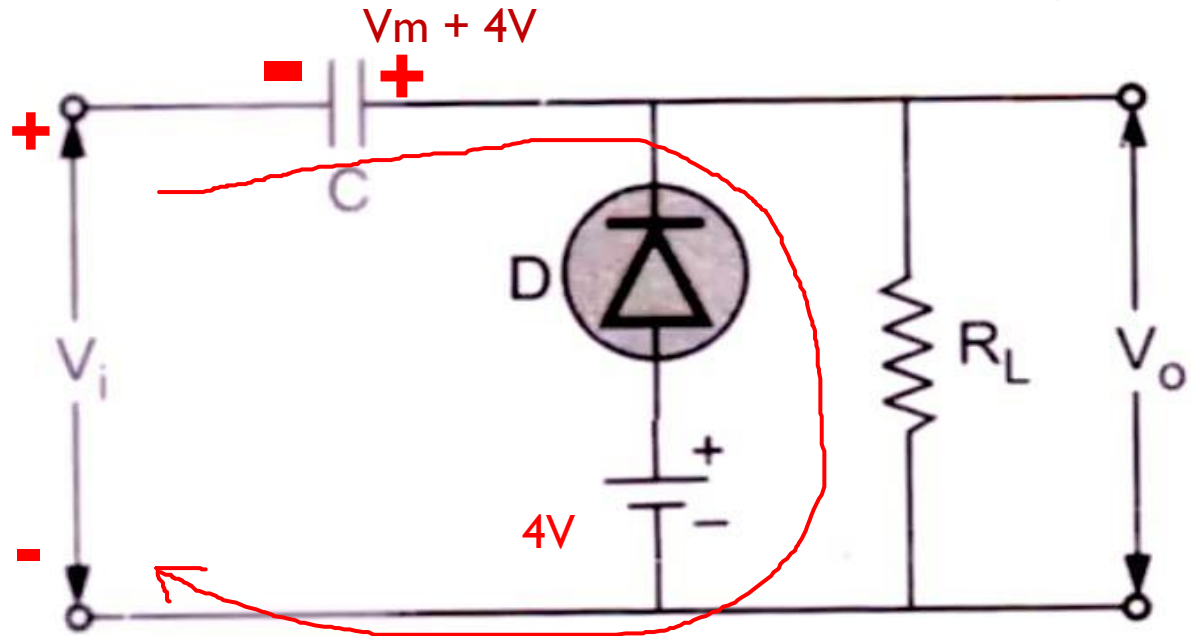BIASED POSITIVE CLAMPER (POSITIVE BIASED)



+ve Half Cycle


0 to +4V | Diode FB |

+4V to +10V | Diode RB |

KVL:


$$V_i + V_c - V_o = 0 ; V_o = V_i + V_c$$
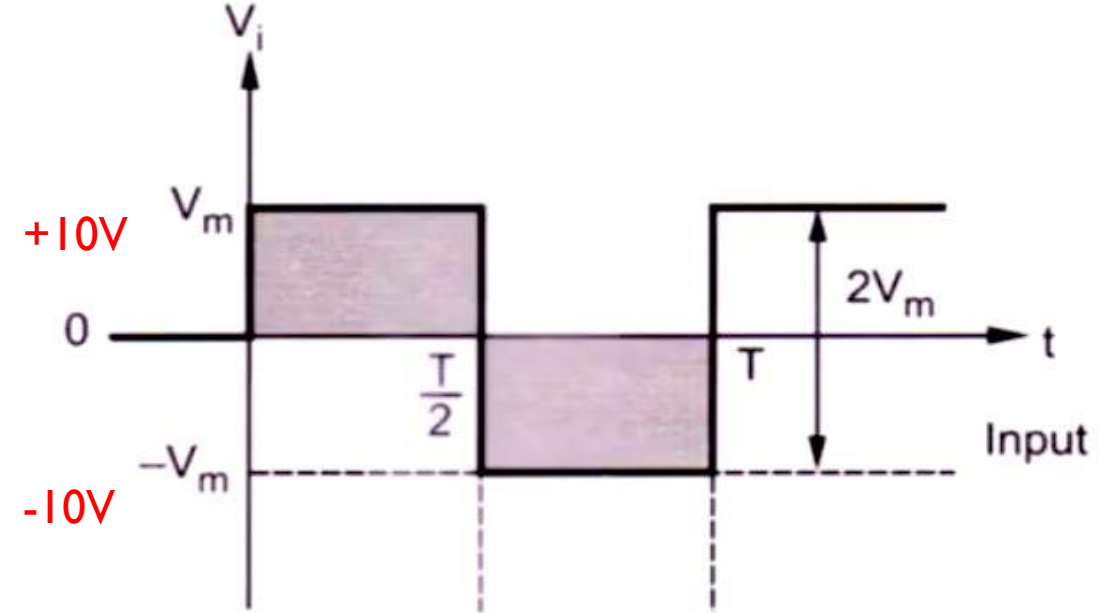
$$V_o = V_m + V_m + 4V = 10 + 10V + 4V = 24V$$



- Diode FB till +4V, Diode RB from +4V to +10V
- When Diode RB, capacitor discharges already charged $V_m + 4V$.
- Output Voltage will be $2V_m + 4V = 24V$

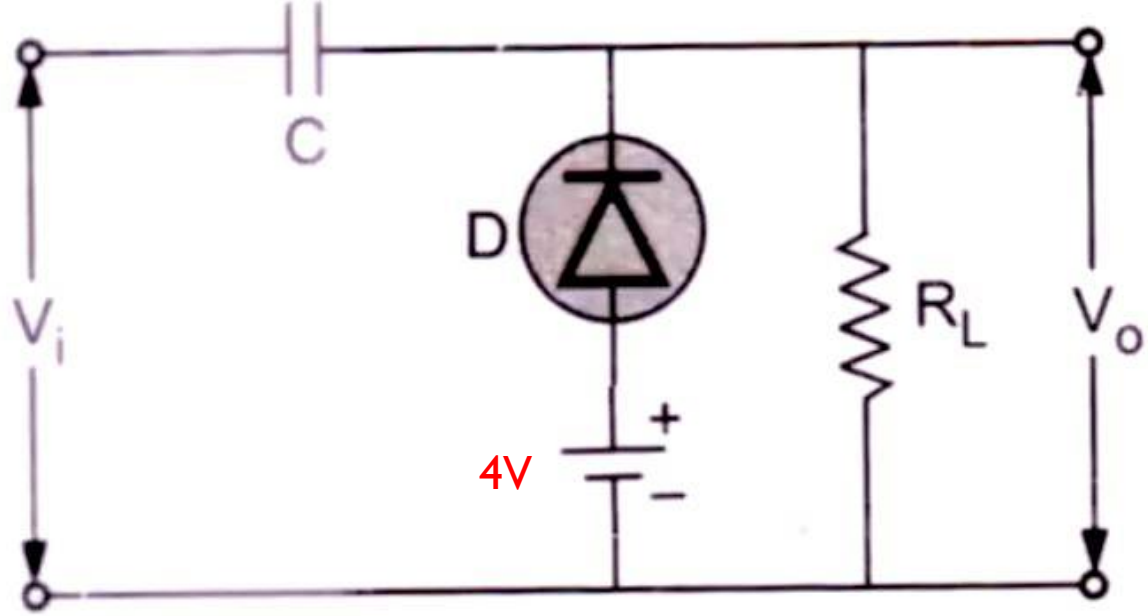BIASED POSITIVE CLAMPER (POSITIVE BIASED)




+ve Half Cycle

$$V_o = V_i + V_c + \text{Battery Voltage}$$

$$V_o = V_m + V_m + (+4V)$$

$$V_o = 10 + 10 + 4 = 24V$$

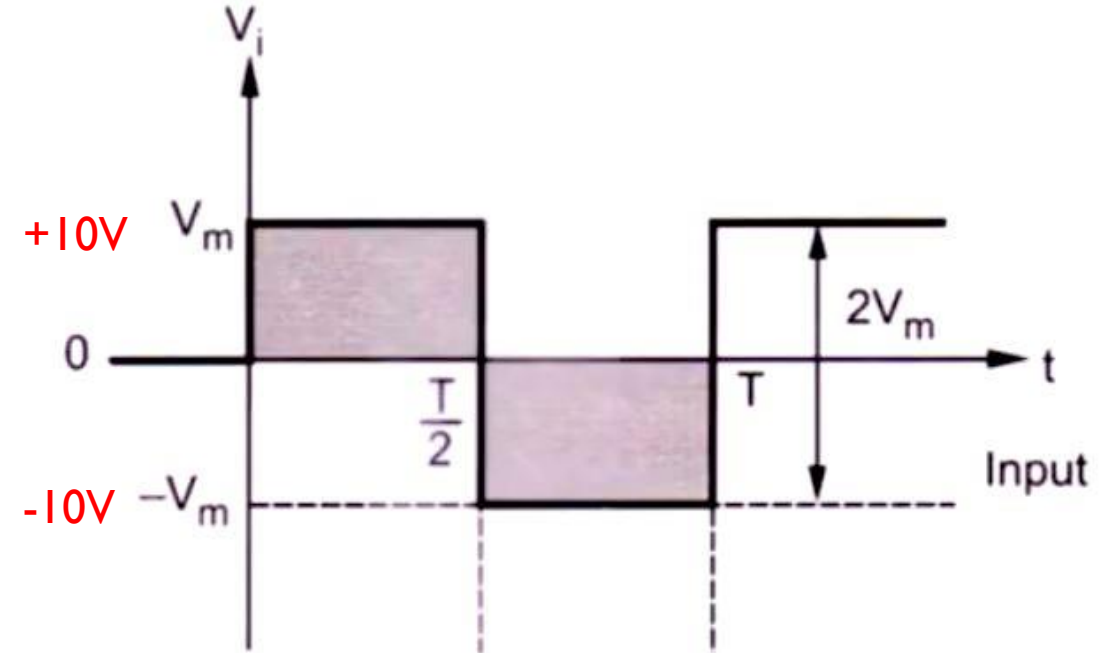



-ve Half Cycle

$$V_o = 0 + \text{Battery Voltage}$$



$$V_o = 0 + (+4V)$$

$$V_o = 0 + 4 = 4V$$

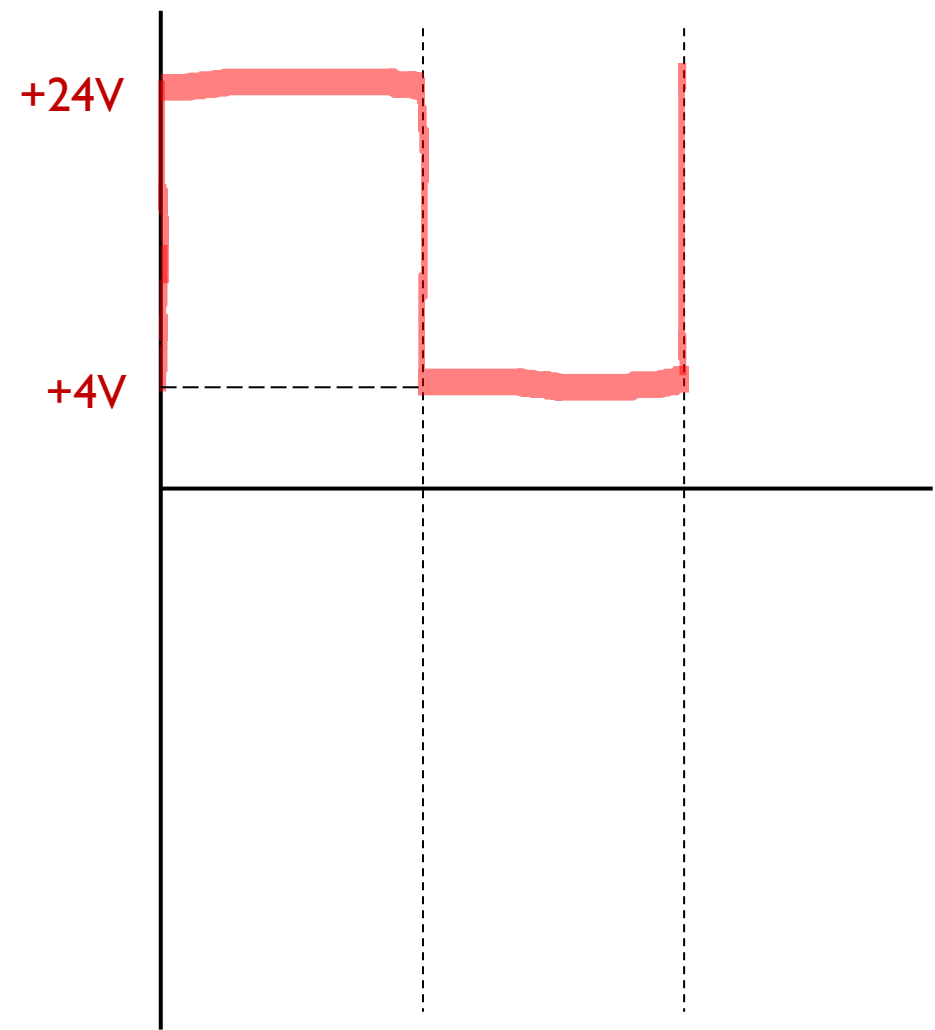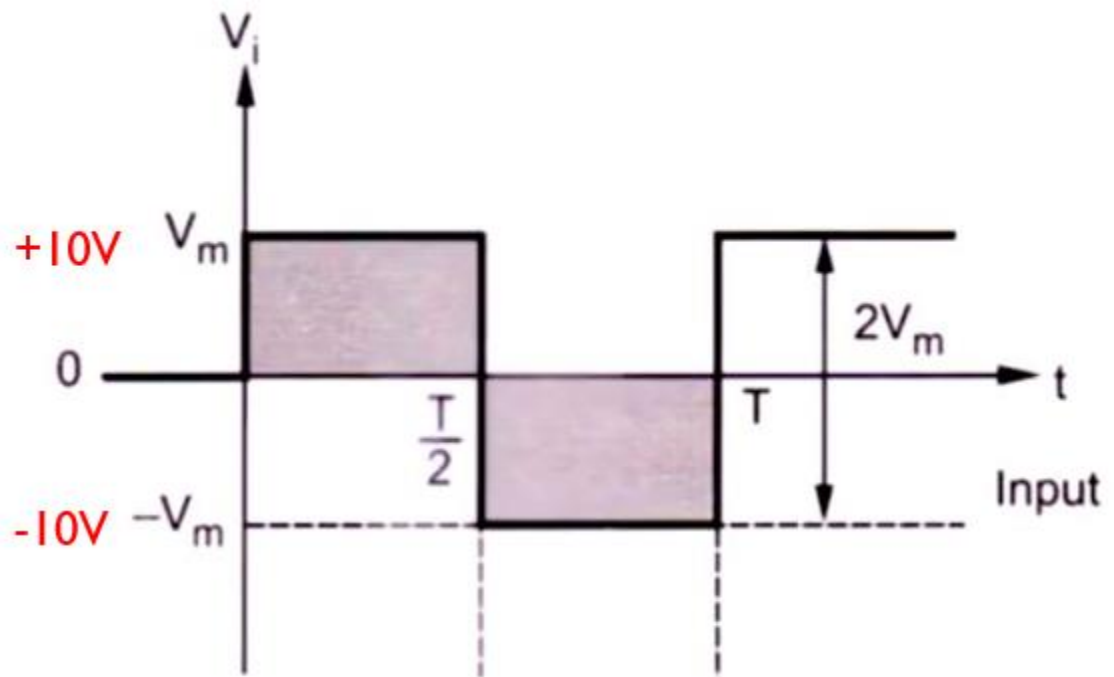
BIASED POSITIVE CLAMPER (POSITIVE BIASED)



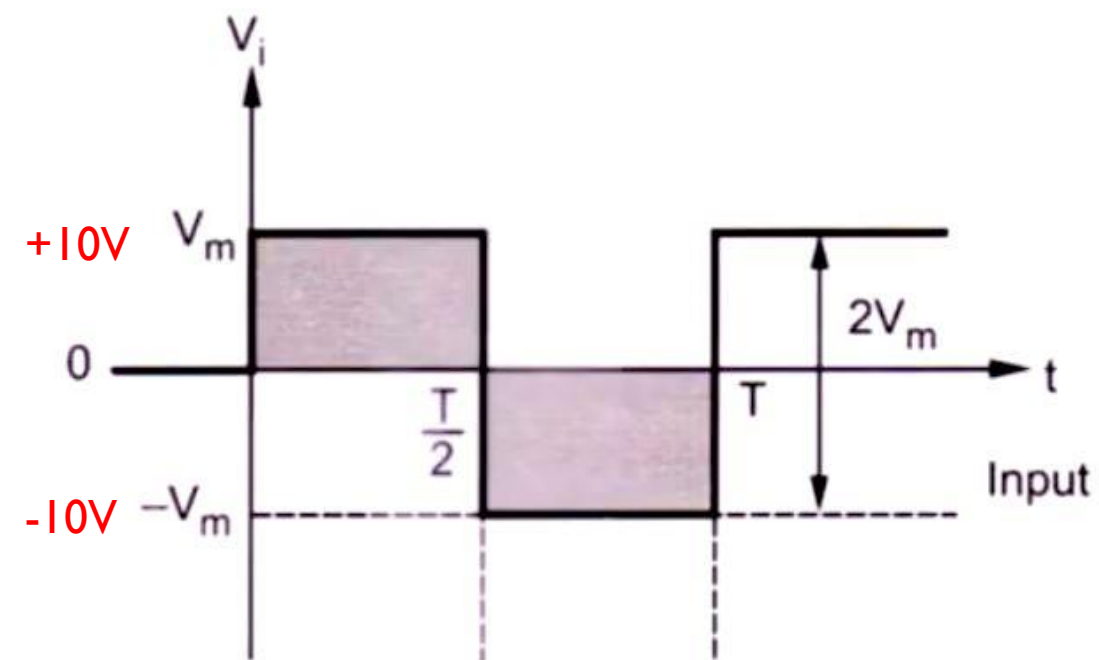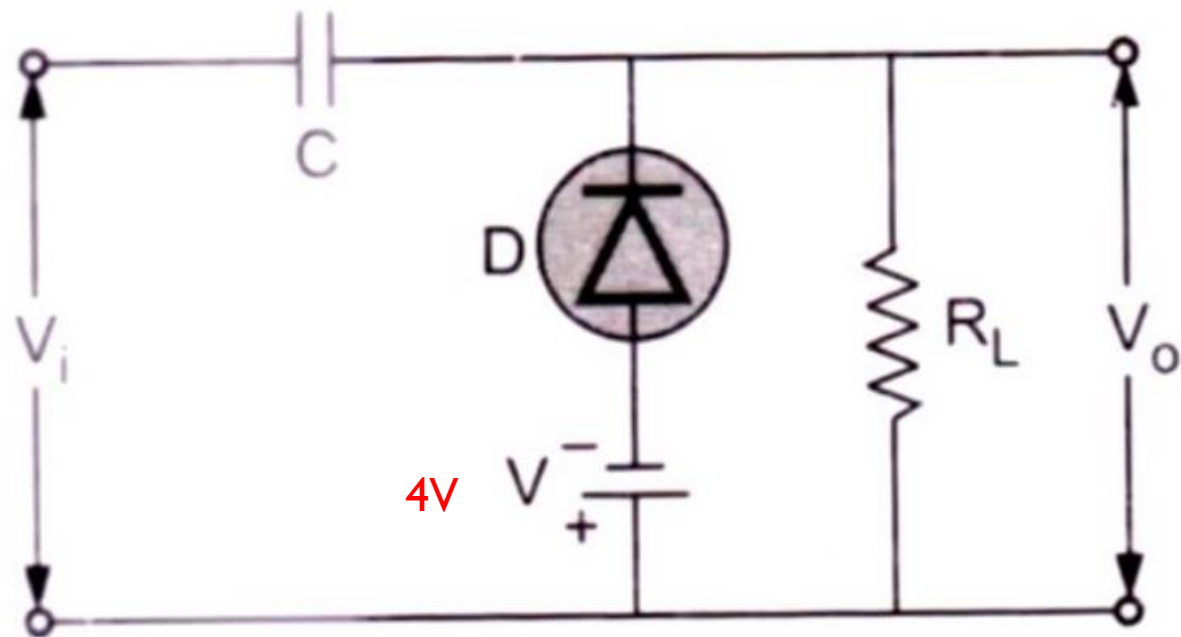BIASED POSITIVE CLAMPER (NEGATIVE BIASED)



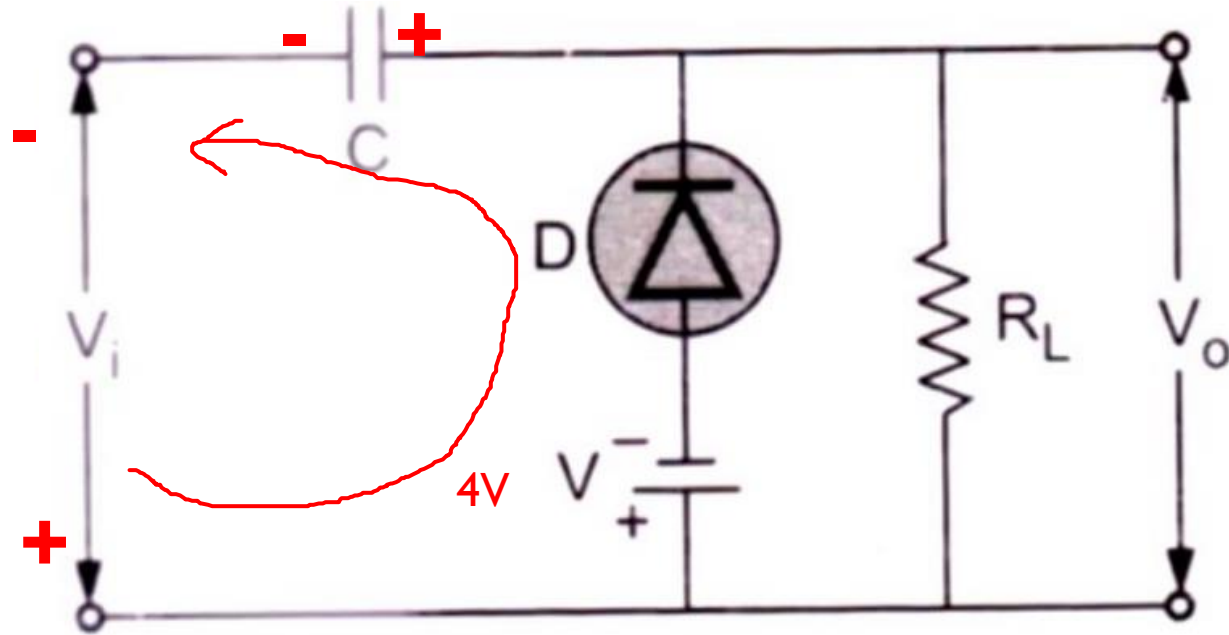BIASED POSITIVE CLAMPER (NEGATIVE BIASED)



-ve Half Cycle


0 to -4V ■ Diode RB ■ $V_o = -4V$

-4V to -10V ■ Diode FB ■

KVL:


$$V_i - 4V - V_c = 0$$

$$V_c = V_i - 4V = 10 - 4V = 6V$$

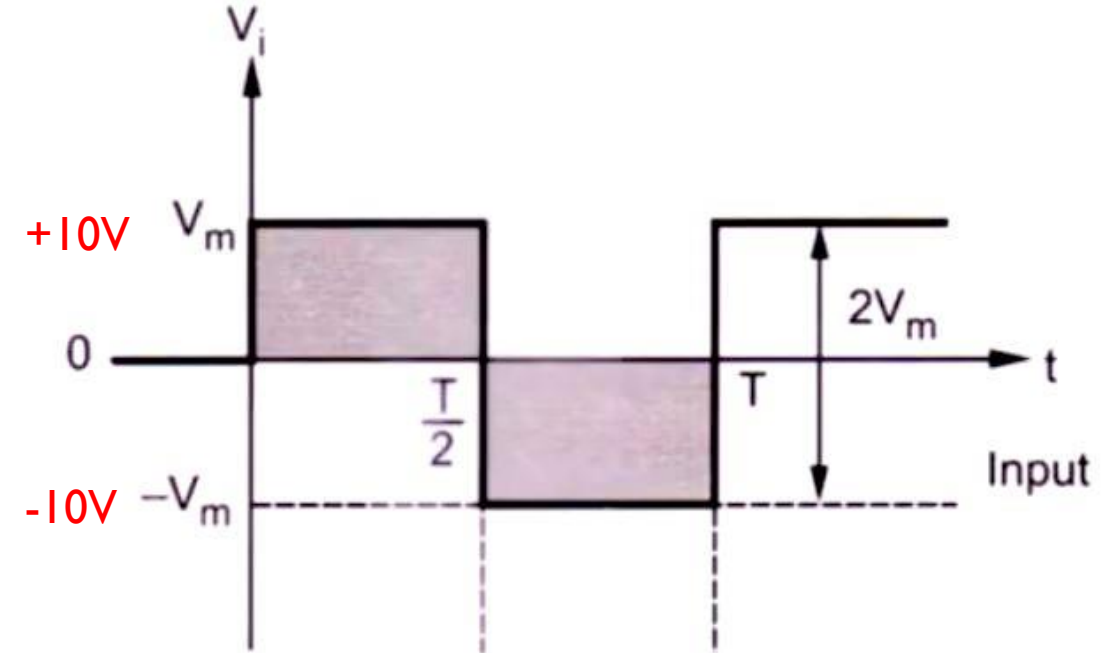

- Diode RB till -4V, Diode FB from -4V to -10V
- When Diode FB, capacitor charges to $V_m - 4V$.
- Output Voltage will be -4V

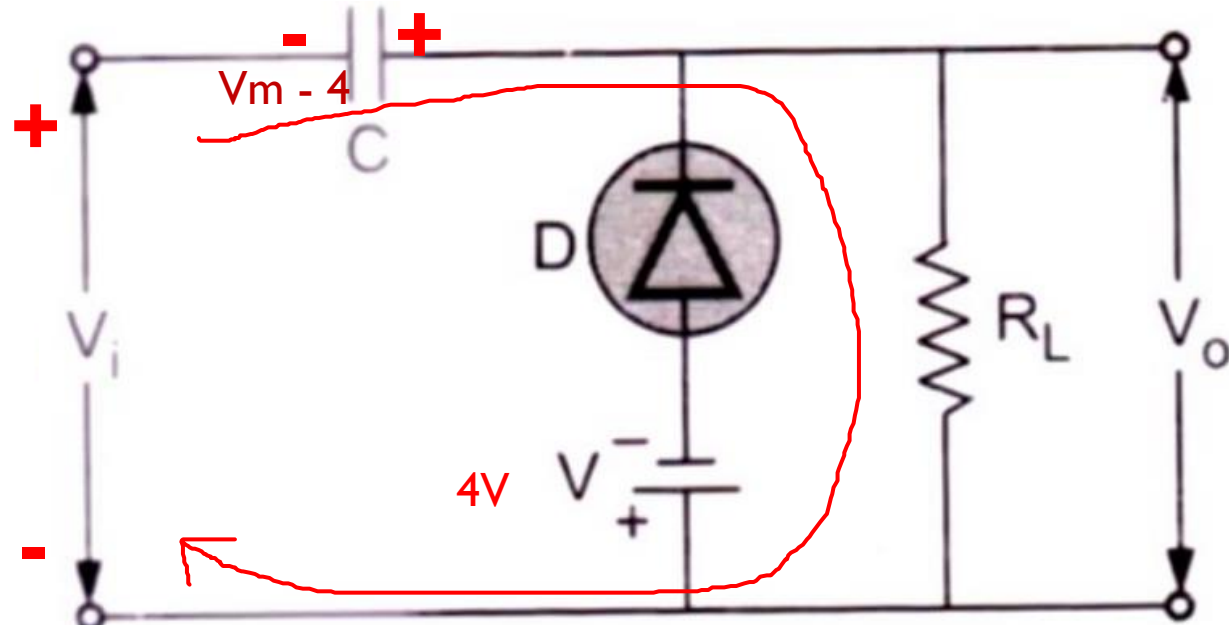BIASED POSITIVE CLAMPER (NEGATIVE BIASED)



+ve Half Cycle


0 to +10V ■ Diode RB ■

KVL:

$$V_i + V_C - V_o = 0$$


$$V_o = V_i + V_C$$
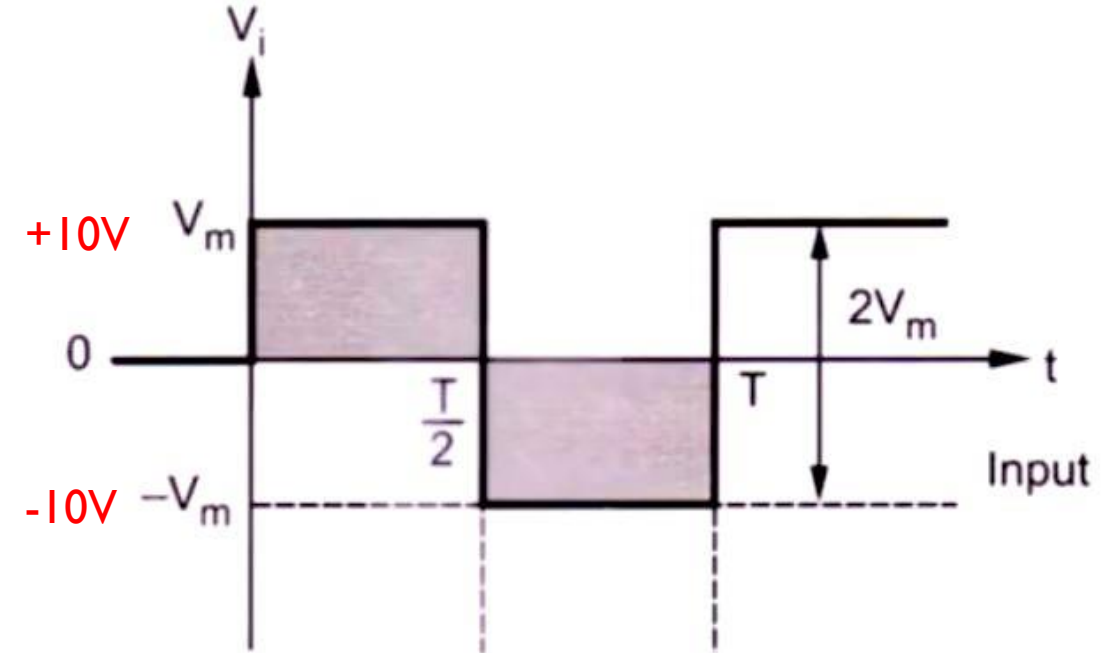
$$V_o = V_m + V_m - 4V = 10 + 10 - 4 = 16V$$



- In Complete Positive Half Cycle Diode will be Reverse Biased.
- When Diode RB, capacitor discharges already charged $V_m - 4V$.
- Output Voltage is $2V_m - 4V = 16V$

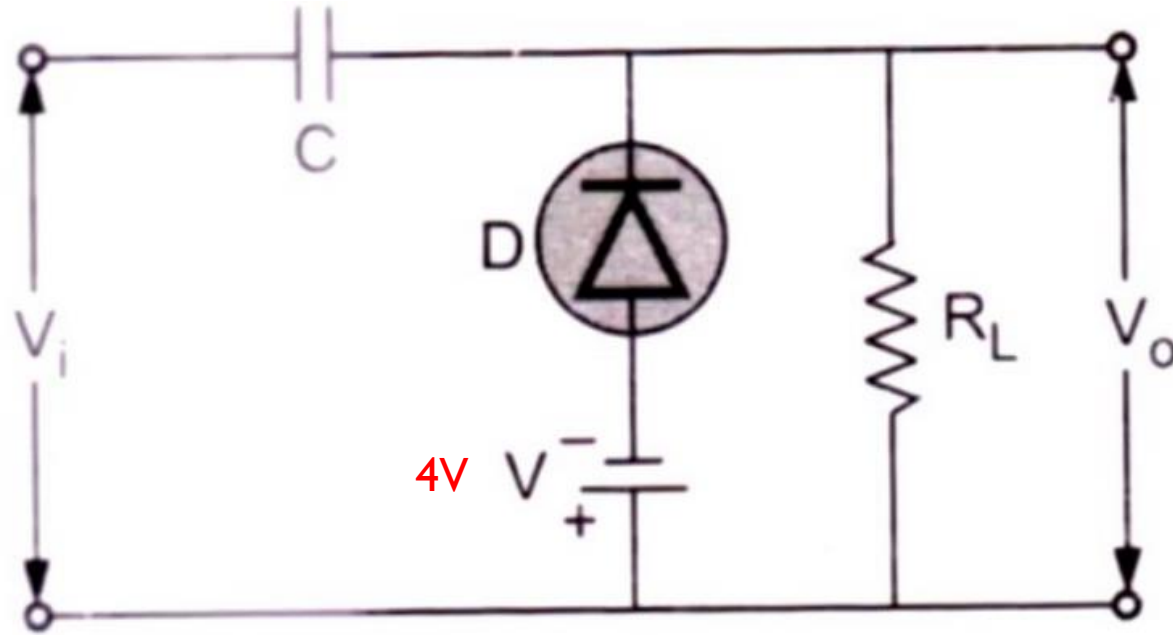BIASED POSITIVE CLAMPER (NEGATIVE BIASED)




+ve Half Cycle

$$V_o = V_i + V_c + \text{Battery Voltage}$$

$$V_o = V_m + V_m + (-4V)$$

$$V_o = 10 + 10 - 4 = 16V$$

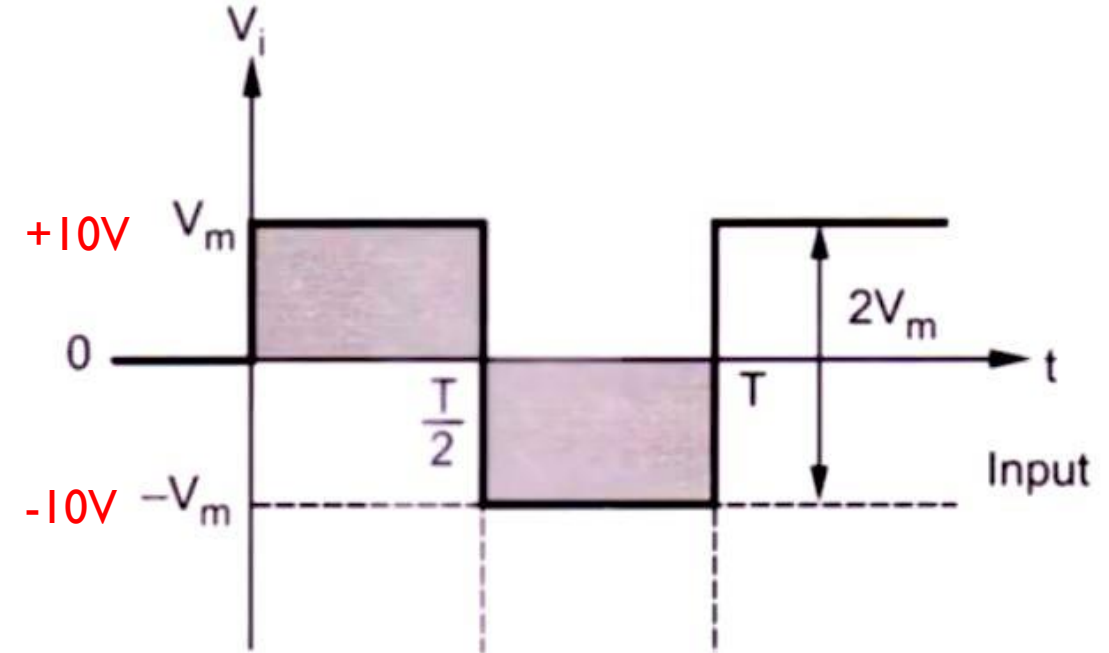



-ve Half Cycle

$$V_o = 0 + \text{Battery Voltage}$$


$$V_o = 0 + (-4V)$$

$$V_o = 0 - 4 = -4V$$

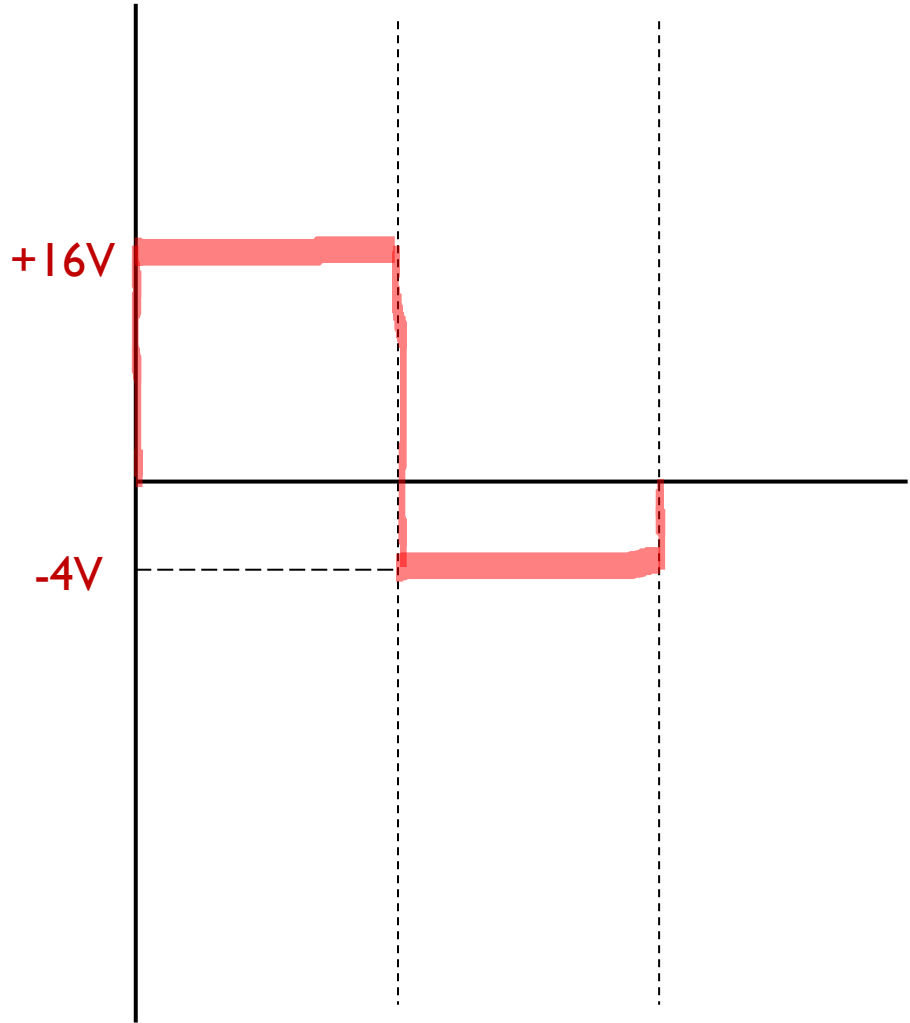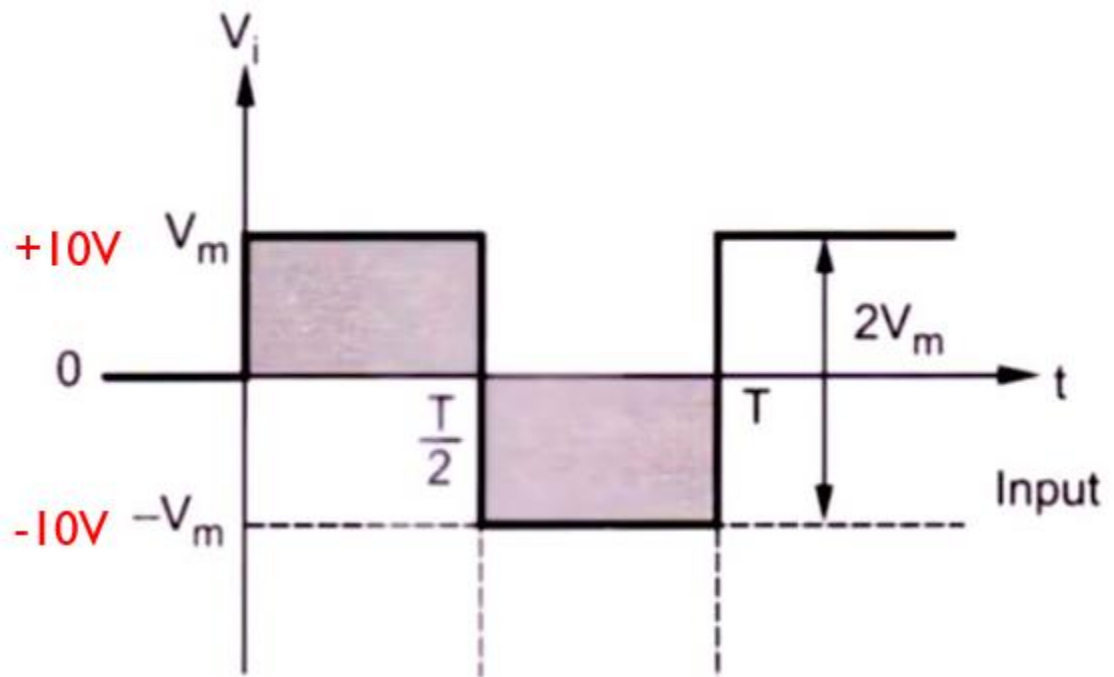BIASED POSITIVE CLAMPER (NEGATIVE BIASED)



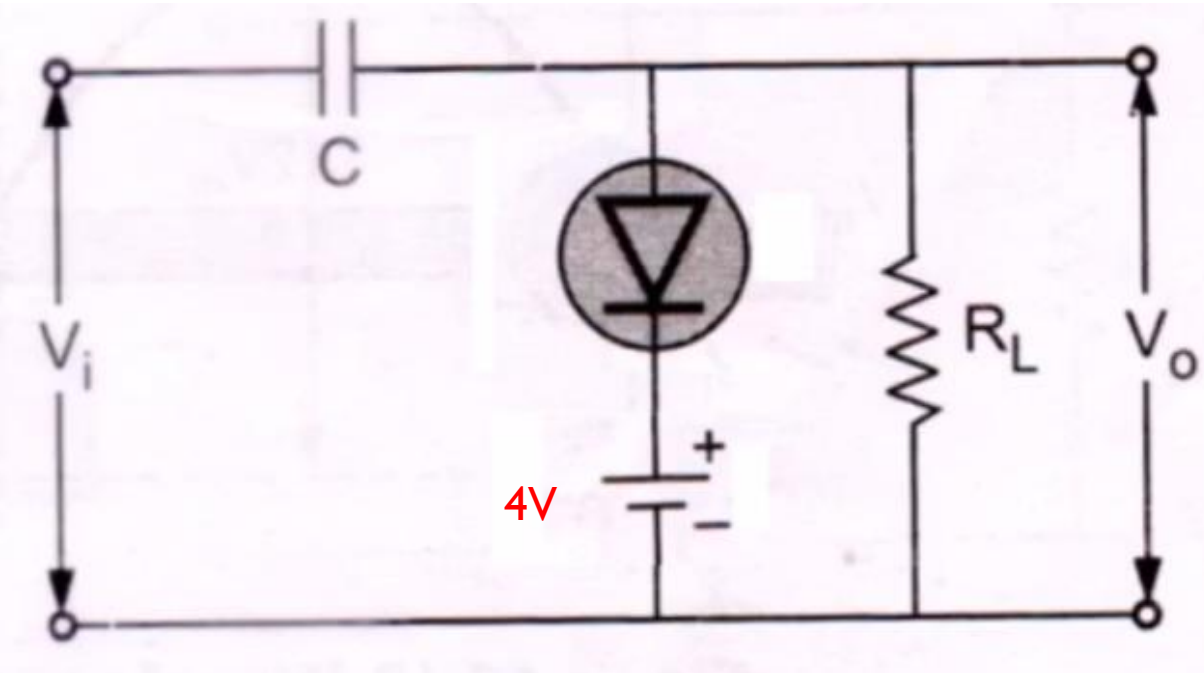BIASED NEGATIVE CLAMPER (POSITIVE BIASED)




+ve Half Cycle

$$V_o = 0 + \text{Battery Voltage}$$

$$V_o = 0 + (+4V)$$

$$V_o = 0 + 4 = +4V$$

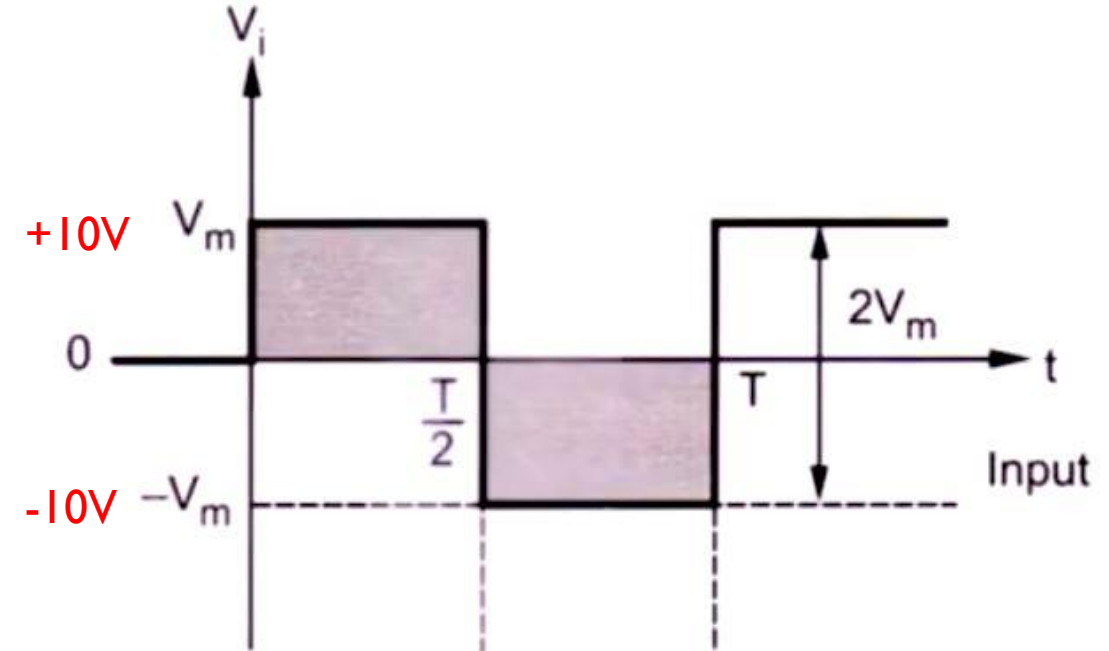



-ve Half Cycle

$$V_o = -V_i - V_c + \text{Battery Voltage}$$


$$V_o = -10 - 10 + (+4V)$$

$$V_o = -20 + 4 = -16V$$

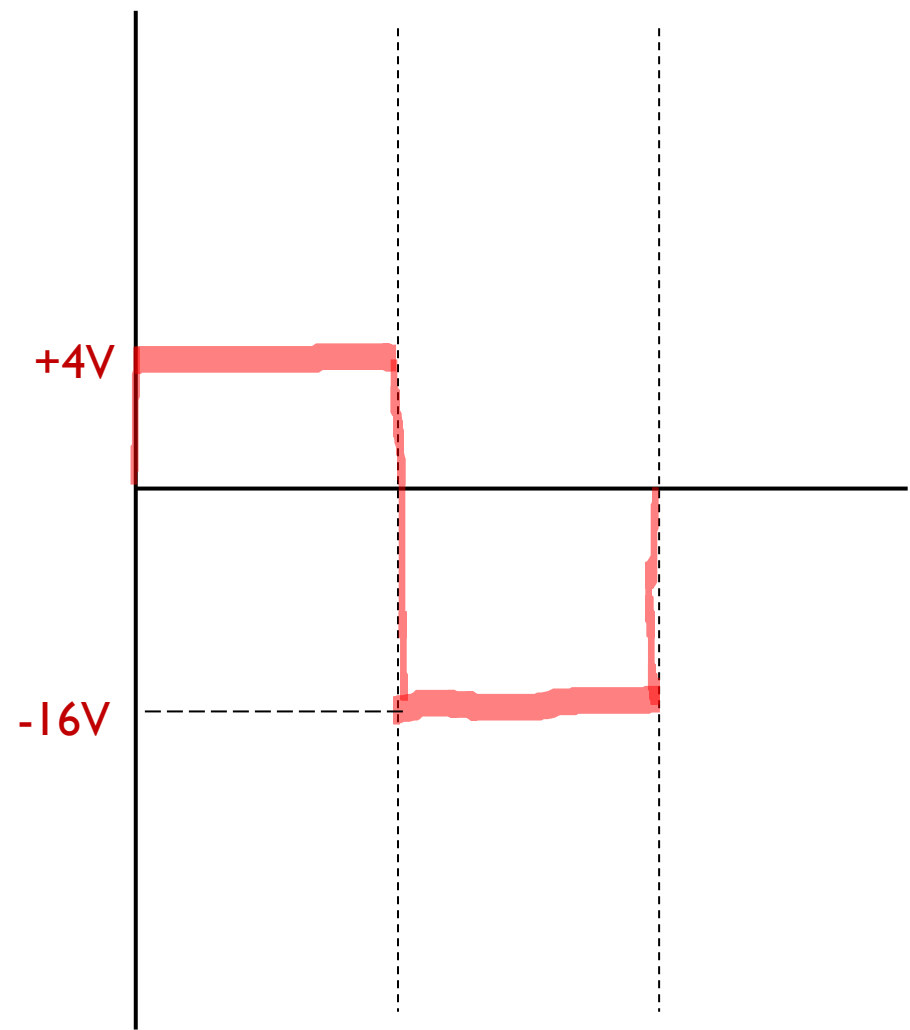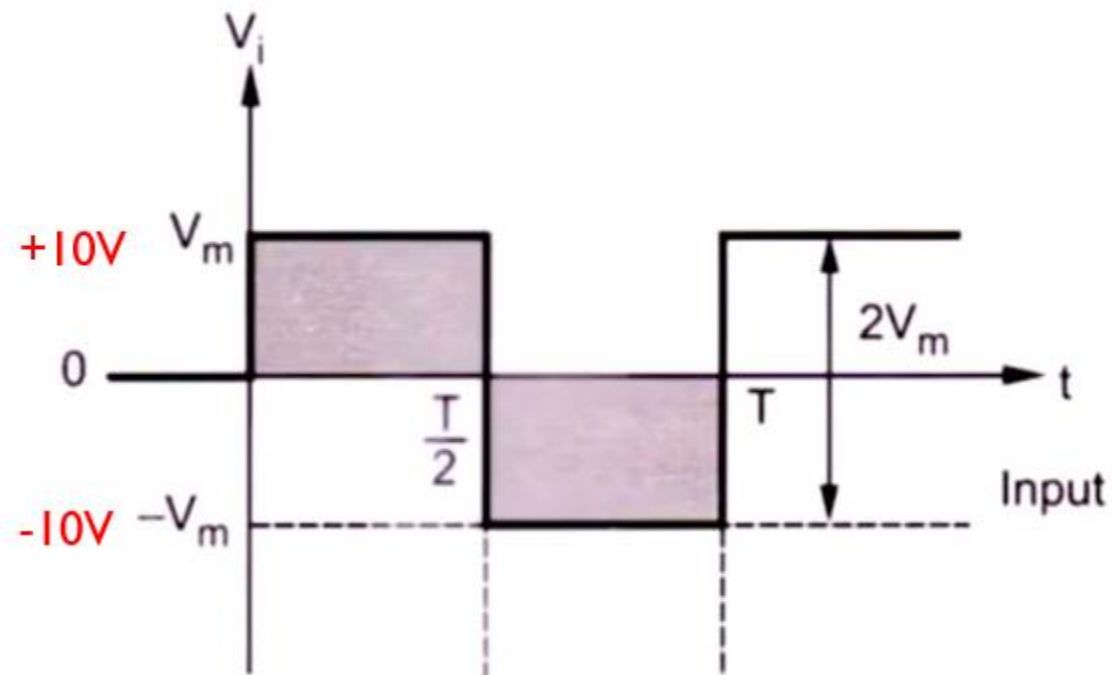BIASED NEGATIVE CLAMPER (POSITIVE BIASED)



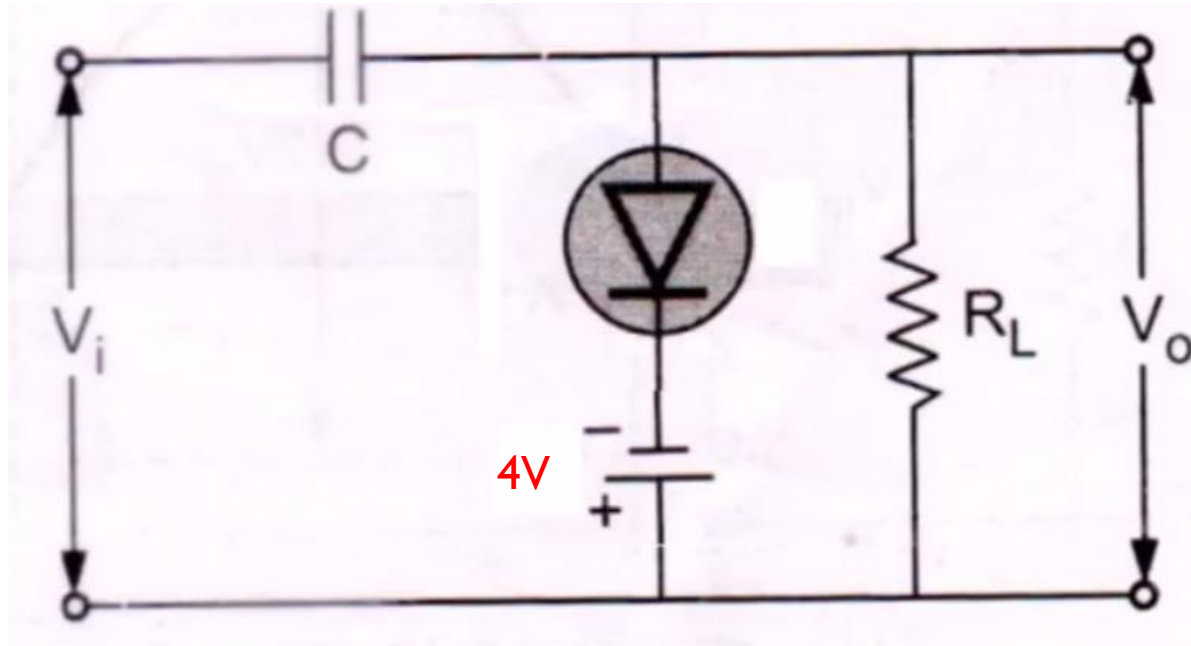BIASED NEGATIVE CLAMPER (NEGATIVE BIASED)




+ve Half Cycle

$$V_o = 0 + \text{Battery Voltage}$$

$$V_o = 0 + (-4V)$$

$$V_o = 0 - 4 = -4V$$

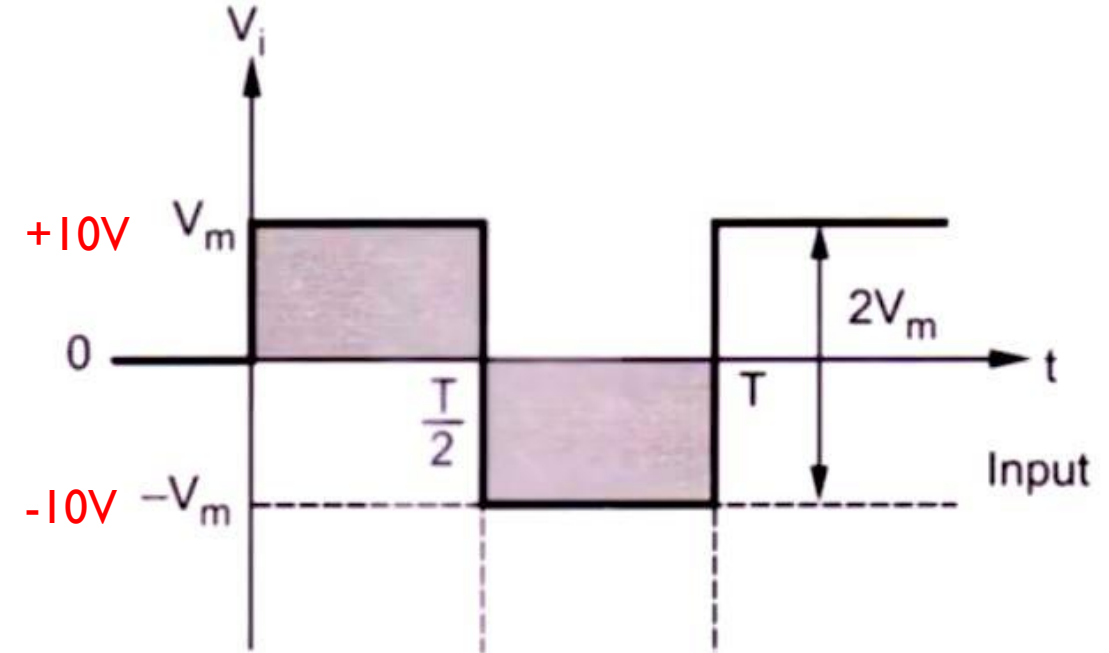

-ve Half Cycle

$$V_o = -V_i - V_c + \text{Battery Voltage}$$

$$V_o = -10 - 10 + (-4V)$$

$$V_o = -20 - 4 = -24V$$

BIASED NEGATIVE CLAMPER (NEGATIVE BIASED)

