


HIGH FREQUENCY EQUIVALENT CIRCUITS

- The performance of BJT is limited at higher frequencies due to the presence of junction and diffusion capacitance.
- So for analysing a transistor circuit at high frequency small signal models are not suitable.
- Equivalent circuit should be modified by including the junction capacitance of the transistor.
- At low frequencies we can analyse transistor using h-parameters, but in high frequencies it is not suitable
 - Value of h-parameters are not constant at high frequencies.
 - At high frequencies h-parameters become more complex



HYBRID π MODEL

- C_{μ} - Transition capacitance between base and collector. Early effect representation
- C_{π} - Diffusion Capacitance. Minority carriers stored in Base region
- r_{π} - small input resistance between base and emitter seen from base
- r_{μ} - collector base reverse resistance (large value)
- r_b - base terminal resistance (small value)
- r_o - output resistance seen from output, collector emitter resistance
- $g_m v_{be}$ - current source

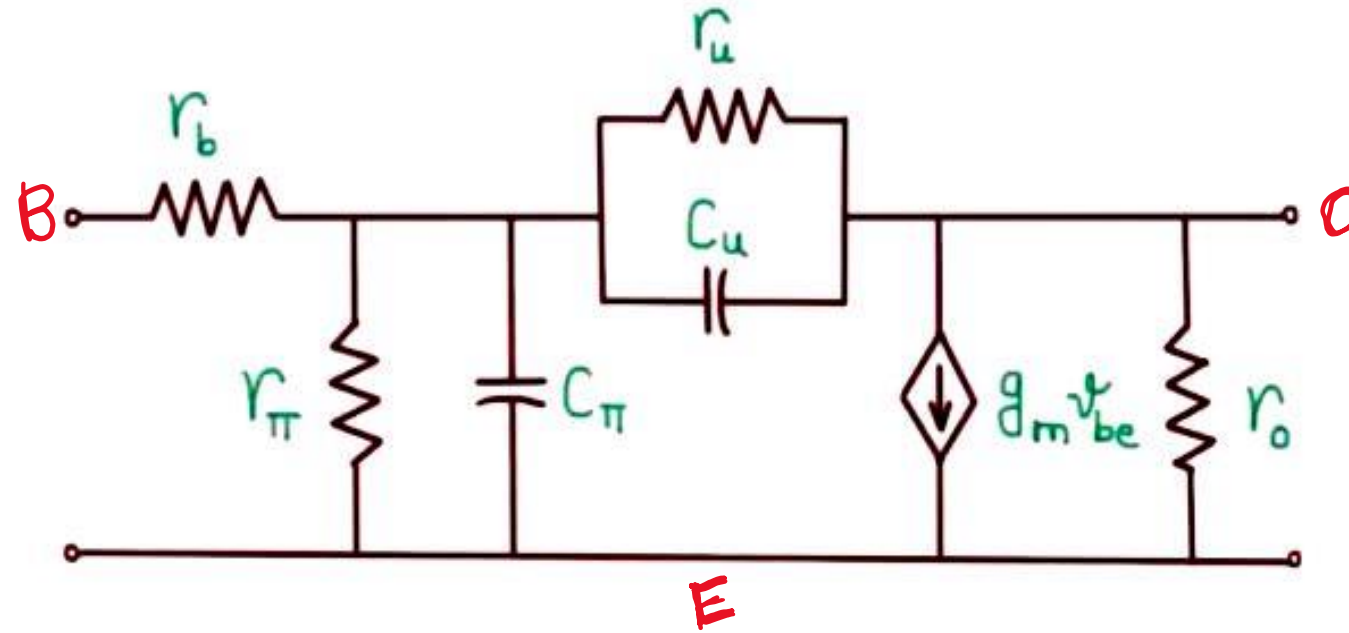

VOLTAGE CONTROLLED CURRENT SOURCE
CURRENT CONTROLLED CURRENT SOURCE




MILLER'S THEOREM

- In analysis of High Frequency response of CE Amplifier, the bridging capacitances (C_{μ} and C_{π}) are replaced by an equivalent input capacitance. This effective technique is based on general theorem known as **Miller's Theorem**.




MILLER'S THEOREM

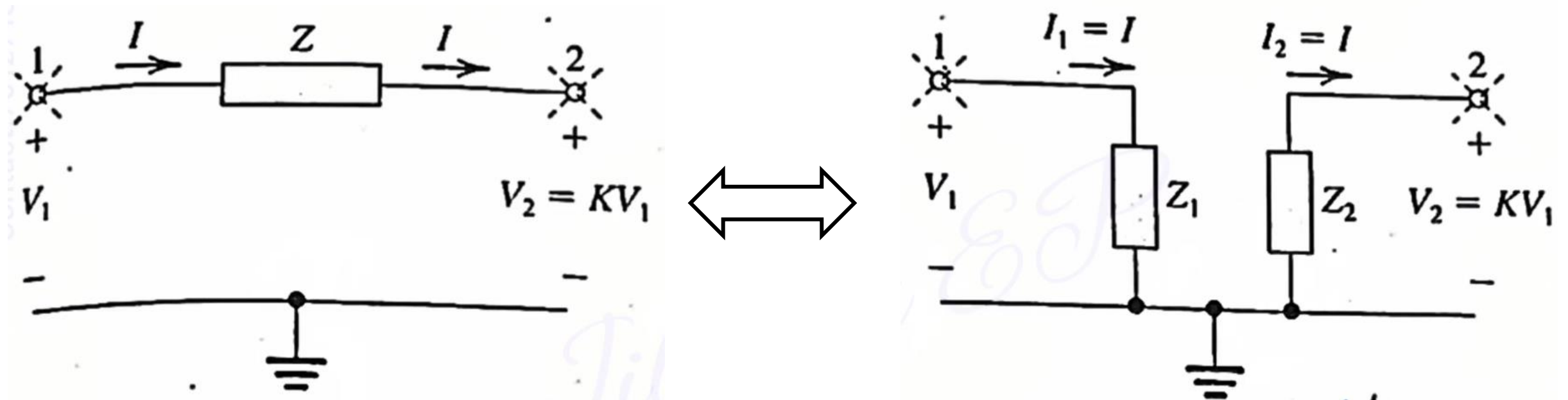

$$Z_i = \frac{Z_f}{(1-A)}$$

$$Z_o = \frac{Z_f A}{(A-1)}$$

MILLER'S THEOREM PROOF

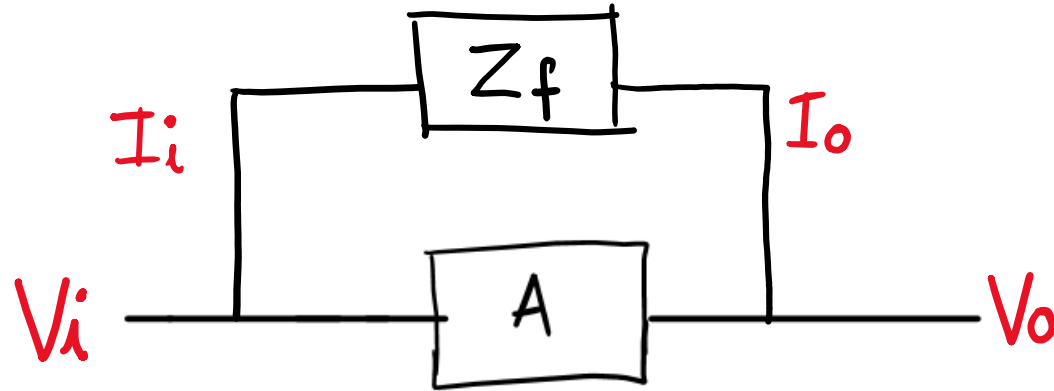


$$A = \frac{V_o}{V_i}$$

$$Z_i = \frac{V_i}{I_i}$$

$$Z_o = \frac{V_o}{I_o}$$

MILLER'S THEOREM PROOF

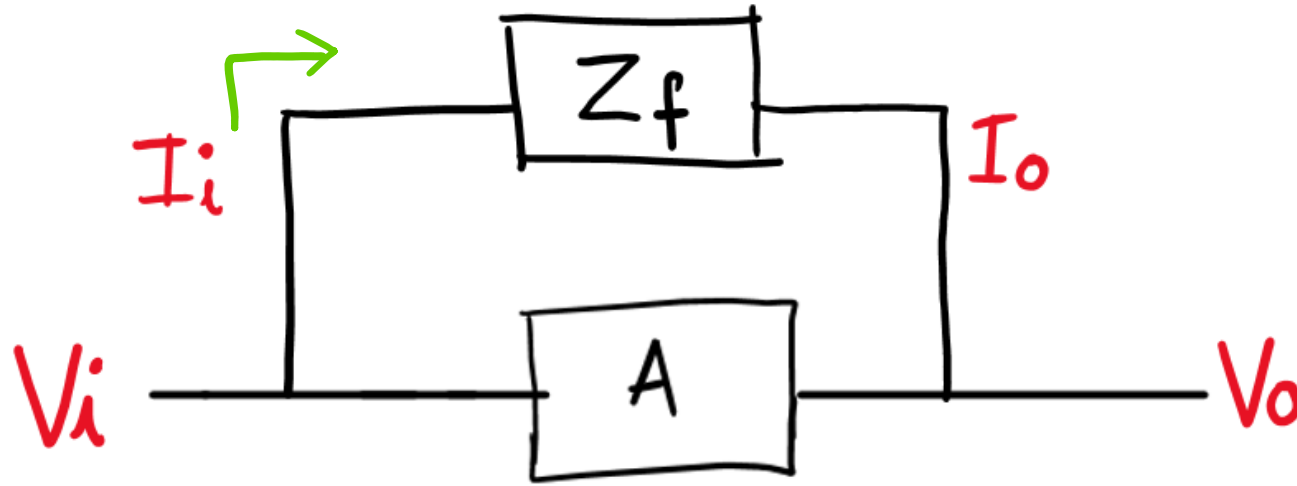

$$I_i = \frac{V_i - V_o}{Z_f} \rightarrow \textcircled{1} \quad I_i = \frac{V_i - AV_i}{Z_f} = \frac{V_i(1-A)}{Z_f}$$


$$A = \frac{V_o}{V_i} \Rightarrow V_o = AV_i$$

We know

$$Z_i = \frac{V_i}{I_i} = \frac{Z_f}{(1-A)}$$

$$Z_i = \frac{Z_f}{(1-A)}$$

MILLER'S THEOREM PROOF

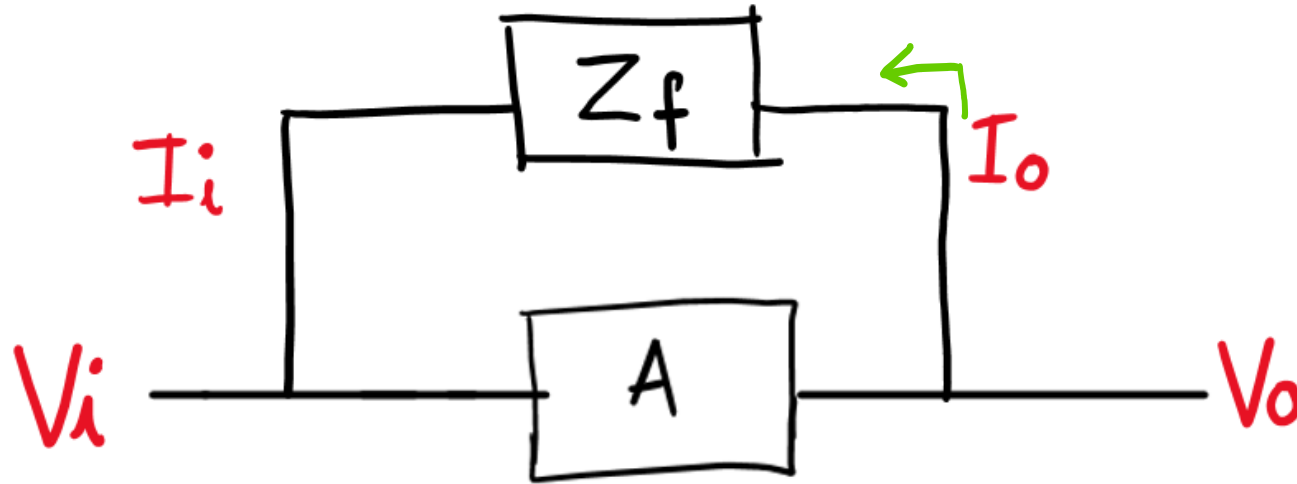

$$I_o = \frac{V_o - V_i}{Z_f}$$

$$A = \frac{V_o}{V_i} \Rightarrow V_i = \frac{V_o}{A}$$


$$I_o = \frac{V_o - V_o/A}{Z_f} = \frac{V_o (1 - 1/A)}{Z_f}$$

We know,


$$Z_o = \frac{V_o}{I_o} = \frac{Z_f}{(1 - 1/A)}$$

$$Z_o = \frac{Z_f A}{(A - 1)}$$

MILLER'S THEOREM PROOF

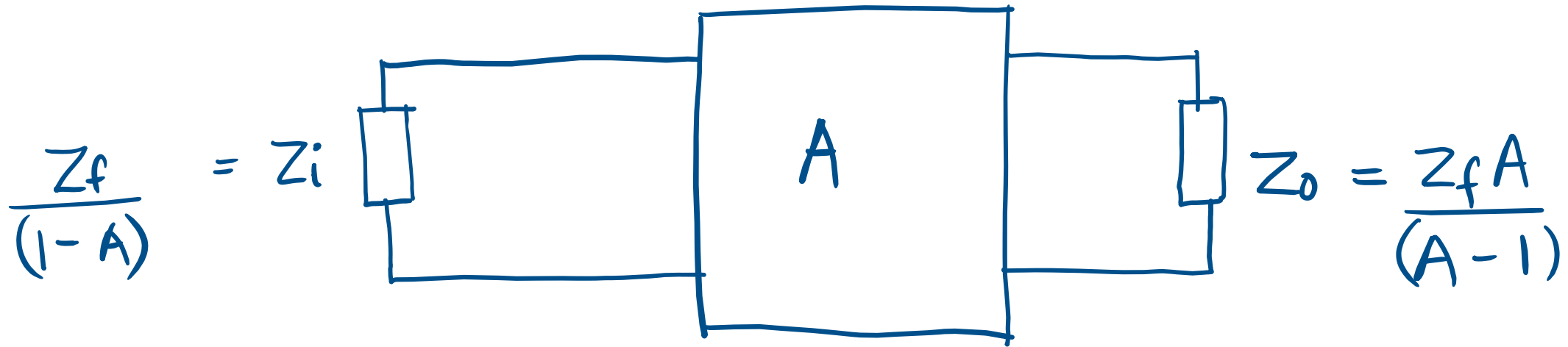

IF CAPACITOR AS FEEDBACK COMPONENT

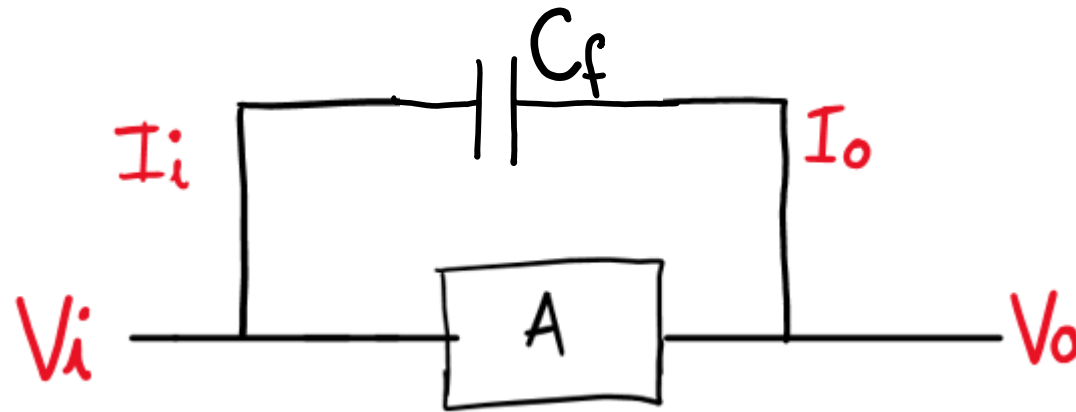

$$Z_i = \frac{Z_f}{(1-A)}$$


$Z_i, Z_f \rightarrow \text{Capacitor}$

$$\frac{1}{j\omega C_i} = \frac{1/j\omega C_f}{(1-A)}$$

$$\frac{1}{C_i} = \frac{1}{C_f(1-A)}$$

$$C_i = C_f(1-A)$$

IF CAPACITOR AS FEEDBACK COMPONENT

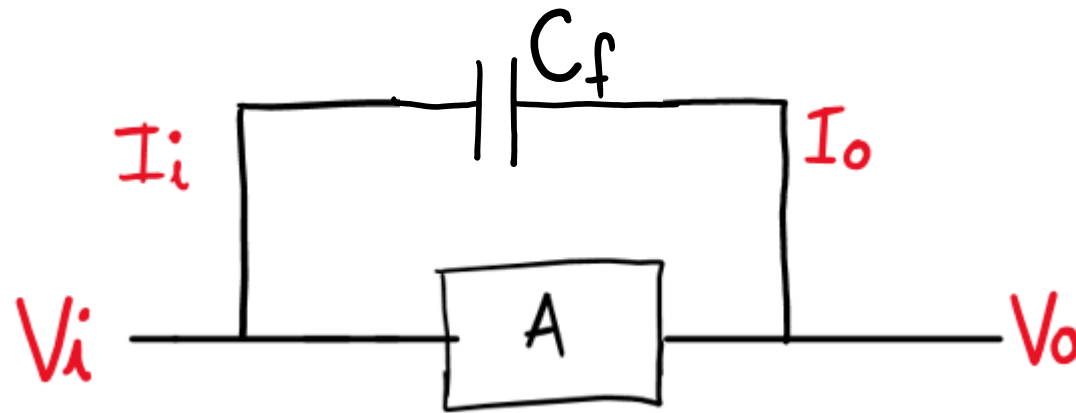

$$Z_o = \frac{Z_f A}{(A-1)}$$

Z_o, Z_f - capacitors

$$\frac{1}{j\omega C_o} = \frac{A/j\omega C_f}{(A-1)}$$


$$\frac{1}{C_o} = \frac{1}{C_f} \left(\frac{A}{A-1} \right)$$

$$\left(\frac{A}{A-1} \right) \approx 1$$

$$C_o \approx C_f$$


$$C_o = C_f \left(\frac{A-1}{A} \right)$$

IF CAPACITOR AS FEEDBACK COMPONENT

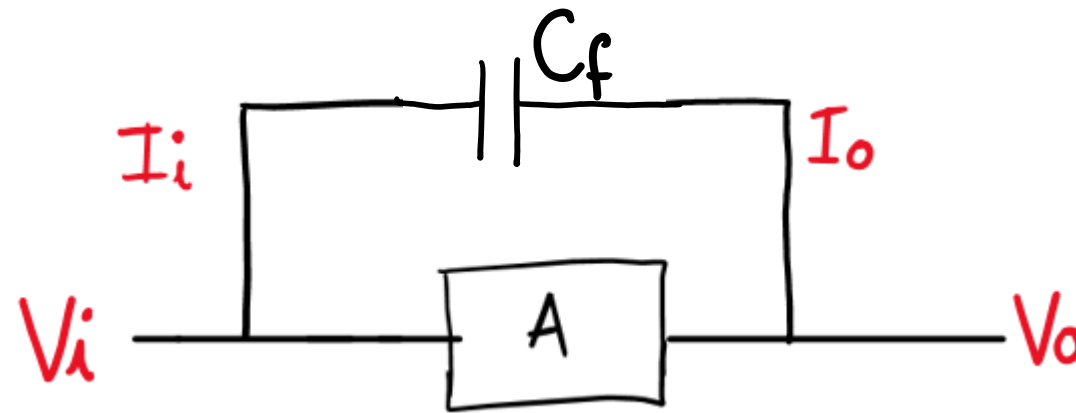


$$C_i = C_f(1-A)$$

$$C_o = C_f \frac{(A-1)}{A}$$

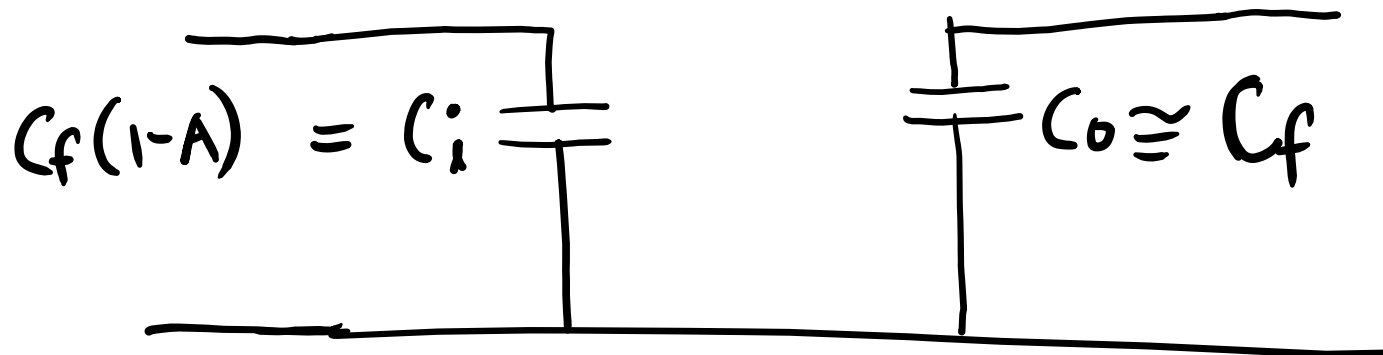

HIGH FREQUENCY HYBRID π MODEL OF CE AMPLIFIER


- C_μ - Transition capacitance between base and collector. Early effect representation
- C_π - Diffusion Capacitance. Minority carriers stored in Base region
- r_π - small input resistance between base and emitter seen from base
- r_μ - collector base reverse resistance (large value)
- r_b - base terminal resistance (small value)
- r_o - output resistance seen from output, collector emitter resistance
- $g_m v_{be}$ - current source

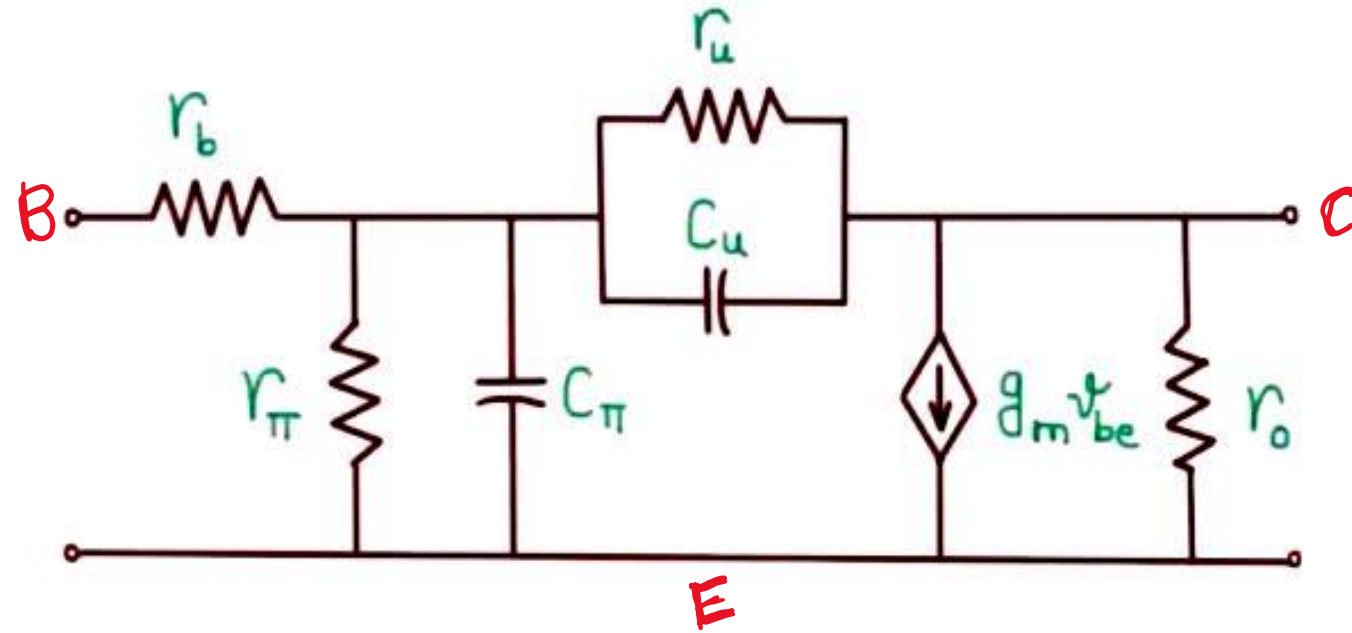


HIGH FREQUENCY HYBRID π MODEL OF CE AMPLIFIER

STEPS TO CONVERT TO HYBRID π MODEL

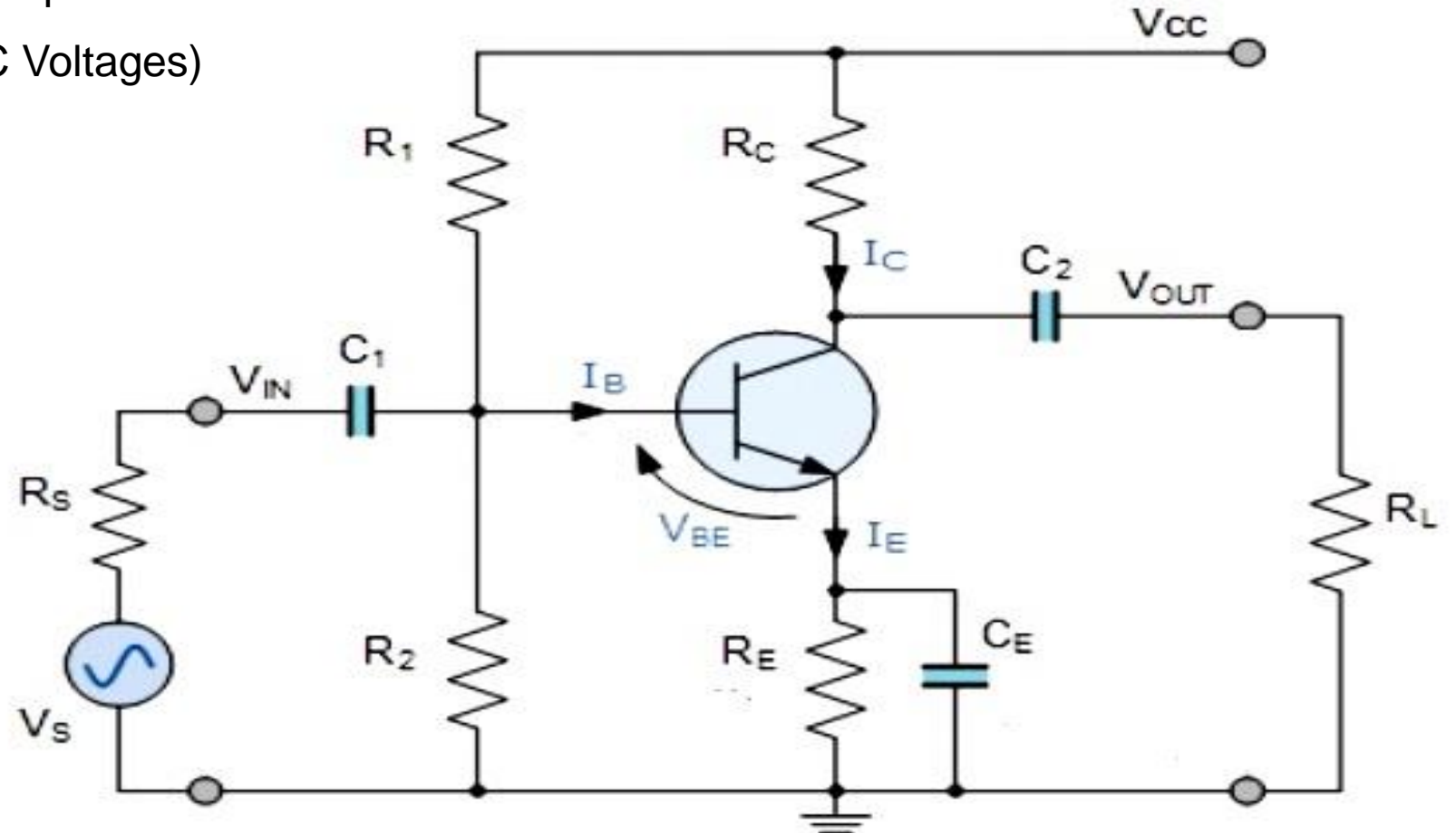- Short circuit all Bypass and Coupling Capacitors.
Remove all external power supply (DC Voltages)
and connect that node to ground




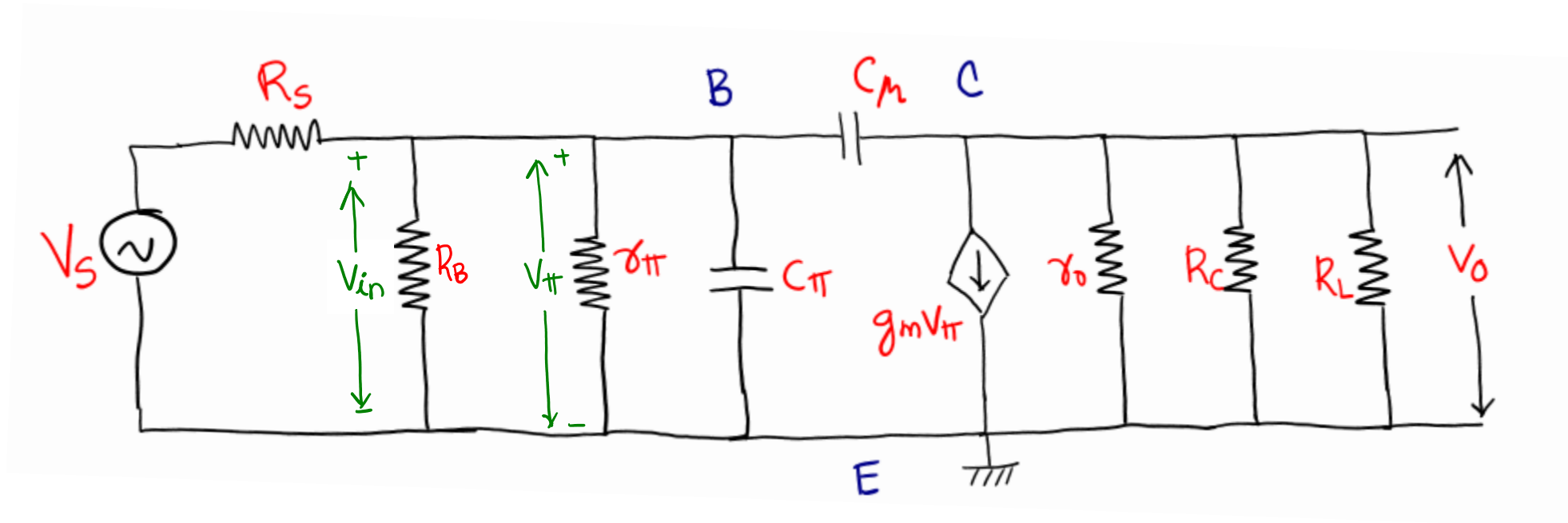HIGH FREQUENCY HYBRID π MODEL OF CE AMPLIFIER



HIGH FREQUENCY HYBRID π MODEL OF CE AMPLIFIER

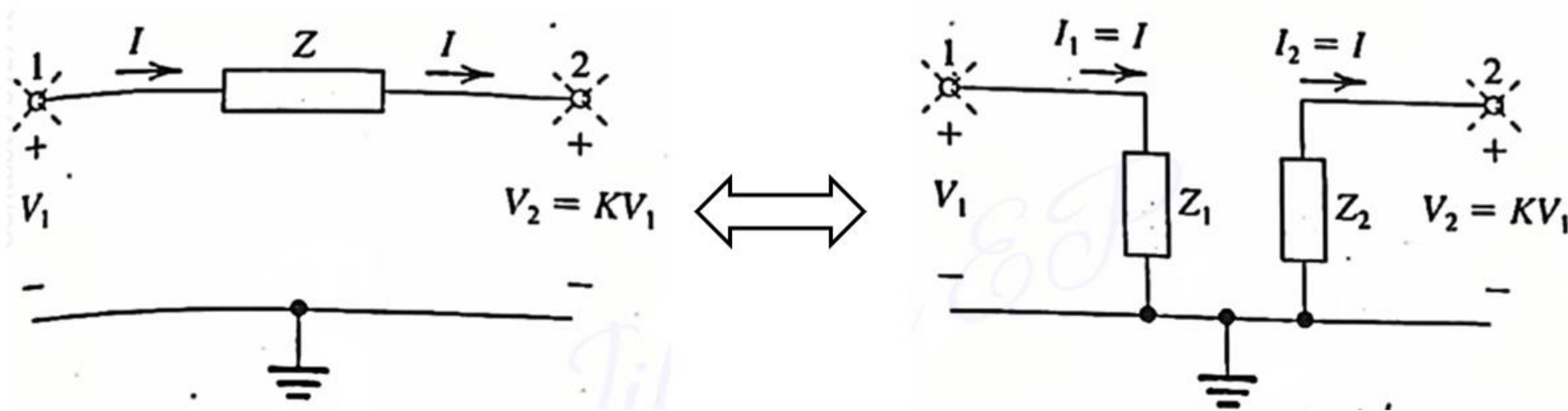
- The feedback capacitor C_μ can be split using **Miller's Theorem**.
- So by Miller's Theorem,



$$Z_i = \frac{Z_f}{(1-A)}$$

$$Z_o = \frac{Z_f A}{(A-1)}$$

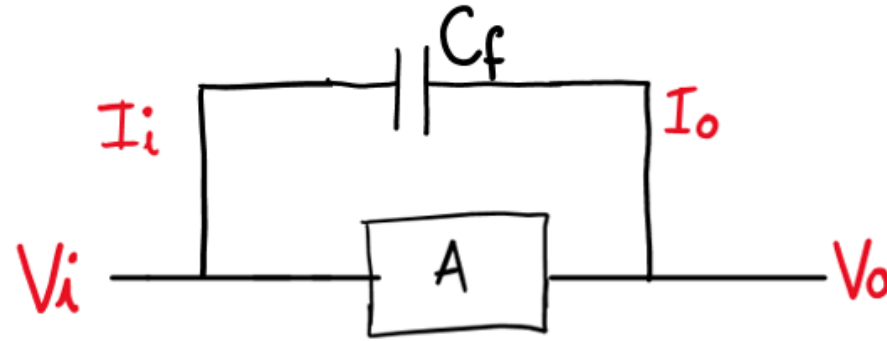HIGH FREQUENCY HYBRID π MODEL OF CE AMPLIFIER



- Applying Miller's theorem at input side

$$c_1 = c_{\mu}(1 - A_V)$$



HIGH FREQUENCY HYBRID π MODEL OF CE AMPLIFIER

- Applying Miller's theorem at input side

$$C_1 = C_\mu (1 - A_V)$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_\pi} \quad (V_{in} \cong V_\pi)$$

$$V_{out} = -g_m V_\pi (\infty \parallel R_C \parallel R_L)$$


$$A_V = \frac{V_{out}}{V_\pi} = \frac{-g_m V_\pi (\infty \parallel R_C \parallel R_L)}{V_\pi}$$

$$C_i = C_\pi (1 + g_m (\infty \parallel R_C \parallel R_L))$$

$$A_V = -g_m (\infty \parallel R_C \parallel R_L)$$



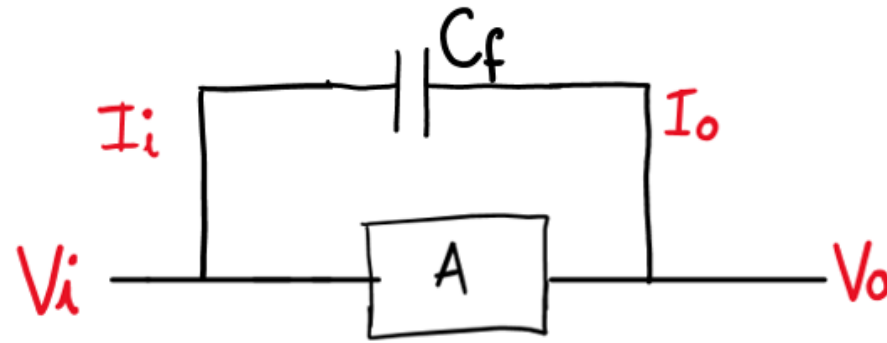HIGH FREQUENCY HYBRID π MODEL OF CE AMPLIFIER



- Applying Miller's theorem at output side




$$C_2 = C_{\mu} \frac{A_V - 1}{A_V}$$

$$A_V = -g_m (r_o \parallel R_c \parallel R_L)$$


$$C_2 \cong C_{\mu}$$



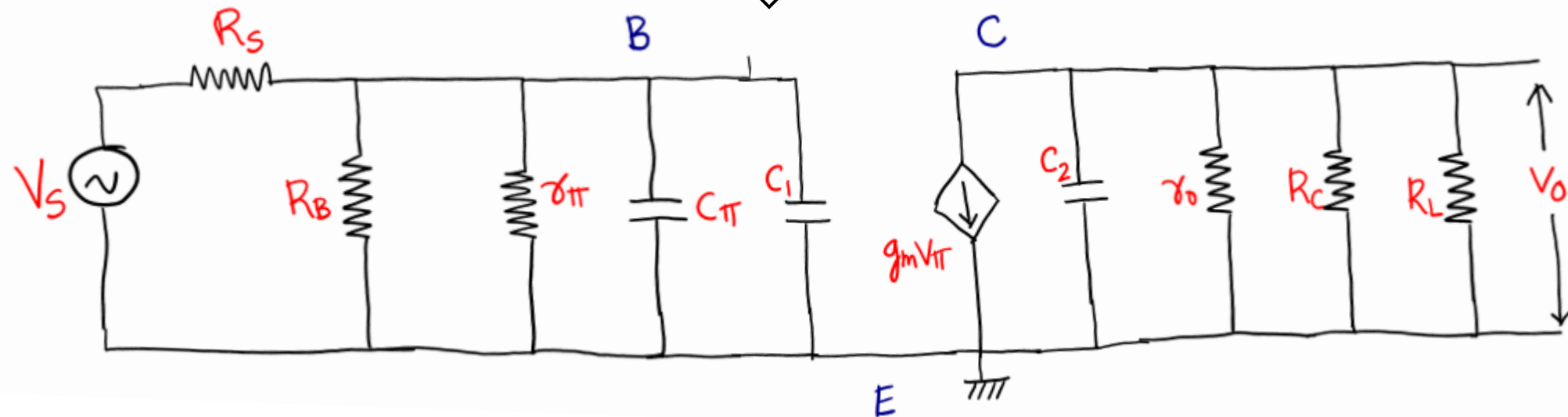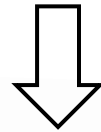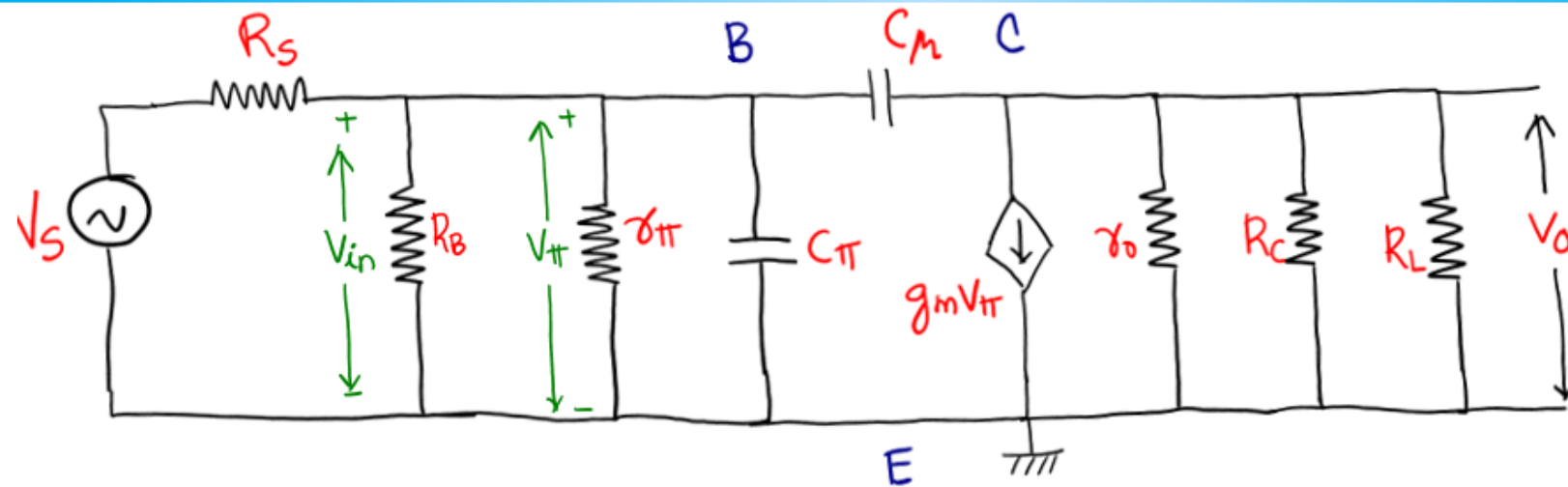HIGH FREQUENCY HYBRID π MODEL OF CE AMPLIFIER



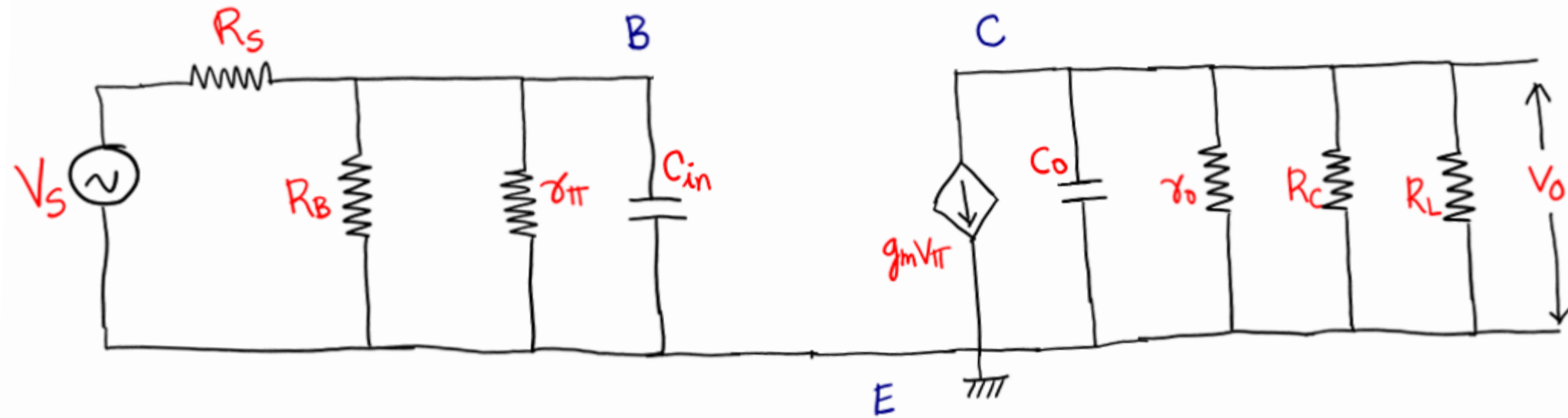HIGH FREQUENCY HYBRID π MODEL OF CE AMPLIFIER




$$C_{in} = C_{\pi} + C_1$$

$$C_o = C_2$$




INPUT RESISTANCE

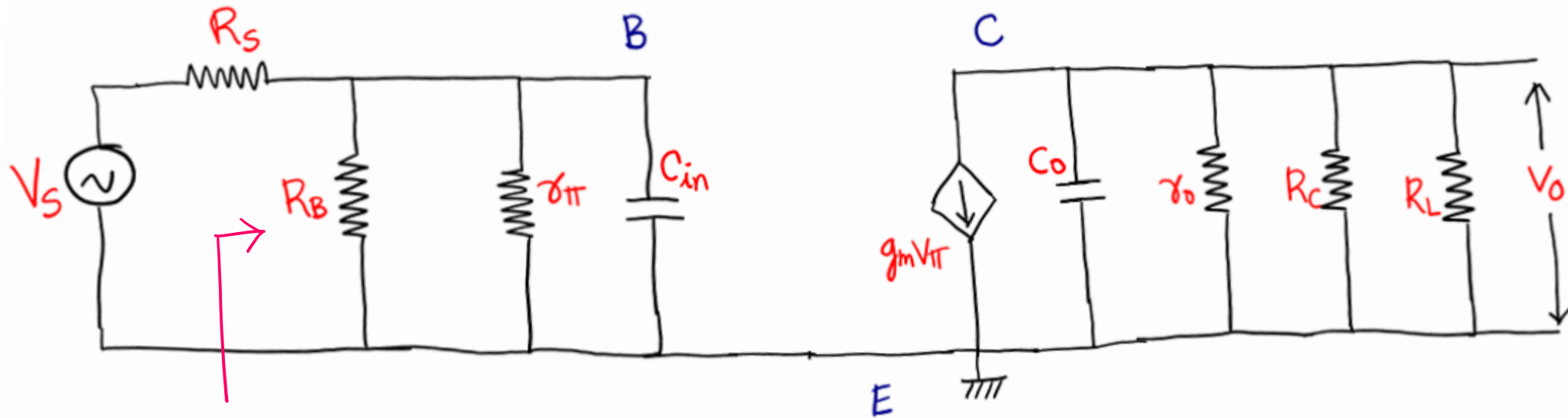

$$R_i = R_B \parallel r_{\pi}$$


VOLTAGE GAIN

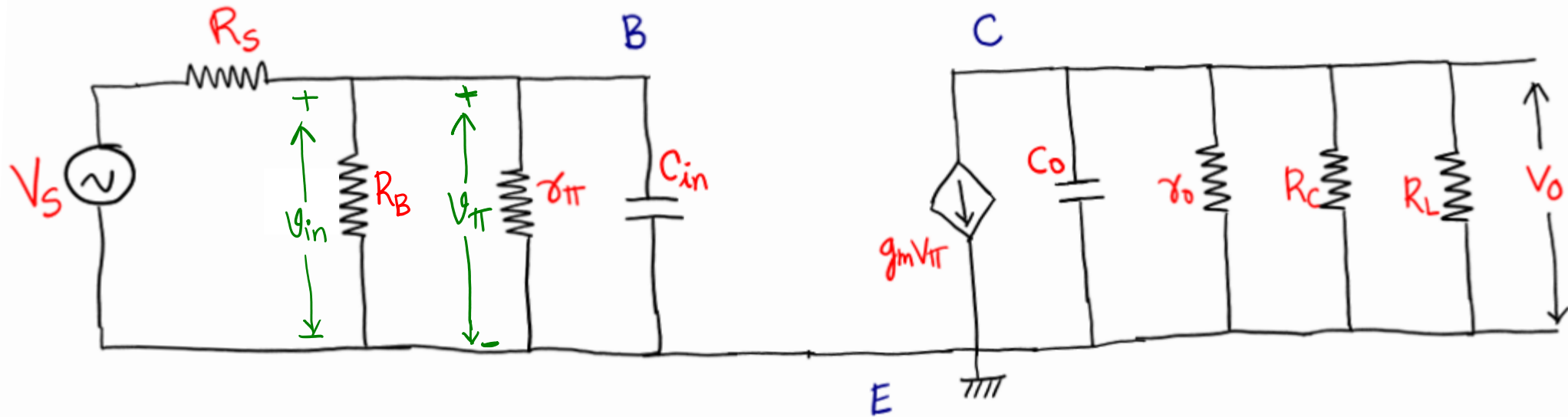

$$A_{V_S} = \frac{V_{out}}{V_S} = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_S}$$




EFFECT OF INPUT CAPACITANCE

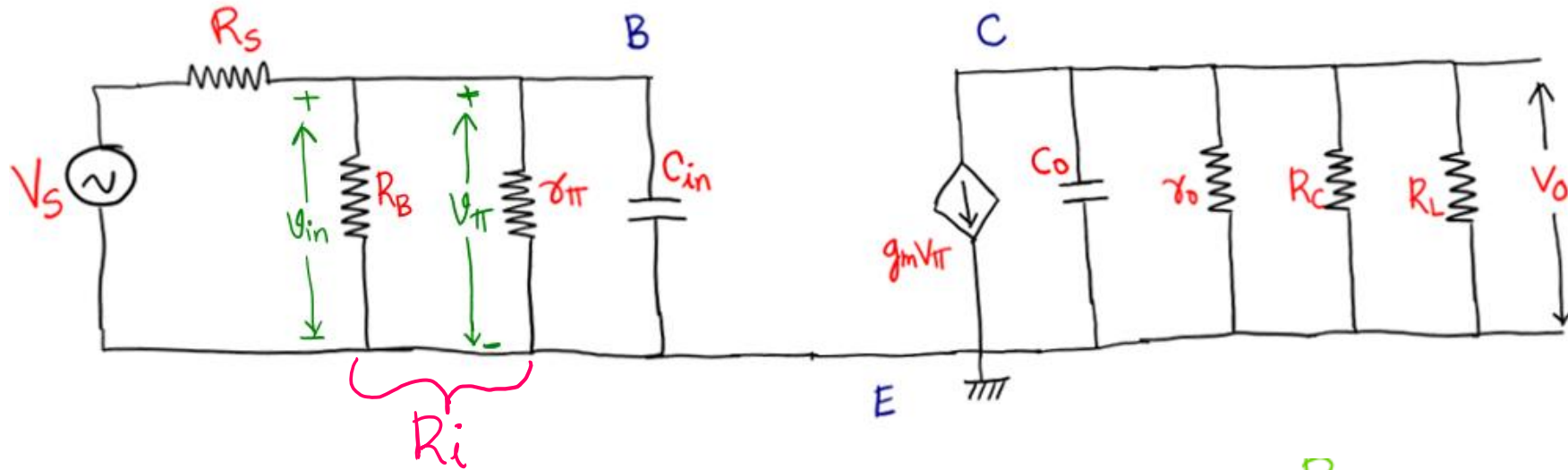

$$R_i = R_B \parallel r_\pi$$

By voltage Division rule
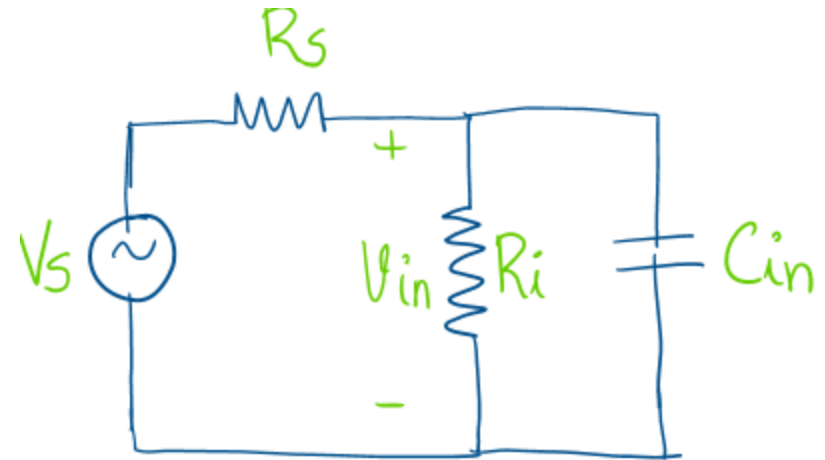
$$V_{in} = \frac{V_s \times (R_i \parallel 1/j\omega C_{in})}{R_s + (R_i \parallel 1/j\omega C_{in})}$$



EFFECT OF INPUT CAPACITANCE

$$\begin{aligned}(R_i \parallel 1/j\omega C_{in}) &= \frac{R_i \times \frac{1}{j\omega C_{in}}}{R_i + \frac{1}{j\omega C_{in}}} \\&= \frac{R_i / \cancel{j\omega C_{in}}}{j\omega R_i C_{in} + 1 / \cancel{j\omega C_{in}}}\end{aligned}$$

$$(R_i \parallel 1/j\omega C_{in}) = \frac{R_i}{1 + j\omega R_i C_{in}}$$



EFFECT OF INPUT CAPACITANCE

$$(R_i \parallel 1/j\omega C_{in}) = \frac{R_i}{1 + j\omega R_i C_{in}} \quad ; \quad V_{in} = \frac{V_s \times (R_i \parallel 1/j\omega C_{in})}{R_s + (R_i \parallel 1/j\omega C_{in})}$$

$$V_{in} = \frac{V_s \times (R_i / (1 + j\omega R_i C_{in}))}{R_s + (R_i / (1 + j\omega R_i C_{in}))}$$


$$V_{in} = \frac{(V_s \cdot R_i / (1 + j\omega R_i C_{in}))}{((R_s(1 + j\omega R_i C_{in}) + R_i) / (1 + j\omega R_i C_{in}))}$$

$$V_{in} = \frac{V_s \cdot R_i}{R_s + j\omega R_i R_s C_{in} + R_i}$$

$$V_{in} = \frac{V_s \cdot R_i}{(R_i + R_s) \left(1 + j\omega \left(\frac{R_i R_s}{R_i + R_s} \right) C_{in} \right)}$$

$$\frac{V_{in}}{V_s} = \left(\frac{R_i}{R_i + R_s} \right) \left(\frac{1}{1 + j\omega (R_i \parallel R_s) C_{in}} \right)$$

EFFECT OF OUTPUT CAPACITANCE

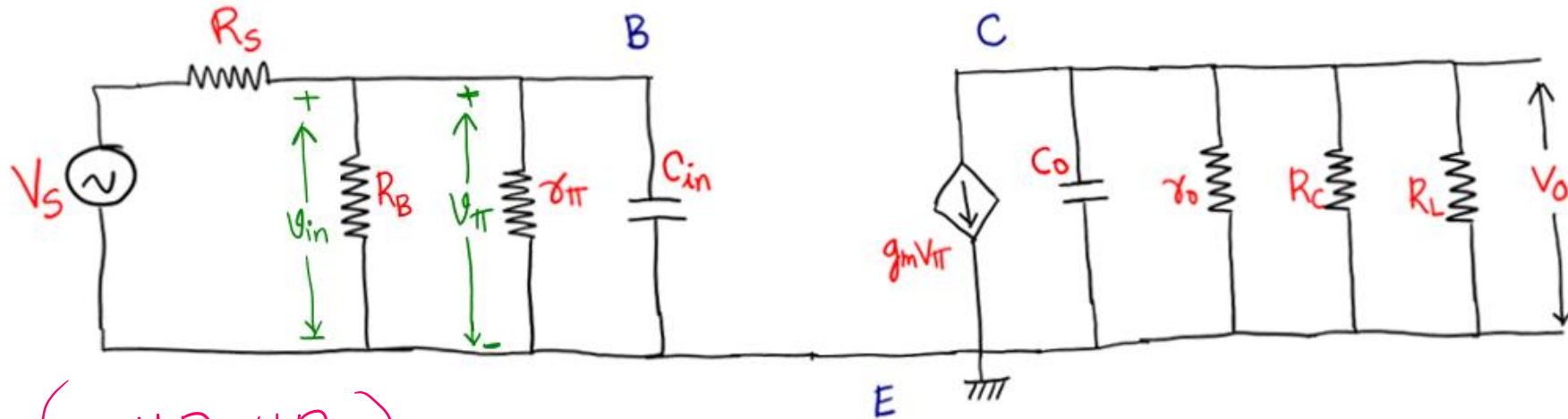

$$\frac{V_o}{V_{in}}$$

$$R_o = (r_o \parallel R_c \parallel R_L)$$

$$V_o = -g_m V_{\pi} (R_o \parallel 1/j\omega C_o)$$

$$V_{in} \cong V_{\pi}$$

$$\frac{V_o}{V_{in}} = \frac{-g_m \cancel{V_{\pi}} (R_o \parallel 1/j\omega C_o)}{\cancel{V_{\pi}}}$$

EFFECT OF OUTPUT CAPACITANCE

$$\begin{aligned} (R_o \parallel 1/j\omega C_o) &= \frac{R_o \cdot 1/j\omega C_o}{R_o + 1/j\omega C_o} \\ &= \frac{R_o / j\omega C_o}{j\omega R_o C_o + 1/j\omega C_o} \end{aligned}$$

$$(R_o \parallel 1/j\omega C_o) = \frac{R_o}{1 + j\omega R_o C_o}$$

$$\frac{V_o}{V_{in}} = -g_m (R_o \parallel 1/j\omega C_o)$$

$$\frac{V_o}{V_{in}} = \frac{-g_m R_o}{1 + j\omega R_o C_o}$$

VOLTAGE GAIN

$$\frac{V_{in}}{V_s} = \left(\frac{R_i}{R_i + R_s} \right) \left(\frac{1}{1 + j\omega(R_i \parallel R_s)C_{in}} \right)$$

$$\frac{V_o}{V_{in}} = \frac{-g_m R_o}{1 + j\omega R_o C_o}$$

$$A_{V_s} = \frac{V_o}{V_s} = \frac{V_o}{V_{in}} \times \frac{V_{in}}{V_s}$$

$$A_{V_s} = \left(\frac{-g_m R_o}{1 + j\omega R_o C_o} \right) \left(\frac{R_i}{R_i + R_s} \right) \left(\frac{1}{1 + j\omega(R_i \parallel R_s)C_{in}} \right)$$

$$A_m = \frac{-g_m R_o R_i}{R_i + R_s}$$

$$A_{V_s} = \frac{A_m}{(1 + j\omega R_o C_o)(1 + j\omega(R_i \parallel R_s)C_{in})}$$

VOLTAGE GAIN IN TERMS OF FREQUENCY

$$A_{Vs} = \frac{A_m}{\underbrace{(1 + j\omega R_o C_o)}_{(2)} \underbrace{(1 + j\omega (R_i \parallel R_s) C_{in})}_{(1)}}$$

$$\textcircled{1} \Rightarrow 1 + j\omega (R_i \parallel R_s) C_{in}$$
$$\omega = 2\pi f$$

$$\Rightarrow 1 + j2\pi f (R_i \parallel R_s) C_{in}$$

$$\Rightarrow \boxed{1 + j \left(\frac{f}{f_{H1}} \right)}$$

$$f_{H1} = \frac{1}{2\pi (R_i \parallel R_s) C_{in}}$$

f_{H1} – Cutoff frequency introduced by Input Capacitor

VOLTAGE GAIN IN TERMS OF FREQUENCY

$$A_{Vs} = \frac{A_m}{\underbrace{(1 + j\omega R_o C_o)}_{(2)} \underbrace{(1 + j\omega (R_i || R_s) C_{in})}_{(1)}}$$

$$(2) \Rightarrow 1 + j\omega R_o C_o$$

$$\omega = 2\pi f$$

$$\Rightarrow 1 + j2\pi f R_o C_o$$

$$\Rightarrow 1 + j\left(\frac{f}{f_{H2}}\right)$$

$$f_{H2} = \frac{1}{2\pi R_o C_o}$$

f_{H2} – Cutoff frequency introduced by Output Capacitor

VOLTAGE GAIN IN TERMS OF FREQUENCY

$$A_{Vs} = \frac{A_m}{(1 + j\omega R_o C_o)(1 + j\omega(R_i \parallel R_s)C_{in})}$$

$$A_{Vs} = \frac{A_m}{(1 + j(f/f_{H2})) (1 + j(f/f_{H1}))}$$

$$f_H = \frac{1}{\sqrt{(1/f_{H1})^2 + (1/f_{H2})^2}}$$

