



# APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

## Scheme for Valuation/Answer Key

*Scheme of evaluation (marks in brackets) and answers of problems/key*

**Third Semester B.Tech Degree (R) Examination December 2020 (2019 scheme)**

**Course Code: ECT205**

**Course Name: NETWORK THEORY**

Max. Marks: 100

Duration: 3 Hours

### PART A

*Answer all questions. Each question carries 3 marks*

Marks

- 1 Example – 1.0 marks (3)  
Explanation - 2.0 marks
- 2 Figure ----1.5 marks (3)  
Explanation ----1.5 marks
- 3 Statement 3 marks (3)
- 4 For LTI n/w 1.0 marks (3)  
Explanation 2.0 marks
- 5 Initial value theorem 1.5 marks (3)  
Final value theorem 1.5 marks
- 6 Circuit and derivation----1.5 marks (3)  
 $i(t) = \frac{1}{R}[\theta(t) - \frac{1}{RC}e^{-\frac{t}{RC}}]$  ----1.5 marks
- 7 No 1.0 marks (3)  
Degree of N(s) greater than degree of D(s) 2.0 marks
- 8 Explanation of Natural frequency 2.5 marks (3)  
Distinction between OCNF & SCNF 0.5 marks
- 9 Definition equations 2 marks (3)  
Equations 1 marks
- 10 
$$\begin{bmatrix} 4 & -3 \\ 15 & 15 \\ -3 & 6 \\ 15 & 15 \end{bmatrix}$$
 (3)

Intermediate calculations- 2 marks



Final answer- 1 mark (1/4 each for the four values)

### PART B

Answer any one full question from each module. Each question carries 14 marks

#### Module 1

11 (7)

a)  $\frac{V_1}{2} + \frac{V_1 - V_2}{2} = 6$  2 mark

$\frac{V_2}{8} + \frac{V_2 - V_1}{2} + 4 = 7$  2 mark

Solving  $V_1 = 14V$  and  $V_2 = 16V$  2 mark

$I = \frac{V_1 - V_2}{2} = -1.0 A$  1 mark

b)  $I_1 = 4 \angle 45^\circ = 2.828 + j2.828$  1 mark

$-(6 + j4)I_1 + (6 + j4 - j2)I_2 = -10 \angle 30^\circ$  2 mark

solving  $I_2 = 3.714 \angle 78.91^\circ = 0.714 + j3.645 A$  2 mark

$V_{6\Omega} = 6(I_1 - I_2) = 12.684 - j4.89V$  2 mark

12 a)  $1.08V_1 - 0.75V_2 = -6.25$  2 mark (7)

$V_x = V_1 + 5 - V_2$  1 mark

$-4.75V_1 + 5.75V_2 = 21.25$  2 mark

Solving  $V_1 = -7.55V$  and  $V_2 = -2.54V$  1 mark

So  $V_x = -0.01 V$  1 mark

b)  $I_1 - I_2 = 3$  2 mark

$50 - 5I_1 - 5I_2 - 10(I_2 - I_3) - 1(I_1 - I_3) = 0$  2 mark

$I_3 = 10$  1 mark

Solving  $I_2 = 6.76 A$  1 mark

Current in  $10\Omega = I_3 - I_2 = 3.24 A$  1 mark

#### Module 2

13 a)  $V_{th} = 24V$  2 mark (7)

$I_N = 10A$  2 mark

$R_{th} = 2.4\Omega$  1 mark

$I_L = 6A$  2 mark

b)  $50 \angle 0$  alone



$$I_1 = 7.46 \angle -26.56 \quad 2.5 \text{ marks} \quad (7)$$

20  $\angle$  90 alone

$$I_2 = 11.94 \angle 63.44 \quad 2.5 \text{ marks}$$

$$I = I_1 + I_2 = 14.08 \angle 31.46 = 12.01 + j 7.35 \text{ A} \quad 2 \text{ mark}$$

14 (7)

a) Node equations

$$V_{th} = 13.09 \text{ V} \quad 2 \text{ mark}$$

$$R_{th} = 1.09 \Omega \quad 2 \text{ mark}$$

$$R_L = R_{th} \quad 1 \text{ mark}$$

$$P_{max} = 39.3 \text{ W} \quad 2 \text{ mark}$$

b) 8V alone

$$I_1 = -0.133 \text{ A} \quad 2.5 \text{ marks} \quad (7)$$

4A alone

$$I_2 = 3.732 \text{ A} \quad 2.5 \text{ marks}$$

$$I_{4\Omega} = I_1 + I_2 = 3.6 \text{ A} \quad 2 \text{ mark}$$

### Module 3

15 a) Each equivalent circuit - 2 mark (8)

b)  $i(0^-) = 2 \text{ A}$  2 mark

$$I(s) = \frac{2s+12}{s(s+2)} \quad 2 \text{ mark} \quad (6)$$

$$i(t) = [6 - 4e^{-2t}]u(t) \quad 2 \text{ mark}$$

16 a)  $I(s) = \frac{A[1-e^{-sT}]}{s[R+sL]}$  3 marks (6)

$$i(t) = \frac{A}{R} \left[ u(t) - U(t-T) - e^{-Rt/L} + e^{-Rt/L} u(t-T) \right] \quad 3 \text{ marks}$$



$$b) \frac{10}{s} - I1(s) - (1 + s)[I1(s) - I2(s)] = 0 \quad 2 \text{ mark}$$

$$-(s + 1)[I2(s) - I1(s)] - I2(s) - \frac{I2(s)}{s} - \frac{4}{s} = 0 \quad 2 \text{ mark}$$

$$I1(s) = \frac{5}{s} - \frac{2}{s+1} \quad 1 \text{ mark}$$

$$I2(s) = \frac{3}{s+1} - \frac{2}{(s+1)^2} \quad 1 \text{ mark}$$

$$i1(t) = 5 - 2e^{-t} \quad 1 \text{ mark}$$

$$i2(t) = 3e^{-t} - 2te^{-t} \quad 1 \text{ mark}$$

In the figure instead of capacitor (equal length parallel lines), symbol is that of a cell (unequal length parallel lines). But from the values (1F, 4V) it can be interpreted as capacitor. It is just a drawing error. In the question it is clearly said initial voltage on capacitor is 4V

#### Module 4

- 17 a) Pole zero plot 2 mark (8)

$$V(s) = 1 + \frac{2(s+3.5)}{(s+1)(s+5)} \text{-----} 2\text{mark}$$

$$V(s) = 1 + \frac{\frac{5}{4}}{s+1} + \frac{\frac{3}{4}}{s+5} \text{-----} 2 \text{ mark}$$

$$v(t) = \mathbf{0}(t) + \frac{5}{4}e^{-t} + \frac{3}{4}e^{-5t} \text{-----} 2\text{mark}$$

- b) Explanation 6 marks (6)

- 18 a) Any six conditions 6 marks (6)

- b) Steps 2 marks

$$Z_{11}(s) = \frac{7s^2 + 7s + 5}{s^2 + s + 1} \quad 2 \text{ mark}$$

$$Z_{21}(s) = \frac{2s}{s^2 + s + 1} \quad 2 \text{ mark} \quad (8)$$

$$G_{21}(s) = \frac{2s}{7s^2 + 7s + 5} \quad 2 \text{ mark}$$

#### Module 5

(8)

(6)

3 marks

mentioned in the syllabus expected marks can be given.

2 marks

(6)

(8)

3 marks + 3 marks + 2 marks