

Roll. No.: S1

Name: Arun C. J.

GOVT. COLLEGE OF ENGINEERING, KANNUR.**Department of Electronics and Communication Engineering**

Third Semester First Series Examination November- 2022 (2019 Scheme)

Course code: ECT205

Course Name: NETWORK THEORY

Max. Marks: 50

Duration: 90 Minutes

PART A

Answer all questions. Each question Carries 3 marks

1. Differentiate between ideal and practical voltage sources. (3 Marks) (CO1)
2. Find the voltage across 2Ω resistor in the network shown in Fig. 1.

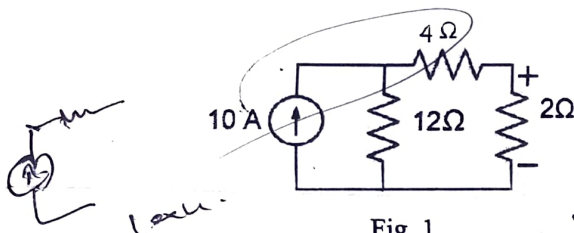


Fig. 1

$$10 \times 12 = 120 \text{ V}$$

$$120 \times \frac{2}{6}$$

$$\begin{aligned} i_0 &= I_1 + I_2 \\ 10 &= \frac{V_1}{12} + \frac{V_1}{6} \\ 120 &= V_1 + 2V_1 \end{aligned}$$

3. State maximum power transfer theorem (3 Marks) (CO1)
4. Write the steps for finding Thevenin equivalent circuit of a given network. (3 Marks) (CO1)
5. Find the Laplace transform of $f(t) = e^{at}$. (3 Marks) (CO2)

PART B

6. a) Find the mesh currents in the network shown in Fig. 2.


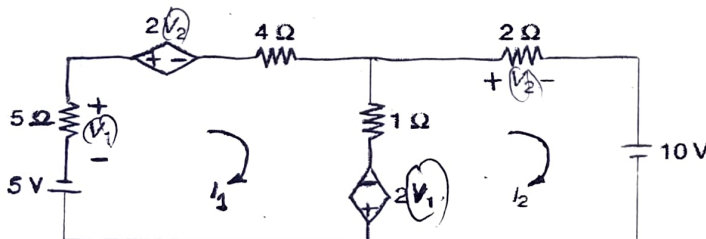


Fig. 2

$$\begin{aligned} V_1 &= 5 \\ V_1 &= 2.5 I_1 \\ V_2 &= 2 I_2 \end{aligned}$$

(7 Marks) (CO1)

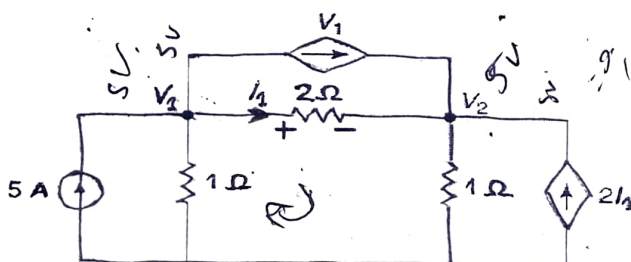- b) Find the voltage across 2Ω resistor in the network shown in Fig. 3.



$$5A = \frac{V_1}{2} + \frac{V_2}{2} + V_1$$

(7 Marks) (CO1)

OR

7. Find mesh currents I_1 , I_2 and I_3 in the network of Fig. 4.

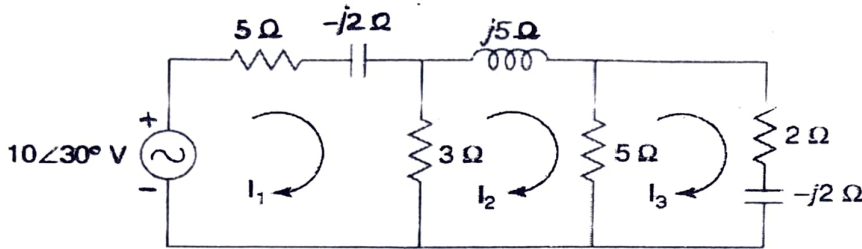


Fig. 4

(14 Marks) (CO1)

8. Find Norton's equivalent network across terminals A and B of Fig. 5.

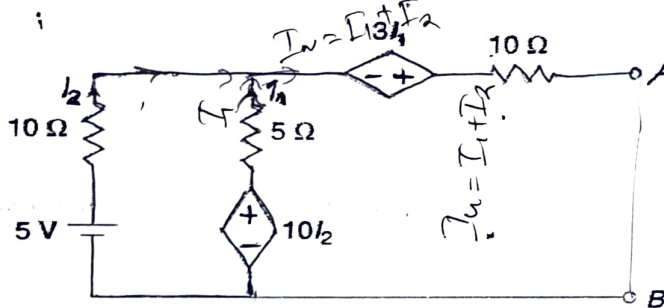


Fig. 5.

(14 Marks) (CO1)

OR

9. Find Thevenin's equivalent network across terminals A and B for Fig. 6.

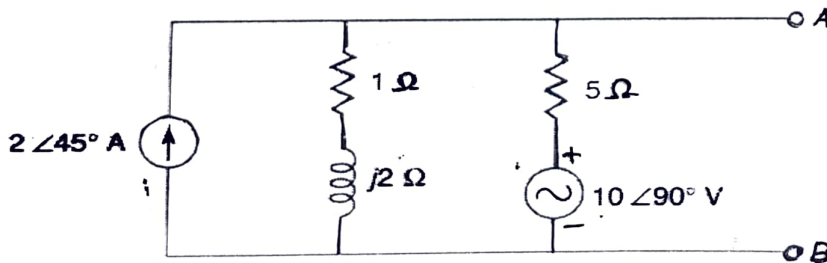


Fig.6.

(14 Marks) (CO1)

10. Find Laplace transform of $\int_0^t f(t)dt$, if the Laplace transform of $f(t)$ is $F(s)$.

(7 Marks) (CO1)

OR

11. State and prove initial value theorem for Laplace transforms.

(7 Marks) (CO1)

Course Outcome (CO)

Sl No.	Description	Questions No.s
ECT205.CO1	Apply mesh/ node analysis or network theorems to obtain steady state response of a linear time invariant networks.	1,2,3,4,6,7,8,9
ECT205.CO2	Apply Laplace transforms to determine the transient behaviour of RLC networks.	5,10,11
